

DipIETE – ET (NEW SCHEME) – Code: DE57

Subject: NETWORKS AND TRANSMISSION LINES

Time: 3 Hours

DECEMBER 2011

Max. Marks: 100

NOTE: There are 9 Questions in all.

- Please write your Roll No. at the space provided on each page immediately after receiving the Question Paper.
- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. A practical current source consists of

- (A) An ideal current source in series with an impedance
- (B) An ideal current source in parallel with an impedance
- (C) Both are correct
- (D) None of the above

b. Compensation theorem is applicable to

- (A) linear networks only
- (B) non linear networks only
- (C) linear and nonlinear networks
- (D) none of the above

c. Peak value of a certain sine wave voltage is 10 V, peak to peak value is

- (A) 10 V
- (B) 20 V
- (C) 5 V
- (D) 7.07 V

d. The maximum value of the coefficient of coupling is

- (A) 100%
- (B) 80%
- (C) more than 100%
- (D) 90%

e. The inverse Laplace transform of $\frac{1}{s}(1 - e^{-as})$ is

- (A) $u(t) - u(t-a)$
- (B) $u(t)$
- (C) $u(t-a)$
- (D) 0

f. The Transfer function of a system having pole-zero plot as in Fig. 1 is

- (A) $\frac{(s-1)}{s(s^2+4)}$
- (B) $\frac{s}{(s-1)(s^2+4)}$
- (C) $\frac{s(s-1)}{s^2+4}$
- (D) $\frac{s^2+2}{(s+1)(s-1)}$


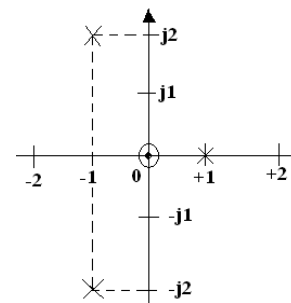


Fig. 1


- g. The h parameters h_{11} and h_{12} are obtained
- (A) by shorting output terminals (B) by opening output terminals
 (C) by shorting input terminals (D) by opening input terminals
- h. If the network short circuit impedance is 16 ohm and open circuit impedance is 25 ohm. Then characteristic impedance of a network is
- (A) 4 Ω (B) 20 Ω
 (C) 5/4 Ω (D) infinite
- i. The propagation constant of a symmetrical T and Π section
- (A) are equal (B) not equal
 (C) None of the above (D) both (A) and (B)
- j. If K is the voltage reflection coefficient then SWR standing wave ratio s is
- (A) $\frac{1-|K|}{1+|K|}$ (B) $\frac{1+|K|}{1-|K|}$
 (C) $1+|K|$ (D) $1-|K|$

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

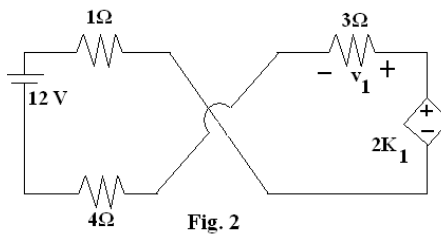- Q.2** a. For the circuit shown in Fig.2, find the power absorbed by each of the elements. (8)



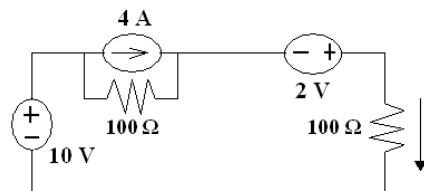- b. Two inductively coupled coils have self inductance $L_1 = 50$ mH, $L_2 = 200$ mH. If the coefficient of coupling is 0.5 (i) find the value of mutual inductance between the coils (ii) what is the maximum possible mutual inductance? (4)
- c. Explain the transformation of sources using transformation find the current I in the load of 100 Ω (Fig.3). (4)



- Q.3** a. Determine the Laplace transform (Fig. 4) (8)
 of $f(t)=t$ for $0 < t < 1$
 $=0$ for $t > 1$

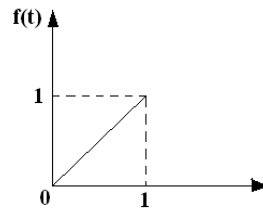


Fig. 4

- b. Verify the initial value theorem for (i) $2 - e^{5t}$ (ii) final value theorem for $2 + e^{-3t} \cos 2t$. (4+4)

- Q.4** a. A 220 V, 100 Hz ac source supplies a series LCR circuit with a capacitor and a coil. If the coil has $50 \text{ m}\Omega$ resistance and 5 mH inductance, find the quality factor and half power frequencies of the circuit. (8)

- b. Find the short circuit admittance parameters for the circuit as shown in Fig.5. (8)

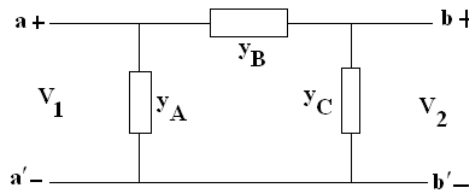


Fig. 5

- Q.5** a. Derive the equations for the elements of an m derived T & π sections. (8)

- b. A 50Ω resistor is connected in series with an inductor having internal resistance, a capacitor and 100 V variable frequency at a frequency of 200 Hz, a maximum current of 0.7 A flows through the circuit and voltage across the capacitor is 200 V. Determine the circuit constants (Fig.6). (8)

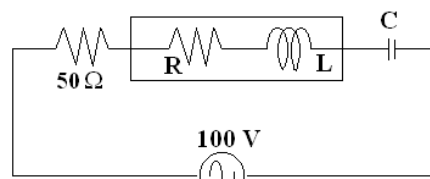


Fig.6

- Q.6** a. Determine the primary line constants of a transmission line / km for a 100 km distortion less line having characteristic impedance $Z_o = 600 \Omega$ terminated in a pure resistive load of 400Ω . When the line is operated at an angular frequency $\omega = 5000 \text{ rad/s}$, α and β were measured to be 2×10^{-3} neper/km $5 \times 10^{-3} \text{ rad/km}$ respectively. (8)

- b. Derive open circuit and short circuit impedance of infinite length transmission line and hence write the expressions for α and β of the lines. (8)

- Q.7** a. A certain lossless transmission line has a characteristic impedance of 400 ohms. Determine the standing wave ratio with the following end impedances
 (i) $Z_L=800 \Omega$ (ii) $Z_L=650-j475 \Omega$. (8)
- b. Explain the principle behind single stub impedance matching on a line. Discuss its limitations also. (8)

- Q.8** a. An inductance of 30 mH and two shunt capacitances of value $0.25 \mu\text{F}$ each are used to form a Π section filter. Find
 (i) type of filter (ii) cut-off frequency, f_c
 (iii) α at 10 kHz (iv) β at 10 kHz (Fig.7) (8)

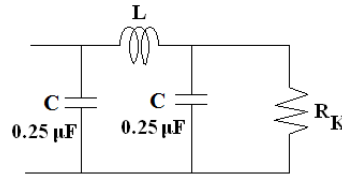


Fig.7

- b. Write short notes on: symmetrical (i) T attenuator and (ii) Π attenuator. (8)
- Q.9** a. State the principle of duality. Obtain the dual of given network (Fig.8). (8)

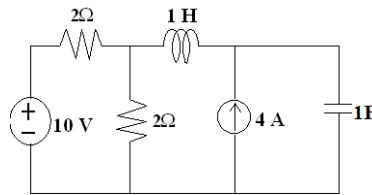


Fig.8

- b. State Milliman theorem. Obtain the equivalent voltage source (V_s) and resistance (R_s) (Fig.9). (8)

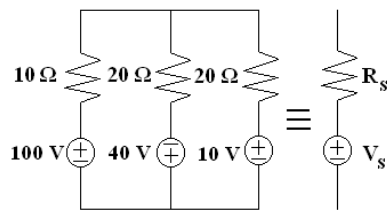


Fig.9