

**AMIETE – ET (Current & New Scheme)**

Time: 3 Hours

**December 2016**

Max. Marks: 100

*PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.*

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

- a. Not taking care of zero adjustment of an instrument before measurement can be classified as
 

(A) systematic error	(B) gross error
(C) random error	(D) dynamic error
- b. A galvanometer recorder has
 

(A) very high input impedance	(B) high input impedance
(C) low input impedance	(D) very low input impedance
- c. A dual beam CRO uses
 

(A) electronic switch	(B) two electron guns
(C) one electron gun	(D) two time base generator circuits
- d. The sensitivity of a Wheatstone bridge depends upon \_\_\_\_\_
 

(A) galvanometer current sensitivity	(B) galvanometer resistance
(C) bridge supply voltage	(D) All of the above
- e. The value of the multiplier resistance on the 500V range of d.c. voltmeter ,that uses 50  $\mu$ A meter movement with an internal resistance of 200ohms is
 

(A) 99.99M $\Omega$	(B) 0.999M $\Omega$
(C) 9.99M $\Omega$	(D) 999M $\Omega$
- f. The chart speed of a recording instrument is 30mm/s. One cycle of the signal being recorded extends over 5mm (time base) then the frequency consumed is
 

(A) 30 cycles	(B) 6 cycles
(C) 0.3cycles	(D) 5 cycles
- g. A 600v voltmeter is specified to accuracy within  $\pm 2\%$  at full scale. The limiting error of the instrument to measure 250V is
 


(A) 4.8%	(B) 3.8%
(C) 8.4%	(D) 8.3%

**Code: AE60/AE111 Subject: INSTRUMENTATION AND MEASUREMENTS**

- h. A voltmeter having a resistance of 998 ohms is connected to a cell of emf 2 volt and internal resistance 2 ohm. The error in the measurement of emf will be  
 (A)  $4 \times 10^{-1}V$  (B)  $2 \times 10^{-1}V$   
 (C)  $4 \times 10^{-3}V$  (D)  $2 \times 10^{-3}V$
- i. Maxwell's bridge is used to measure Q factor in the range of  
 (A) 1-100 (B) 1-10  
 (C) 1-50 (D) 2-200
- j. The sensitivity of a  $500\mu A$  meter movement which is to be used as a dc voltmeter is  
 (A)  $2K\Omega/V$  (B)  $20K\Omega/V$   
 (C)  $0.2K\Omega/V$  (D)  $2\Omega/V$


**Answer any FIVE Questions out of EIGHT Questions.  
 Each question carries 16 marks.**

- Q.2** a. Distinguish between direct and indirect methods of measurement. Give examples to support your answer. (8)
- b. A voltmeter having a sensitivity of  $1.5K \Omega/ V$  reads 80V on its 150 V scale when connected across an unknown resistor in series with a milli-ammeter. When milli-meter reads 15mA, (8)  
 Calculate (i) apparent resistance of the unknown resistor  
 (ii) Actual resistance of the unknown resistor and  
 (iii) Error due to the loading effect of voltmeter
- Q.3** a. A Kelvin's bridge is shown in fig. below, the ratio of  $R_a$  to  $R_b$  is 1200 ohms  $R_1=10$  ohms and  $R_1=0.5R_2$ . Calculate unknown resistance  $R_x$ . (8)

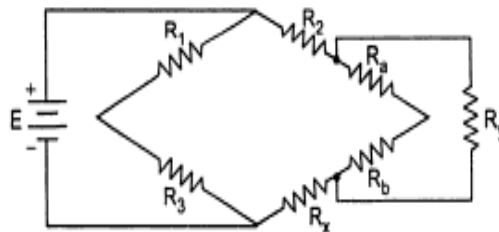

**Fig.1**


- b. How Schering Bridge is used for the measurement of unknown capacitance? Derive its balance equation. (8)
- Q.4** a. Convert a basic D'Arsonval movement with an internal resistance of 100ohm and full scale deflection of 10mA into a multirange dc voltmeter with ranges from 0-5V, 0-50V, 0-100V. (8)

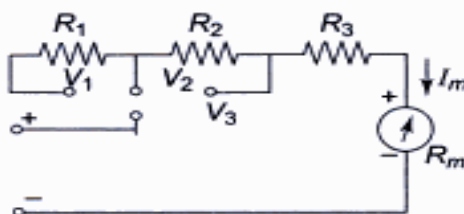

**Fig.2**

**Code: AE60/AE111 Subject: INSTRUMENTATION AND MEASUREMENTS**

- b. Calculate the value of the multiplier resistor for a 10V rms ac range on the voltmeter shown in fig. below: (8)

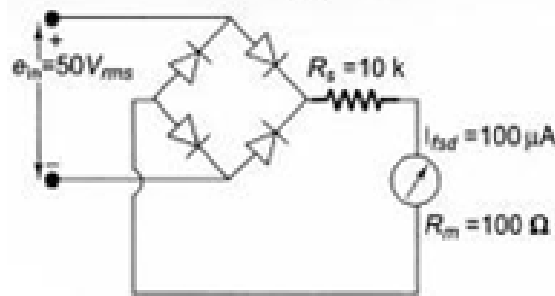

**Fig.3**

- Q.5** a. Explain with the help of a neat diagram the working of a Universal Counter for measurement of frequency and time period. (8)
- b. Describe the circuit and working of a Q-meter. Describe its applications. (8)
- Q.6** a. Describe with the help of a neat block diagram the operation of an AF Sine wave generator. (8)
- b. What are the advantages of dual trace over dual beam CRO for multiple trace? (8)
- Q.7** a. What are the applications of wave analyzer? (8)
- b. What is the dynamic range of a spectrum analyzer with a bandwidth of 30KHz, a noise figure of 15dB and a third order intercept of +25 dBm? (8)
- Q.8** a. Explain the working of X-Y recorder. Give its applications. (8)
- b. Discuss in detail the objectives and requirements of recording data. (8)
- Q.9** a. What are the objectives of data acquisition system? (8)
- b. (i) Calculate the strain in a specimen if the attached strain gauge has a strain factor of 2, a resistance of 120ohms and the change in resistance measured is 0.1ohms. (4)
- (ii) Calculate the gauge factor of a strain gauge made from a material that acts like a perfectly incompressible deforming elastically at strain. (assuming the resistivity doesn't change with strain)? (4)