

DiplETE - ET (Current & New Scheme)

Time: 3 Hours

December 2016

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Q2 TO Q8 CAN BE ATTEMPTED BY BOTH CURRENT AND NEW SCHEME STUDENTS.
- Q9 HAVE BEEN GIVEN INTERNAL OPTIONS FOR CURRENT SCHEME (CODE DE56) AND NEW SCHEME (CODE DE106) STUDENTS.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

- a. Which of the following is not a unipolar device _____
- (A) JFET (B) MOSFET
(C) IGFET (D) BJT
- b. The trans-conductance curve of a JFET is _____
- (A) Linear (B) A straight line
(C) Non linear (D) Zero
- c. The Voltage gain of an inverting amplifier using OP-AMP is _____.
- (A) $-\frac{R_f}{R_1}$ (B) $\frac{R_f}{R_1}$
(C) $1 + \frac{R_f}{R_1}$ (D) $1 - \frac{R_f}{R_1}$
- d. In a class-AB power amplifier, the output current flows for _____.
- (A) Full-cycle (B) More than half-cycle
(C) Less than half-cycle (D) Half-cycle
- e. A coupling capacitor transmits _____ but blocks _____.
- (A) DC, AC (B) AC, DC
(C) DC, DC (D) AC, AC
- f. A class A amplifier is biased _____
- (A) At the midpoint of load line (B) At cutoff
(C) At saturation (D) None of these

- g. CMMR of a differential amplifier is expressed as _____
 (A) A_d / A_c (B) A_c / A_d
 (C) $A_d \cdot A_c$ (D) $A_d + A_c$
- h. Which of the following IC is an OP-AMP _____
 (A) IC 555 (B) IC 741
 (C) IC 7805 (D) IC 723
- i. _____ is used to obtain a square waveform from a sawtooth waveform
 (A) Clamper circuit (B) Monostable multivibrator
 (C) Astable multivibrator (D) Schmitt trigger
- j. The Time period of IC 555 Astable multivibrator is _____
 (A) $T = 0.69(R_A + 2R_B)C$ (B) $T = 1.1(R_A + 2R_B)C$
 (C) $T = 0.69(2R_A + R_B)C$ (D) $T = 1.1RC$

**Answer any FIVE Questions out of EIGHT Questions.
 Each question carries 16 marks.**

- Q.2** a. With the help of neat diagrams, explain the various isolation techniques used in IC's. (8)
- b. Describe the various ways for fabricating P-N-P transistor with the help of diagrams. (8)
- Q.3** a. Draw the h-parameter equivalent circuit of a Common Emitter Amplifier circuit and derive an expression for its (i) input impedance, (ii) output impedance, (iii) voltage gain and (iv) current gain. (10)
- b. The transistor in the CE circuit shown in Fig.1 has the following parameters: $h_{ie} = 2.1k\Omega$, $h_{fe} = 75$, and $h_{oe} = 1\mu S$. Calculate the
 (i) Circuit input impedance (ii) Output impedance
 (iii) Voltage gain (6)

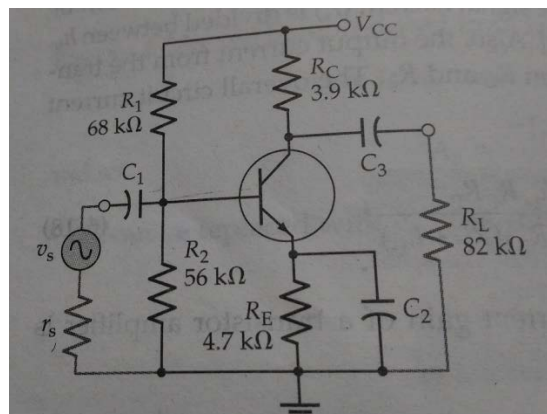


Fig. 1 Common Emitter (CE) circuit

- Q.4** a. Draw and explain the operation of N-channel Depletion – Enhancement mode of MOSFET. Sketch drain and transfer characteristics for an n-channel DE-MOSFET. (8)
- b. Define the following FET parameters: (4)
 (i) Transconductance (g_m)
 (ii) Output Admittance
- c. Draw the symbols of N & P - channel JFET, N & P - channel EMOSFET, N-channel DE-MOSFET and N-channel VMOSFETs. (4)
- Q.5** a. With the help of a neat circuit diagram, explain the working of a Class-B transformer-coupled power amplifier and derive an expression for its collector efficiency. (10)
- b. Calculate the total power supplied to a 3 ½ digit LED display when it indicates 1888. A 5V supply is used, and each LED has a 10 mA current. (6)
- Q.6** a. Draw the circuit of inverting and non-inverting amplifiers using OP-AMP when feedback resistor is connected between input and output. Derive the closed loop gain of (i) inverting amplifier and (ii) non- inverting amplifier. (12)
- b. Define Slew Rate. What causes the slew rate? (4)
- Q.7** a. Explain the working of the following circuits using OP-AMP with circuit diagrams: (10)
 (i) Half-Wave Rectifier (ii) Peak Detector
- b. Draw the circuit diagram of Inverting Summing Amplifier and derive an expression for its output voltage. (6)
- Q.8** a. Draw the circuit diagram of RC Phase Shift Oscillator and derive the expression for frequency of oscillation. (8)
- b. A 555 timer is configured to run in Astable mode with $R_A = 6.8 \text{ K}\Omega$, $R_B = 3.3 \text{ K}\Omega$ and $C = 0.1 \mu\text{F}$. Calculate (8)
 (i) T_{High} (ii) T_{Low}
 (iii) Free running frequency (iv) Duty cycle D
- Q.9 (For Current Scheme students i.e. DE56)**
- a. List and explain the characteristics of three terminal IC voltage regulators. (4)
- b. Draw the circuit of successive approximation type Analog to Digital Converters and explain its operation. (8)
- c. Write the important features of LM380 monolithic audio Power amplifier. (4)
- Q.9 (For New Scheme students i.e. DE106)**
- a. Draw the Circuit of Series-Parallel arrangement of solar cells and explain its operation with the help of solar cell characteristics. (8)
- b. Explain in detail, the working of R-2R Ladder Digital to Analog Converter with the help of neat circuit diagrams. (8)