

DipIETE – ET/CS (Current & New Scheme)

Time: 3 Hours

December 2016

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

- The Gray code of $(10111011)_2$ is _____
 (A) 10011010 (B) 10011011
 (C) 01100111 (D) 11100110
- The Hexadecimal number equivalent of $(1001\ 01011101)_2$ is _____
 (A) $(95D)_{16}$ (B) $(94D)_{16}$
 (C) $(95C)_{16}$ (D) $(95B)_{16}$
- $A + \bar{A}B$ is same as _____
 (A) B (B) A+B
 (C) A.B (D) 1
- In Karnaugh map, Looping Groups of Eight is also called as _____
 (A) Pair (B) Octet
 (C) Quad (D) Cell
- In a RS NAND latch, when R=1 and S=1, then Q(t+1) will be _____
 (A) 1
 (B) 0
 (C) 1 or 0 depending on the value Q(t)
 (D) $\bar{Q}(t)$
- The logical expression for SUM of the full adder is _____
 (A) $A \oplus B \oplus C$ (B) $\overline{A + B + C}$
 (C) $\overline{A \oplus B \oplus C}$ (D) $\overline{A.B.C}$
- A decade counter has _____ no of states count
 (A) 9 (B) 8
 (C) 10 (D) 11
- How many lines are required to address 4096x8 memory chip _____
 (A) 9 (B) 12
 (C) 10 (D) 8

- i. An N- bit register requires _____ no of flip flops
 (A) N-1 (B) 2^N
 (C) N (D) 2^{N-1}
- j. The size of BCD Decoder is _____
 (A) 10x4 (B) 4x10
 (C) 16x4 (D) 4x16

**Answer any FIVE Questions out of EIGHT Questions.
 Each question carries 16 marks.**

- Q.2** a. What are the advantages and limitations of digital techniques? (6)
 b. Convert the decimal number 104.25 to its equivalent binary number. (4)
 c. Convert the following numbers first into Binary code and then into Gray Code
 (i) $(FBC)_{16}$ (ii) $(743)_8$ (3x2)
- Q.3** a. Minimize the logic function $F(W, X, Y, Z) = \Sigma m(2,3,4,5,6,7) + d(8,14,15)$ using K-maps and implement it with NAND gates only (10)
 b. By using boolean algebra, prove that $[\overline{A\overline{B}} (C+BD) + \overline{A\overline{B}}] C = \overline{A\overline{B}} C$ (6)
- Q.4** a. Draw and explain the operation of JK Flip Flop with the help of logic diagram. Also draw its truth table and timing diagram. (8)
 b. How JK Flip Flop can be used as T-Flip Flop and D- Flip Flop? (4)
 c. What is the difference between Latch and Flip Flop? (4)
- Q.5** a. Explain in detail, how two half adders and an OR gate can be used to implement a Full Adder? (9)
 b. What are the various ways of representing signed number? Explain with example. (7)
- Q.6** a. Explain the operation of Decade Counter with the help of neat diagram. Also draw its timing diagram. (10)
 b. Differentiate between Asynchronous Counter and Synchronous Counter. (6)
- Q.7** a. Design 1x4 demultiplexer. (6)
 b. What is a Decoder? Draw the truth table for 4x16-line Decoder and implement the logic diagram from the truth table. (10)
- Q.8** a. Design MOD5 synchronous counter and draw its logical diagram. (8)
 b. Draw and explain the logic diagram for 4-bit Serial In Parallel Out (SIPO) Shift Register. (8)
- Q.9** a. Draw and explain the internal organization of 64x4 RAM in detail. (10)
 b. Explain the operation of dynamic memory cell. (6)