

Code: AE54/AC54/AT54/AE104

Subject: LINEAR ICs & DIGITAL ELECTRONICS

AMIETE – ET/CS/IT (Current & New Scheme)

Time: 3 Hours

DECEMBER 2018

Max. Marks: 100


PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions, selecting at least TWO questions from each part, each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

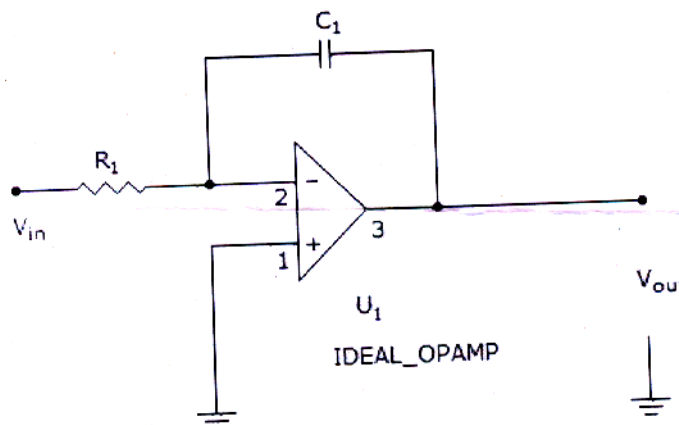- a. The most popular form of IC package is
 (A) TO-5 (B) DIL
 (C) Flatpack (D) None of these
- b. A 22 kΩ resistor and a 0.02 F capacitor are connected in series to a 5 V source. How long will it take the capacitor to charge to 3.4V?
 (A) 0.44 ms (B) 0.501 ms
 (C) 0.66 ms (D) 0.70 ms
- c. What is output waveform in below circuit.



- (A) sine wave (B) square wave
 (C) saw tooth wave (D) triangle wave
- d. A differential amplifier
 (A) is a part of an Op-amp (B) has one input and one output
 (C) has two outputs (D) Both (A) and (B)

Code: AE54/AC54/AT54/AE104

Subject: LINEAR ICs & DIGITAL ELECTRONICS

- e. In order for an output to swing above and below a zero reference, the op-amp circuit requires
 (A) a resistive feedback network (B) zero offset
 (C) a wide bandwidth (D) a negative and positive supply
- f. What is the maximum possible range of bit-count specifically in n-bit binary counter consisting of 'n' number of flip flops?
 (A) 0 to 2^{n-1} (B) 0 to 2^n
 (C) 0 to 2^{n+1} (D) 1 to 2^{n+1}
- g. The bit sequence 0010 is serially entered (right-most bit first) into a 4-bit parallel out shift register that is initially clear. What are the Q outputs after two clock pulses?
 (A) 1000 (B) 1111
 (C) 0000 (D) 0110
- h. The simplest equation which implements the K-map shown below is:

	\bar{C}	C
$\bar{A} \bar{B}$	0	0
$\bar{A} B$	1	1
A B	1	1
A \bar{B}	0	1

- (A) $AB\bar{C} + ABC + A\bar{B}C$ (B) $X = AC + B$
 (C) $AB + \bar{A}B$ (D) A
- i. Convert the binary number 1001.0010 to decimal
 (A) 90.125 (B) 12.5
 (C) 9.125 (D) 125
- j. A 16-input multiplexer is to be used to perform parallel-to-serial data conversion. Which of the following counters would be required to provide the data select inputs?
 (A) MOD 8 (B) MOD 16
 (C) MOD 4 (D) MOD 2

PART - A

Answer at least TWO questions. Each question carries 16 marks.

- Q.2** a. (i) What are monolithic integrated Circuits?
 (ii) Draw and explain Block Diagram of an Op Amp. (10)
- b. Describe internal Circuit of Operational Amplifier. (6)

Code: AE54/AC54/AT54/AE104

Subject: LINEAR ICs & DIGITAL ELECTRONICS

- Q.3** a. (i) Explain in details about the Effect of Slew Rate on Sinusoidal Signals and Power Bandwidth.
(ii) Explain with necessary sketches V to I converter. **(10)**
- b. Explain block diagram Instrumentation amplifier. **(6)**
- Q.4** a. (i) Explain with neat sketches OP-AMP using diodes.
(ii) Draw only circuit and waveforms of comparator. **(8)**
- b. Describe operation of Differentiator with necessary equations. **(8)**
- Q.5** a. Explain 555 Timer as astable Multivibrator. **(8)**
- b. Give details about R-2R Ladder Digital to Analog Convertor (DAC). **(8)**

PART - B**Answer at least TWO questions. Each question carries 16 marks.**

- Q.6** a. Write short notes on:-
(i) NOR gate latch
(ii) D Latch **(10)**
- b. Explain about Propagation Delay in Ripple Counters. **(6)**
- Q.7** a. What is Priority encoder? Draw and explain the truth table of decimal to BCD priority encoder. **(8)**
- b. Explain with neat sketches Magnitude comparator circuit. **(8)**
- Q.8** a. Why NAND and NOR gates are called universal gates? **(10)**
- b. (i) Draw the logic circuit for the identity $Y = ABC + ABC + B$
(ii) Simplify the expression and draw a logic circuit for the same. **(6)**
- Q.9** a. (i) What do you understand by complement, compare 1's complement and 2's complement in tabular form?
(ii) Explain the following codes:-
Excess 3 code, Grey code **(8)**
- b. Perform the following conversions: **(8)**
- | | |
|--|--|
| (i) $(110011011001)_2 = (\text{_____})_{10}$ | (ii) $(268)_{10} = (\text{_____})_{16}$ |
| (iii) $(39.12)_{10} = (\text{_____})_2$ | (iv) $(1054)_8 = (\text{_____})_{10}$ |
| (v) $(2040.125)_{10} = (\text{_____})_{16}$ | (vi) $(1001101.1011)_2 = (\text{_____})_8$ |
| (vii) $(153)_{10} = (\text{_____})_8$ | (viii) $(0.513)_{10} = (\text{_____})_8$ |