

**DipIETE – ET (New Scheme)**

Time: 3 Hours

**DECEMBER 2018**

Max. Marks: 100

*PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.*

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following:** (2×10)

- a. In Z- parameter representation if  $Z_{21}=Z_{12}$ , the network is:  
 (A) Bilateral (B) Symmetrical  
 (C) Balanced (D) Inverse
- b. Bridged T-network can be used as  
 (A) Attenuator (B) Low pass filter  
 (C) High pass filter (D) Band pass filter
- c. The time constant of a series R-C circuit is:  
 (A) RC (B) R/C  
 (C)  $R^2C$  (D)  $RC^2$
- d. A resonance curve for a series circuit is a plot of frequency verses  
 (A) Voltage (B) Impedance  
 (C) Current (D) Reactance
- e. The Inverse Laplace transform of  $2/(s+1)$  is  
 (A)  $2(t+1)$  (B)  $2e^{-2t}$   
 (C)  $e^{-2t}$  (D)  $2e^{-t}$
- f. Terminating half sections used in composite filters are built with the following.  
 (A)  $m=0.6$  (B)  $m=0.8$   
 (C)  $m=0.3$  (D)  $m=1$
- g. A transmission line works as  
 (A) Attenuator (B) LPF  
 (C) HPF (D) Neither of these
- h. Propagation constant in a lossless line is given by  
 (A)  $L/C$  (B)  $LC$   
 (C)  $j\omega\sqrt{LC}$  (D)  $1/\sqrt{LC}$

- i. VSWR in a transmission line lies between  
 (A) 0 to  $\infty$  (B) 1 &  $\infty$   
 (C) 0 and 1 (D) 0 and  $Z_0$
- j. The reciprocity theorem applies to only one of the network.  
 (A) Bilateral n/w only (B) Linear as well as non linear  
 (C) Linear Bilateral (D) None of these

**Answer any FIVE Questions out of EIGHT Questions.**  
**Each question carries 16 marks.**

- Q.2** a. Explain Millman Theorem with the help of suitable example. (8)
- b. Find the current in the 1ohm resistor of fig 1 using Norton's theorem. (8)

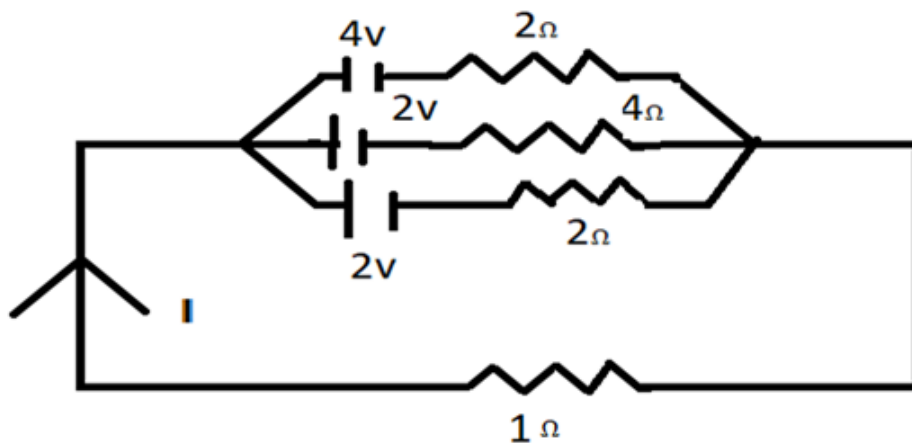


Fig. 1

- Q.3** a. Explain the Laplace transform of singularity function with an example? (8)
- b. Explain initial & final value theorem. (4)
- c. Explain convolution theorem. (4)
- Q.4** a. Explain the condition of reciprocity in two port representation. (8)
- b. In a two port network  $Z_{11}=100\Omega$ ,  $Z_{21}=120\Omega$ ,  $Z_{12}=120\Omega$  and  $Z_{22}=50\Omega$ , compute Y-parameters. (8)
- Q.5** a. Explain in detail about secondary constants of transmission line. (8)
- b. A line has following primary constants per km loop  
 $R=26\Omega$   $L=16mH$   $C=0.2\mu F$   $G=5\mu mho$   
 Find the characteristic impedance at  $\omega=7500$  rad/sec. (8)

- Q.6** a. Derive an expression for the input impedance of a lossless line. (8)
- b. A low loss transmission line has characteristic impedance of  $80\Omega$  and is terminated by another impedance of  $(110-j70)\Omega$ . Find
- (i) Reflection Co-efficient
- (ii) Standing wave Ratio (8)
- Q.7** a. Derive a relation between VSWR and reflection co-efficient in ultra high frequency lines. (8)
- b. What are the advantages of double stub matching over single stub matching? (8)
- Q.8** a. Explain in detail balanced and unbalanced attenuator with example. (8)
- b. Design an m-derived T section Low pass filter having cut off frequency  $f_c=8$  kHz , design impedance  $R_o = 600 \Omega$  and frequency of infinite attenuation  $f_\infty=10$  kHz? (8)
- Q.9** a. Drive expression between resonance frequency and Q in terms of lower and upper frequencies of a series RLC Network. (8)
- b. A 150 mH inductor with  $500 \Omega$  self resistance is in parallel with 5 nF capacitor. Find resonance frequency of the circuit. (8)