

**DiplETE – ET (Current Scheme)**

Time: 3 Hours

**DECEMBER 2018**

Max. Marks: 100

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

- Q.1 Choose the correct or the best alternative in the following: (2×10)**
- a. Where is the ROC defined or specified for the signals containing causal as well as anti-causal terms Multiplication by  $e^{-sT_0}$  in the time domain
    - (A) Greater than the largest pole
    - (B) Less than the smallest pole
    - (C) Between two poles
    - (D) Cannot be defined
  - b. Which result is obtained by the addition of a step to a ramp function
    - (A) Step function shifted by an amount equal to ramp
    - (B) Ramp function shifted by an amount equal to step
    - (C) Ramp function of zero slop
    - (D) Step function with zero slop
  - c. Production of induced current in one coil due to production of current in neighbouring coil is
 

(A) Electromagnetism	(B) Induction
(C) Mutual induction	(D) Steady current
  - d. Voltage across inductor is equals to time derivative of total
 

(A) Outflux linkage	(B) Influx linkage
(C) Capacitance	(D) Inductance
  - e. According to Millman's Theorem, if there are n voltage sources with n internal resistances respectively, which are in parallel then these sources are replaced by?
    - (A) Single current source  $I'$  in series with  $R'$
    - (B) Single voltage source  $V'$  in series with  $R'$
    - (C) Single current source  $I'$  in parallel to  $R'$
    - (D) Single voltage source  $V'$  in parallel to  $R'$
  - f. An ideal voltage source should have
 


(A) Large value of e.m.f	(B) Small value of e.m.f
(C) Zero source resistance	(D) Infinite source resistance

- g. When power cables laid in proximity of communication cables what is the minimum horizontal and vertical clearance for separation of these two cables?  
 (A) 1.0 m (B) 0.6 m  
 (C) 2.4 m (D) 4.0 m
- h. A circuit is said to be selective if it has a \_\_\_\_\_ peak and \_\_\_\_\_ bandwidth.  
 (A) Blunt, narrow (B) Sharp, narrow  
 (C) Sharp, broad (D) Blunt, broad
- i. Fourier transform of unit impulse at origin is  
 (A) Undefined (B) Infinity  
 (C) Zero (D) One
- j. What is the Q factor of a selective circuit?  
 (A) Very low (B) Very high  
 (C) Zero (D) Infinity

Answer any FIVE Questions out of EIGHT Questions.

Each question carries 16 marks.

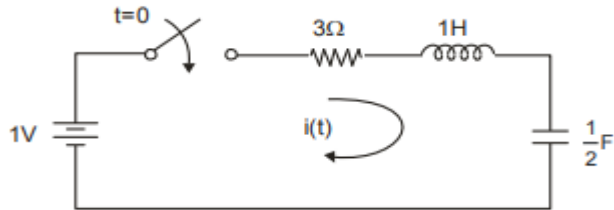- Q.2 a. For the circuit shown below solve for  $i(t)$  using Laplace transform with switch closed at  $t = 0$ . Assume zero initial conditions.




(8)

- b. Derive and explain the linearity and shifting property of Laplace transform

(8)

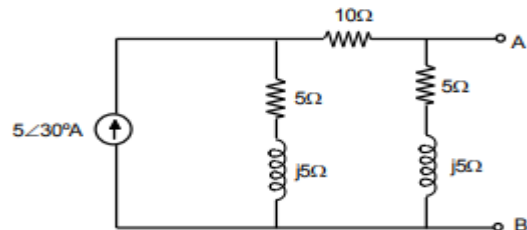- Q.3 a. Obtain the Thevenin's and Norton's equivalent circuit across the terminals A-B for the circuit shown here.






(8)

- b. State and prove Reciprocity Theorem. and Maximum Power Transfer Theorem

(8)

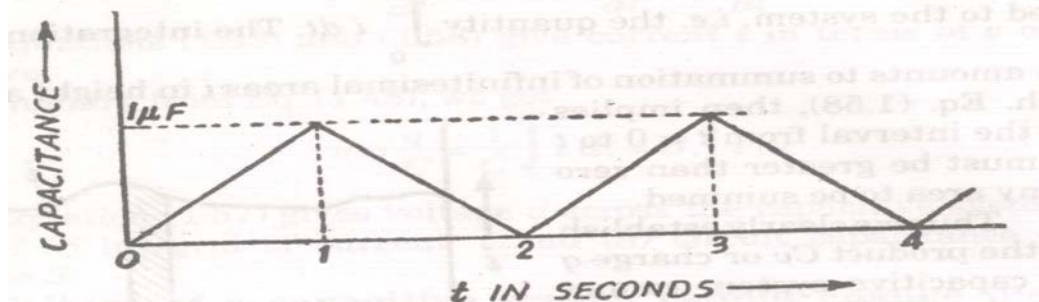- Q.4 a. A condenser has one plate so rotated that the capacitance varies as shown in the following figure. A battery of constant voltage 10 volts is connected across the condenser. Find (i) current during time  $t = 0$  to  $t = 1$  second. (ii) Charge accumulated across the condenser at  $t = 1$  second (iii) power in the condenser at  $t = 1$  second and (iv) energy stored in the condenser at  $t = 1$  second.



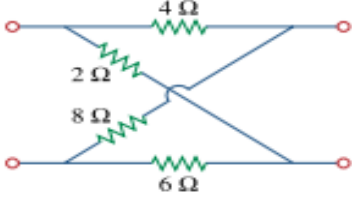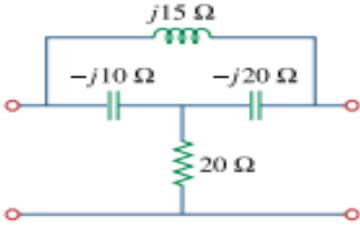- b. Explain transformation of energy sources using suitable Example. (8)
- Q.5** a. Determine the z and y parameters for the given circuit (8)
- 
- b. Determine the transmission parameters of the circuit given here. (8)
- 
- Q.6** a. Compute the quality factor and damping factor of simple parallel R, L, C network (all elements parallel to each other) for the following conditions and comment on Quality factor and damping factor. (8)
- $R = 1 \text{ k } \Omega$ ,  $C = 10 \text{ mF}$  and  $L = 1 \text{ H}$
  - $R = 1 \text{ k } \Omega$ ,  $C = 1 \text{ F}$  and  $L = 1 \text{ H}$
  - $R = 1 \text{ k } \Omega$ ,  $C = 100 \text{ mF}$  and  $L = 1 \text{ H}$
  - $R = 1 \text{ k } \Omega$ ,  $C = 100 \text{ mF}$  and  $L = 0.1 \text{ mH}$
  -
- b. Derive the resonance frequency, Q factor and damping factor for series RLC circuit. (8)
- Q.7** a. A distortion less line operating at 120 MHz has  $R = 20 \text{ } \Omega/\text{m}$ ,  $L = 0.3 \text{ } \mu\text{H}/\text{m}$ , and  $C = 63 \text{ pF}/\text{m}$ . (i) Determine  $\gamma$ ,  $u$ , and  $Z_0$ . (ii) How far will a voltage wave travel before it is reduced to 20% of its initial magnitude? (iii) How far will it travel to suffer a  $45^\circ$  phase shift? (8)
- b. Define transmission line coefficient and derive its formula in terms of  $Z_i$  and  $Z_0$  (8)
- Q.8** a. A lossless transmission line is 80 cm long and operates at a frequency of 600 Mhz. The line parameters are  $L = 0.25 \text{ } \mu\text{H}/\text{m}$  and  $C = 100 \text{ pF}/\text{m}$ . Find the characteristics impedance, the phase constant, the velocity on the line and the input impedance for  $Z_L = 100 \text{ } \Omega$  (8)
- b. A distortion less line has  $Z_0 = 60 \Omega$ ,  $\alpha = 20 \text{ mN}/\text{m}$ ,  $u = 0.6c$ . Where  $c$  is the speed of light in vacuum Find  $R$ ,  $L$ ,  $G$ ,  $C$  and  $\lambda$  at 100Mhz (8)
- Q.9** a. Give the classification of filters and explain each in brief. (8)
- b. What is attenuator? Classify its types. An attenuator is composed of symmetrical T – section having series arm of  $175 \text{ } \Omega$  each and shunt arm of  $350 \Omega$ . Find the characteristic equation and attenuation (in dB). (8)