

**DiplETE – ET/CS (Current & New Scheme)**

Time: 3 Hours

**DECEMBER 2018**

Max. Marks: 100

*PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.*

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

- The binary equivalent of  $(85.63)_{10}$  is
 

(A) 1010101.10100	(B) 1110101.10100
(C) 1010111.10100	(D) 1010101.11100
- BCD code 01010011 represents decimal number \_\_\_\_\_.
 

(A) 52	(B) 53
(C) 256	(D) 51
- A Karnaugh map with 4 variables has \_\_\_\_\_.
 

(A) 2 cells	(B) 4 cells
(C) 8 cells	(D) 16 cells
- A memory that requires refreshing is \_\_\_\_\_.
 

(A) ROM	(B) SRAM
(C) DRAM	(D) Flash RAM
- The sum of product of  $(A + B'C)(B + C'A)$  is \_\_\_\_\_.
 

(A) $AB + AC'$	(B) $AC + BC$
(C) $AB + AC$	(D) $AC + B'C$
- In a 7 segment display, LEDs a, b and c light up. The decimal number displayed is \_\_\_\_\_.
 

(A) 9	(B) 7
(C) 1	(D) 3
- A multiplexer having 32 data input lines needs \_\_\_\_\_ select lines.
 

(A) 5	(B) 3
(C) 4	(D) 8
- In general the number of states = \_\_\_\_\_, where n is equal to the number of flip-flops.
 

(A) $1/2^n$	(B) $2^n$
(C) $2n$	(D) $n^2$
- A 4 bit modulo-16 ripple counter uses JK flip-flops. If the propagation delay of each flip-flop is 100 nsec, the maximum clock frequency that can be used is equal to \_\_\_\_\_.
 

(A) 2.5 MHz	(B) 5 MHz
(C) 25 MHz	(D) 10 MHz

- j. An 8 bit data is to be entered into a parallel in register. The number of clock pulses required is  
 (A) 2 (B) 1  
 (C) 4 (D) 8

**Answer any FIVE Questions out of EIGHT Questions.  
 Each question carries 16 marks.**

- Q.2** a. What is a Digital System? Explain the advantages and limitations of Digital Techniques over Analog Techniques. (8)
- b. Perform the following conversions. (8)
- (i)  $(111101.011)_2 = ( )_{10}$  (ii)  $(5267)_8 = ( )_{10}$   
 (iii)  $(68B)_{16} = ( )_8$  (iv)  $(1A2.C) = ( )_{10}$
- Q.3** a. Show, that how NAND and NOR gates are universal gates? (8)
- b. Obtain (i) minimal sum of product (ii) minimal product of sum expression for function  $F(A, B, C, D) = \Sigma (0, 2, 3, 6, 7, 8, 10, 11, 12, 15)$ . (8)
- Q.4** a. Draw and explain the operation of JK Flip Flop with the help of logic diagram. Also draw its truth table and timing diagram. (8)
- b. Explain the application of Flip-Flop as a Shift Register using D Flip-Flops. (8)
- Q.5** a. Build a Full Adder using two Half Adders and prove that the addition of two numbers results in subtraction when 2's complement is used. (8)
- b. Perform followings using 2's complement method. (4)
- (i)  $(01001)_2 - (10100)_2$   
 (ii)  $(100101)_2 - (100100)_2$
- c. Draw the circuit diagram of 8 bit parallel adder. (4)
- Q.6** a. What is a Ripple Counter? Draw the logic diagram of 3-bit Ripple Counter and explain its working with the help of timing diagram. (8)
- b. Design 4 bit up/down binary ripple counter. (8)
- Q.7** a. Design a BCD to excess 3 code converter using minimum number of NAND gates. (8)
- b. Design a seven segment decoder that is required to drive an active low seven segment display. (8)
- Q.8** a. Design a mod 7 synchronous counter and calculate its maximum frequency of operation if the flip flop delay time is 8 nano sec and gate delay time is 5 nano sec. (8)
- b. Design 4 bit (serial In/Parallel out shift register), write the truth table with relevant diagram after 5 clock pulses. (8)
- Q.9** a. How will you read and write into a  $16 \times 4$  RAM? Draw a schematic of this RAM and explain the process. (8)
- b. Design a combinational circuit using a ROM that accepts a 3-bit number and generates an output binary number equal to the square of the input number. (8)