

AMIETE – ET/CS (Current & New Scheme)

Time: 3 Hours

DECEMBER 2015

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. CMOS is equal to

- (A) NMOS+ PMOS (B) PMOS+PMOS
(C) VMOS+NMOS (D) None of the above

b. To achieve equal pullup and pulldown times in a CMOS inverter, the P device is usually several times wider than the N device. What is the main reason for this?

- (A) Hole mobility is greater than electron mobility.
(B) Electron mobility is greater than hole mobility.
(C) The P threshold is greater than the N threshold.
(D) The N threshold is greater than the P threshold.

c. Which of the following layers is NOT needed to layout an nMOS transistor?

- (A) Active (B) Via
(C) Poly (D) n-Select

d. In saturation mode of operation drain current I_{ds} depends on

- (A) V_{GS}, V_t (B) V_{DS}, V_{GS}, V_{SB}
(C) V_{GS} (D) None of the above


e. Which equation is correct? V_{NL} = Noise Margin Low, V_{NH} = Noise Margin High

- (A) $V_{NL} = V_{IL(max)} + V_{OL(max)}$ (B) $V_{NH} = V_{OH(min)} + V_{IH(min)}$
(C) $V_{NL} = V_{OH(max)} - V_{IH(max)}$ (D) $V_{NH} = V_{OH(min)} - V_{IH(min)}$

- f. Which logic family combines the advantages of CMOS and TTL?
- (A) BiCMOS (B) TTL/CMOS
(C) ECL (D) TTL/MOS
- g. The total propagation delay time T in Carry Skip Adder is given by
- (A) $T = n/M$ (B) $T = 2(P-1)K_1 + (M-2)K_2$
(C) $T = 2(P-1)K_1$ (D) $T = M/n$
- h. The power consumption is least in CMOS circuits as compared to NMOS and PMOS circuits. This is because, in CMOS
- (A) Both the transistors remain in off-state most of the time.
(B) Small voltages are required.
(C) High value resistors are used
(D) Both the transistors go to on-state simultaneously only for a very short time during change of states
- i. The gate area of the device is
- (A) $A_g = C_{ox} L W$ (B) $A_g = L W$
(C) $A_g = LW/C_{ox}$ (D) $A_g = C_oL$
- j. The fastest memory is
- (A) DRAM (B) ROM
(C) CACHE (D) EPROM

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

 - Q.2** a. Explain the C-V characteristics of Ideal MOS System. Explain Flat Band Voltage. (8)
- b. Explain the different fabrication steps of n well process for CMOS Inverter. (8)
- Q.3** a. Derive the expression for the threshold voltage of a MOS transistor and explain the significance of different parameters present in the equation. (8)
- b. Determine the pull up to pull down ratio for an n MOS inverter driven through one or more pass transistors. (8)
- Q.4** a. Draw the schematic for EX-OR gate using CMOS logic. (8)
- b. Explain Lambda (λ) based design rules. (8)
- Q.5** a. Explain how to estimate wiring capacitances? (8)
- b. Calculate area capacitance values associated with structures occupying more than one layer as shown in figure given below (8)



Typical area capacitance values for MOS circuits

Capacitance	Value in $\text{pF} \times 10^{-4}/\mu\text{m}^2$ (Relative values in brackets)		
	$5 \mu\text{m}$	$2 \mu\text{m}$	$1.2 \mu\text{m}$
Gate to channel	4 (1.0)	8 (1.0)	16 (1.0)
Diffusion (active)	1 (0.25)	1.75 (0.22)	3.75 (0.23)
Polysilicon* to substrate	0.4 (0.1)	0.6 (0.075)	0.6 (0.038)
Metal 1 to substrate	0.3 (0.075)	0.33 (0.04)	0.33 (0.02)
Metal 2 to substrate	0.2 (0.05)	0.17 (0.02)	0.17 (0.01)
Metal 2 to metal 1	0.4 (0.1)	0.5 (0.06)	0.5 (0.03)
Metal 2 to polysilicon	0.3 (0.075)	0.3 (0.038)	0.3 (0.018)

Notes: Relative value = specified value/gate to channel value for that technology.

*Poly. 1 and Poly. 2 are similar (also silicides where used).

- Q.6** a. What is short channel effect? Explain (8)
- b. Explain the difference between static Logic circuits and Dynamic Logic Circuits (8)
- Q.7** a. Design and explain 4 X 4 crossbar switch. (8)
- b. Draw and explain a possible arrangement of the adder elements for both arithmetic and logical functions. (8)
- Q.8** a. Briefly explain the operation of 6T SRAM memory structure with read and write circuitry. Explain their timing diagrams. (8)
- b. Discuss the different ground rules for successful design. (8)
- Q.9** a. Explain the aspects of design tools. (8)
- b. Explain different VLSI design styles. (8)