

DipIETE – ET {NEW SCHEME}

Time: 3 Hours

DECEMBER 2015

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

- a. $\frac{1}{s+a}$ is the Laplace transform of _____
 (A) e^{at} (B) e^{-at}
 (C) se^{at} (D) se^{-at}
- b. The reversal due to interchange of the dependent and independent variables is called _____
 (A) Thevenin's theorem (B) Norton's theorem
 (C) Superposition theorem (D) Principle of duality
- c. Condition for reciprocity in y- parameters is _____
 (A) $Y_{21} = Y_{12}$ (B) $Y_{11} = Y_{22}$
 (C) $Y_{11} = Y_{12}$ (D) $Y_{21} = Y_{22}$
- d. A series RLC circuit draws current at leading power factor at _____
 (A) resonant frequency (B) more than resonant frequency
 (C) less than resonant frequency (D) none of these
- e. In coaxial cables, radiation loss in comparison to open wire line is _____
 (A) lower (B) higher
 (C) same (D) none of these
- f. A transmission line is terminated by its characteristic impedance. The reflection coefficient is _____
 (A) +1 (B) -1
 (C) infinity (D) zero
- g. Characteristic impedance of transmission lines is given by the expression _____
 (A) $Z_0 = \frac{R + j\omega L}{G + j\omega C}$ (B) $Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$
 (C) $Z_0 = \sqrt{(R + j\omega L)(G + j\omega C)}$ (D) $Z_0 = (R + j\omega L)(G + j\omega C)$

- h. Distortion less condition of a transmission line is given by the relation _____
- (A) $Z_0 = \sqrt{\frac{L}{C}}$ (B) $RG = LC$
- (C) $\frac{R}{G} = \frac{L}{C}$ (D) All of these
- i. Attenuator always consist of _____
- (A) resistors only (B) inductors only
- (C) capacitors only (D) All of these
- j. A passive filter which passes all low frequencies up to a cut off frequency and attenuates all high frequencies above the cut off frequency is called _____
- (A) BPF (B) HPF
- (C) both BPF and HPF (D) LPF

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

- Q.2** a. Write the advantages of Laplace transformation. (4)
- b. Find the convolution integral when $f_1(t) = e^{-t}$ and $f_2(t) = e^{-2t}$ (4)
- c. Voltage $V(s) = \frac{1 - 2e^{-s} + e^{-2s}}{s^2}$ is applied as input to a series RL circuit with $R = 2\Omega$, $L = 2$ H. Calculate $i(t)$ using Laplace transform through the circuit. (Assume $i(0^+) = 0$) (8)
- Q.3** a. State and prove maximum power transfer theorem. (8)
- b. A black box consisting of generators and impedances where only two output terminals are available gives the following data:
- (i) Open circuit voltage = 120 volts
- (ii) Short circuit current = 10 Amp
- (iii) When output terminals are connected to a resistance of 8Ω , current flowing = 6Amp., determine Thevenin's equivalent generator. (8)
- Q.4** a. What are h- parameters? Draw equivalent circuit using h-parameters and derive equation for calculating h-parameters. (8)
- b. Find the equivalent π -network for the T-network shown in Fig.1. (8)

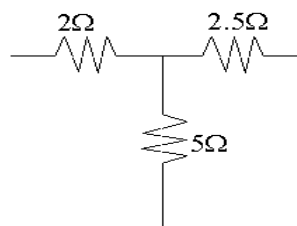


Fig.1

Code: DE107

Subject: NETWORKS & TRANSMISSION LINES

- Q.5** a. Determine the relationship between the resonant frequency f_0 and the half-power frequencies f_1 and f_2 in a series resonating circuit. (8)
- b. A coil with resistance of 20 ohms and induction of 0.2 H is connected in parallel with a 100 μ F capacitor. Calculate the frequency at resonance (f_0) and Q factor. (8)
- Q.6** a. Define and explain the term characteristic impedance and propagation constant of a transmission line. (8)
- b. An open wire transmission line terminated in its characteristic impedance has the following primary constant at 1 KHz. $R = 6 \Omega / \text{km}$; $L = 2 \text{ mH} / \text{km}$; $G = 0.5 \mu\Omega / \text{loop km}$ and $C = 0.005 \mu\text{F} / \text{loop km}$. Calculate (i) characteristic impedance (ii) phase velocity and (iii) the attenuation suffered by a signal in a length of 100 km. (8)
- Q.7** a. Define VSWR for transmission line. (3)
- b. Open and short circuit of a transmission line at 1.6 kHz are $900 \angle -30^\circ$ ohms and $400 \angle -10^\circ$ ohms respectively. Calculate its characteristic impedance. (6)
- c. Derive an expression for the input impedance of a lossless transmission line when line is terminated with any impedance Z_R . (7)
- Q.8** a. Describe double stub matching of a transmission line. What are the advantages of this method over single stub matching? (8)
- b. A low loss transmission line has characteristic impedance of 70Ω and is terminated by another impedance of $(115 - j80) \Omega$. Find (i) reflection co-efficient and (ii) standing wave ratio. (8)
- Q.9** a. Draw T and π sections of a constant - K high pass filter. Derive an expression for cut-off frequency. (4+4)
- b. Design a symmetrical Bridged-T network with an attenuation of 40 dB and an impedance of 600 ohms. (8)