

AMIETE – ET

Time: 3 Hours

DECEMBER 2012

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. Which of them is a non linear device?

- | | |
|----------------|------------------|
| (A) Capacitor | (B) Inductor |
| (C) Transistor | (D) All of these |

b. At time $t=0$, if the switching of source is done, then an initially relaxed capacitor behaves as a

- | | |
|--------------------|--------------------|
| (A) Short circuit | (B) Open circuit |
| (C) Voltage source | (D) Current source |

c. If a function $f(t)$ is shifted by 'T', then is correctly represented as

- | | |
|--------------------|-------------------|
| (A) $f(t-T)U(t)$ | (B) $f(t)U(t-T)$ |
| (C) $f(t-T)U(t-T)$ | (D) $f(t-T)(t-T)$ |

d. Laplace transform of function $e^{-2t} \sin 2t$ is

- | | |
|--------------------|--------------------|
| (A) $2/(s^2+2s+8)$ | (B) $4/(s^2+2s+8)$ |
| (C) $2/(s^2+4)$ | (D) $4/(s^2+4)$ |

e. Nortons theorem is valid for

- | | |
|--------------------------|--------------------------|
| (A) Linear loads only | (B) bilateral loads only |
| (C) Nonlinear loads only | (D) all types of load |

f. A lattice with $Z_a=2s$ and $Z_b=2/s$ is terminated in a load $R_L=2$. Then input impedance is

- | | |
|--------------------------------|--|
| (A) An inductor of value 2 H | (B) A capacitor of value $\frac{1}{2}$ F |
| (C) A resistor of value 2 ohms | (D) A resistor of value $\frac{1}{2}$ ohms |

- g. Use CG:GC transformation to obtain the element values of an LP filter given the values for the HP filter as $C=2F$ and $R=2.5\Omega$. R' and C' in LP filter have respectively values
- (A) $\frac{1}{2.5}\Omega, 1/2 F$ (B) $2\Omega, \frac{1}{2.5}F$
 (C) $2\Omega, 2.5F$ (D) $\frac{1}{2}\Omega, \frac{1}{2.5}F$
- h. Given $Z(s)=(s+2)/(s+1)(s+3)$. The number of elements in a canonical realization is
- (A) 2 (B) 3
 (C) 4 (D) 5
- i. In a series RLC circuit, the maximum voltage across the capacitor occurs at a frequency
- (A) Equal to resonant frequency (B) Greater than resonant frequency
 (C) Smaller than resonant frequency (D) Both (A) and (B)
- j. The h parameter of two port network can be obtained by setting
- (A) $I_1 = 0$ or $V_2 = 0$ (B) $I_1 = 1A$ or $V_2 = 0$
 (C) $I_1 = 0$ or $V_2 = 1V$ (D) All of these

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

- Q.2** a. For the circuit shown in Fig.1, determine the equivalent voltage source and equivalent current source across the terminal 'a' and 'b' (8)

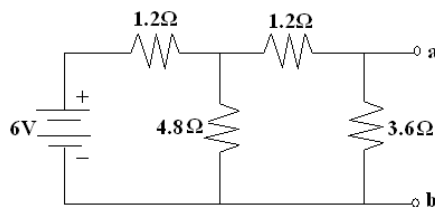


Fig. 1

- b. Express the node voltage V in Fig. 2 as a function of time if $R=1/2\Omega$. Given that the initial voltage across the capacitor (C) is +10V and there is no initial current through the inductor (L). (8)

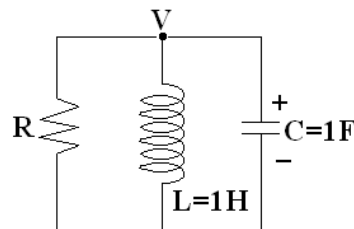


Fig. 2

- Q.3** a. Fig.3 shows a two loop network. Assuming that prior to closing of switch K (at $t=0$) there was no voltage across the capacitor nor any current through the inductor. Find $\frac{di_1}{dt}(t = 0^+)$, $\frac{di_2}{dt}(t = 0^+)$, $\frac{d^2i_1}{dt^2}(t = 0^+)$ and $\frac{d^2i_2}{dt^2}(t = 0^+)$ (8)

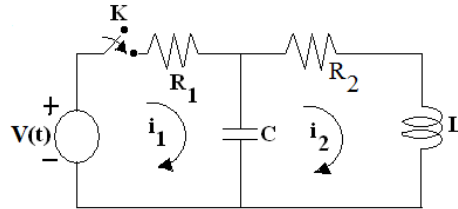


Fig. 3

- b. In the given network, the switch K is opened at $t=0$. At $t=0^+$, solve the values of V , $\frac{dV}{dt}$ and $\frac{d^2V}{dt^2}$, if $I=10A$, $R=1000\Omega$ and $C=1\mu F$ (Fig. 4) (8)

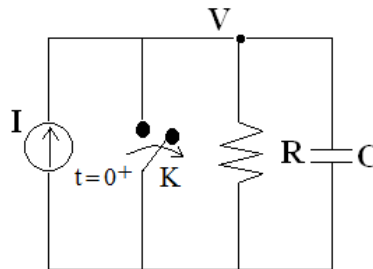


Fig. 4

- Q.4** a. At $t=0$, a switch is closed, connecting a voltage source $V=V_m \sin \omega t$ to a series RL circuit. Find the expression for current by using method of Laplace transform. (8)
- b. For the circuit as shown in Fig. 5 obtain the value of transfer function $H(s)$ and impulse response $h(t)$ if the output is taken as voltage across the capacitor. (8)

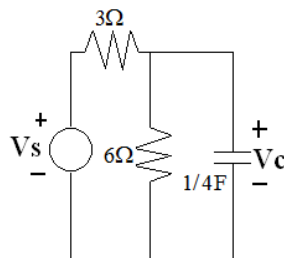


Fig. 5

- Q.5** a. State and explain Norton's theorem. Obtain the Thevenin's equivalent of circuit shown in Fig.6. (8)
- b. State and prove Superposition theorem. (8)

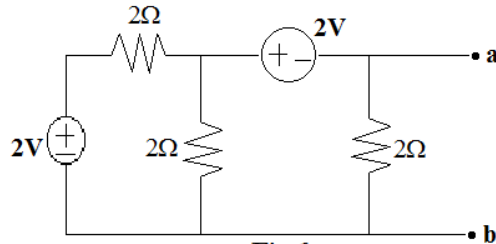


Fig.6

- Q.6**
- Define Y and h parameters of a two-port. Hence obtain the relations between them. (8)
 - For the circuit as shown in Fig.7, find the Z-parameters. (8)

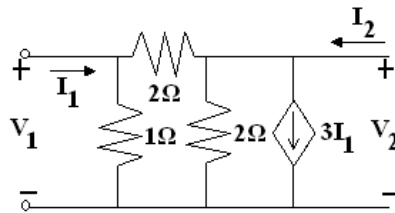


Fig.7

- Q.7**
- Write the properties of positive real functions. (8)
 - For the given polynomial $P(S)=S^6+3S^5+4S^4+6S^3+13S^2+27S+18$, determine the number of zeros lying in the right half of S-plane, left half of S-plane and on the imaginary axis of S-plane. (8)

- Q.8**
- Given $F(S) = \frac{6(S+2)(S+4)}{S(S+3)}$, find the continued function expression and hence synthesise the network for the case when F(S) is an impedance Z(S). (8)

- Given $\text{Real}[Z_d(j\omega)] = \frac{18\omega^2 + 48}{\omega^4 + 17\omega^2 + 16}$. Obtain $Z_d(S)$. Show that $Z_d(S)$ is RC impedance and realize it in Cauer form. (8)

- Q.9**
- Design a low pass T and π section filter having a design $R_o=600$ ohm and cut-off frequency=2000 Hz. (8)

- Synthesize the function given below with a 1 ohm termination $Z_{21}(s) = \frac{2}{s^3 + 3s^2 + 4s + 2}$. (8)