

Time: 3 Hours

DECEMBER 2012

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. The threshold voltage of p-MOS depletion mode transistor when $V_{SB}=0$ is

- (A) $V_{td} = +0.2V_{DD}$ (B) $V_{td} = -0.7V_{DD}$
 (C) $V_{td} = -0.2V_{DD}$ (D) $V_{td} = +0.7V_{DD}$


b. P-well CMOS fabrication process uses _____ substrate

- (A) P-type Semiconductor (B) N-type Semiconductor
 (C) Pure conductor (D) Pure Insulator

c. The total number of transistors required to realize 4-input CMOS NAND gate is

- (A) 4 (B) 16
 (C) 8 (D) 10

 d. If $V_{in} = +0.5V$ and $V_{in1} = V_{in2} = 2.9V$ then the output voltage (V_{out}) of the n-FET structure shown in figure1 is



- (A) 2.3V (B) 2.9V
 (C) 3.3V (D) 0V

Code: AE74**Subject: VLSI DESIGN**

- e. In n-MOS design rules the minimum separation between poly silicon to diffusion is
- (A) 2λ (B) 1λ
(C) 3λ (D) 4λ
- f. In $5\mu\text{m}$ technology, if a metal length is 30λ , width is 4λ and metal to substrate relative C value is $0.075\lambda C_g$ then its capacitance with respect to substrate is
- (A) $4\lambda C_g$ (B) $2.25\lambda C_g$
(C) $1.125\lambda C_g$ (D) $1\lambda C_g$
- g. _____ are used to join metal 1 to metal 2 layers
- (A) Simple contacts (B) Buried contacts
(C) Vias (D) Butting contacts
- h. In a CMOS inverter with equal length of PMOS and NMOS transistors the rise time and fall time will be equal when
- (A) $W_p=W_n$ (B) $W_p=2.5W_n$
(C) $2.5W_p=W_n$ (D) $W_p=5W_n$
- i. In constant voltage scaling model, the gate capacitance (C_g) is scaled by
- (A) $\frac{1}{\alpha^2}$ (B) $\frac{1}{\beta^2}$
(C) $\frac{\beta}{\alpha^2}$ (D) $\frac{1}{\alpha}$
- j. The propagation delay of cascaded pass transistors is given by
- (A) rct (B) $2.5n\tau$
(C) n^2rct (D) $3.5n\tau$

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

- Q.2** a. Explain with sketches n-well process of CMOS fabrication. (8)
- b. What are the advantages of E-beam masks? Explain the steps involved in making E-beam mask. (8)
- Q.3** a. Derive an expression for Pull-up to Pull-down ratio for an n-MOS inverter driven through one or more pass transistors. (8)
- b. Draw BiCMOS inverter circuit with MOS transistors for base current discharge and explain its operation. (5)

Code: AE74**Subject: VLSI DESIGN**

- c. An inverter uses FETs with $\beta_n=2.1\text{mA/V}^2$ and $\beta_p=1.8\text{mA/V}^2$, the threshold voltages are given as $V_{tn}=0.6\text{V}$, $V_{tp}=-0.7\text{V}$ and a supply voltage of $V_{DD}=5\text{V}$. Calculate midpoint voltage. (3)
- Q.4** a. Discuss λ -based C-MOS design rules for P-well and contacts. (8)
- b. Draw the monochrome stick encoding of (8)
- (i) 2-input CMOS NOR gate
- (ii) Two-way selector with enable
- Q.5** a. Obtain the expression for total delay for N stages of NMOS and CMOS inverters in terms of width factor 'e' and delay factor ' τ '. (8)
- b. Define sheet resistance and standard unit of capacitance $\square C_g$. Find the static and dynamic resistance of a minimum sized CMOS inverter. (8)
- Q.6** a. Write the scaling factors for the following device parameters: (8)
- (i) Saturation current I_{dss} (ii) Channel resistance R_{on}
- (iii) Gate delay (iv) Power speed product (P_T)
- b. Explain the structured design of a parity generator with necessary blocks and write stick diagram of a NMOS one bit parity generator cell. (8)
- Q.7** a. What are the problems associated with the design of VLSI system. How to overcome these problems? (5)
- b. Draw and explain carry-select adder (6-bit) structure. (8)
- c. Write Manchester carry-chain element and explain its operation. (3)
- Q.8** a. Explain with circuit diagram:-
- (i) Six transistor static CMOS memory cell
- (ii) CMOS pseudo-static D-flipflop (5+5)
- b. Explain the optimization of NMOS inverter. (6)
- Q.9** Write short notes on: (4×4=16)
- (i) System partitioning
- (ii) Design testability
- (iii) Testing of combinational logic
- (iv) Boundary Scan Test (BST)