

Time: 3 Hours

DECEMBER 2013

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)


a. The threshold voltage of n-MOS depletion mode transistor when $V_{SB} = 0$ is

- (A) $V_{td} = +0.2V_{DD}$ (B) $V_{td} = -0.7V_{DD}$
 (C) $V_{td} = -0.2V_{DD}$ (D) $V_{td} = +0.7V_{DD}$

b. The total number of transistors required to realize 3-input n-MOS NAND gate is

- (A) 2 (B) 3
 (C) 4 (D) 6

 c. If $V_{tn} = +0.55V$ and $V_{in} = 2.9V$, then the output voltage (V_{out}) of the two n-FET chain shown in **Fig.1** is



- (A) 2.75V (B) 2.9V
 (C) 3.3V (D) 0V

d. In n-MOS design rules the minimum separation between diffusion to diffusion is

- (A) 1λ (B) 2λ
 (C) 3λ (D) 4λ

Code: AE74**Subject: VLSI DESIGN**

- e. In 5 μm technology, the value of standard unit of capacitance is
- (A) 0.1 PF (B) 0.0023 PF
(C) 0.0032 PF (D) 0.01 PF
- f. The condition to work n-MOS transistor in saturation region
- (A) $V_{gs} > V_t$ & $V_{ds} < V_{gs} - V_t$ (B) $V_{gs} < V_t$ & $V_{ds} > V_{gs} - V_t$
(C) $V_{gs} > V_t$ & $V_{ds} > V_{gs} - V_t$ (D) $V_{gs} > V_t$ & $V_{ds} = 0$
- g. The Z_{pu}/Z_{pd} ratio of Pseudo n-MOS inverter driven through similar inverter is
- (A) 3/1 (B) 1/3
(C) 4/1 (D) 1/4
- h. The dynamic power consumption (P_d) of a CMOS is given by
- (A) $m(C_L V_{DD}^2 f)$ (B) $V_{DD}^2 f$
(C) $V_{DD}^2 T$ (D) $V_{DD} f$
- i. The High level noise margin (NM_H) of inverter is given by
- (A) $V_{IH} - V_{IL}$ (B) $V_{OH \min} - V_{IL \min}$
(C) $V_{OH \max} - V_{OL \max}$ (D) $V_{IH \max} - V_{IL \max}$
- j. The objective of Built in Self Test (BIST) is to
- (A) Reduce test pattern generation cost (B) Reduce the value of test data
(C) Reduce test time (D) All of these

**Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.**

- Q.2** a. Explain with sketches P-well process of CMOS fabrication. (8)
- b. What is the importance of Twin-Tub process? Sketch cross-sectional view of Twin-Tub Inverter. (5)
- c. Mention the advantages of CMOS over Bipolar technology. (3)
- Q.3** a. Starting from the fundamentals derive an expression for I_{ds} of n-MOS inverter in saturation region and linear region. (7)
- b. What is Latch-up in CMOS? Sketch latch-up circuit for CMOS n-well process. (5)
- c. For n-MOS enhancement transistor, $\mu_n = 215 \text{ cm}^2/\text{Vsec}$, Oxide capacitance (C_{ox}) = $2.3 \text{ fF}/\mu\text{m}^2$, drain current (I_d) = $100 \mu\text{A}$ and $W/L = 10$. Calculate Transconductance (g_m). (4)

Code: AE74

Subject: VLSI DESIGN

- Q.4** a. Discuss λ -based design rules for wires and contacts. (8)
- b. Draw stick-diagrams for n-MOS inverter, P-well CMOS inverter (8)
- (i) 3-input n-MOS NOR gate
- (ii) 2-input CMOS (P-well) NOR gate
- Q.5** a. Show that the total delay of cascaded N number of CMOS inverters is $3.5 eN\tau$. (7)
- b. Explain how Super buffers can be used to achieve symmetrical transitions, when inverters are used to drive more capacitive loads. (5)
- c. Find the time constant (τ_p) of p-FET for the following parameters:
 $(W/L)_p = 8$, $K_p = 62 \mu A/V^2$, $V_{tp} = -0.85 V$, $V_{DD} = 3.3 V$, the total capacitance is 150 fF. (4)
- Q.6** a. Write the scaling factors for the following device parameters. (8)
- (i) Gate capacitance
- (ii) Saturation current I_{dss}
- (iii) Power speed product (P_T)
- b. With truth table and stick diagram explain Bus arbitration logic for n-line bus. (8)
- Q.7** a. Explain the operation of 4x4 barrel shifter with schematic. What is the limitation of 4x4 crossbar switch? (8)
- b. Design a single bit adder and implement 4-bit ALU functions using adder elements. (8)
- Q.8** a. Explain with circuit diagram n-MOS and CMOS Pseudo-static memory cells. (8)
- b. Discuss briefly the ground rules for successful design. (8)
- Q.9** Write short notes on : (4×4=16)
- (i) Design style and philosophy
- (ii) System partitioning
- (iii) Boundary Scan Test (BST)
- (iv) Built-In-Self-Test (BIST)