

Time: 3 Hours

DECEMBER 2013

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. The characteristic impedance Z_o of transmission line is

- (A) Arithmetic mean of Z_{oc} and Z_{sc}
- (B) Geometric mean of Z_{oc} and Z_{sc}
- (C) Harmonic mean of Z_{sc} and Z_{oc}
- (D) Always equal to Z_{sc} and Z_{oc}

b. A transmission line becomes distortion less if

- (A) $G = 1/R$
- (B) $LG = CR$
- (C) It operate in AF range
- (D) It is properly matched

c. Norton's equivalent circuit consists of

- (A) voltage source in parallel with impedance
- (B) voltage source in series with impedance
- (C) current source in series with impedance
- (D) current source in parallel with impedance

d. The convolution of $f(t)*g(t)$ is

(A) $\int_0^{\infty} f(t)g(t-\tau)d\tau$

(B) $\int_0^t f(t)g(t-\tau)d\tau$

(C) $\int_0^t f(t-\tau)g(t)d\tau$

(D) $\int_0^t f(t)g(t-\tau)d\tau$

- b. For the network shown in Fig.2 determine the voltage across inductor. (8)

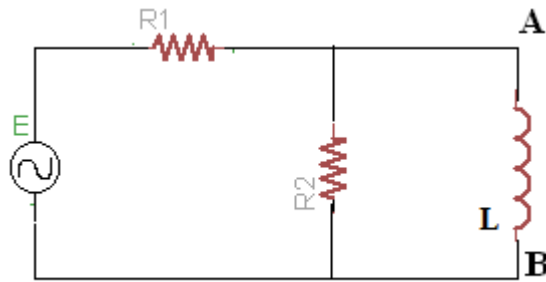


Fig.2

- Q.3 a. Find the Laplace transform of any function that repeats itself. (8)
- b. Write short note on- (8)
- Initial and final value theorem
 - Convolutional Integrals
- Q.4 a. State Reciprocity theorem and check whether the circuit shown in fig.3 obeys reciprocity theorem (8)

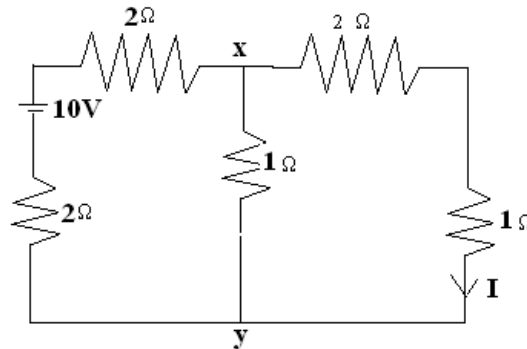


Fig.3

- b. State and prove the substitution theorem. (8)
- Q.5 a. The z-parameter for a 2-port network are $Z_{11}=30\Omega$, $Z_{22} = 40\Omega$, $Z_{21} = 20\Omega$. Find the equivalent T network. (8)
- b. For the given 2 port network calculate ABCD. Parameters and image impedances. (8)

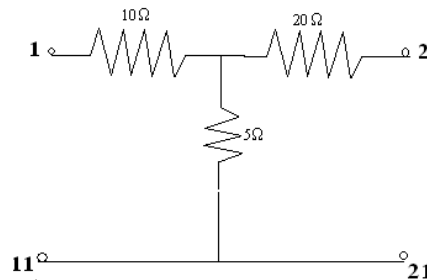


Fig.4

- Q.6 a. Draw and explain a series resonant circuit with the help of phasor diagram. (8)

Code: DE57**Subject: NETWORKS AND TRANSMISSION LINES**

- b. What is quality factor? Explain its effect on bandwidth. Determine Q factor of a coil for the series circuit having resonance frequency $f_r = 7.12$ Hz and $BW = 3.178$ Hz (8)
- Q.7** a. Explain the following
(i) Reflection coefficient (ii) Secondary line constants
(iii) Distortion less Transmission Line (9)
- b. A transmission line connects a transmitter of 1.2 MHz to the aerial located 100m away from it. If Z_0 of the lines be equal to 500Ω . What is the input impedance of this line if antenna end is a) open circuited b) short circuited. (7)
- Q.8** a. What is stub? Explain the different type of stub matching used in transmission lines. (10)
- b. Derive the relation between VSWR ('S') and Reflection coefficient ('K'). (6)
- Q.9** a. A Π section filter network consists of a series arm inductance of 10mH and two shunt arm capacitances of $0.16 \mu\text{F}$ each. Calculate the cut-off frequency and attenuation and phase shift at 12 KHz. What is the value of nominal impedance in the pass band? (8)
- b. Design k- type band pass filter having a design impedance of 500Ω and cut-off frequencies 1 KHz and 10 KHz. (8)