

AMIETE – CS/IT {NEW SCHEME}

Time: 3 Hours

DECEMBER-2014

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions selecting at least TWO from each part, each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. The material used for forming P-type semiconductor is

- (A) Boron (B) Arsenic
(C) Phosphorous (D) Antimony

b. The forward voltage drop across a practical silicon diode is

- (A) 0.3 V (B) 0.7 V
(C) 0.0 V (D) Infinity

c. The average value of the half wave rectified output waveform is given by

- (A) $0.375 V_{PO}$ (B) $0.5 V_{PO}$
(C) $0.318 V_{PO}$ (D) $0.707 V_{PO}$

d. The relationship between α_{DC} and β_{DC} is given by

- (A) $\beta_{DC} = \frac{1 - \alpha_{DC}}{\alpha_{DC}}$ (B) $\alpha_{DC} = \frac{\beta_{DC}}{1 - \beta_{DC}}$
(C) $\beta_{DC} = \frac{\alpha_{DC}}{1 - \alpha_{DC}}$ (D) $\alpha_{DC} = \frac{1 - \beta_{DC}}{\beta_{DC}}$

e. The input and output resistances in a series voltage feedback are

- (A) Input resistance increases and output resistance decreases
(B) Input resistance decreases and output resistance increases
(C) Both input and output resistances decrease
(D) Both input and output resistances increase

f. $(2AF)_{16} = (\quad)_{10}$

- (A) 687
-
- (C) 617

- (B) 667
-
- (D) 597

g. $\bar{x} + xy$

- (A) x
-
- (C)
- $\bar{x} + y$

- (B)
- $x + y$
-
- (D)
- $x + \bar{y}$

h. In a K-map, looping a quad of adjacent 1s eliminates

- (A) One variable
-
- (C) Three variables

- (B) Two variables
-
- (D) Four variables

i. 1's complement of 101101 is

- (A) 010011
-
- (C) 100010

- (B) 010010
-
- (D) 011100

j. In a Mod-8 counter, the output from the last flip-flop will have a frequency of _____ of the input frequency

- (A) Half
-
- (C) One eighth

- (B) One fourth
-
- (D) One sixteenth

PART (A)**Answer at least TWO questions. Each question carries 16 marks.****Q.2** a. Explain the formation of barrier voltage and depletion region in a PN junction. **(8)**b. Explain the purpose of a dc load line. Write the equation for drawing a dc load line for a series circuit consisting of a supply voltage (E), a resistor (R_1) and a diode (D_1). **(8)****Q.3** a. Draw the circuit of two diode full wave rectifier and explain the working along with the waveforms. **(8)**b. Draw the positive and negative voltage clamping circuits. Explain its working along with the waveforms. **(8)****Q.4** a. Explain the operation of PNP transistor with neat diagrams. Why they are termed as 'bipolar' junction transistors? **(8)**

Code: AC103/AT103 Subject: ANALOG AND DIGITAL ELECTRONICS

- b. The base bias circuit shown in **Fig.1** has $R_B = 470k\Omega$, $R_C = 2.2k\Omega$ and $V_{CC} = 18V$, and the transistor has $h_{FE} = 100$. Determine I_B , I_C and V_{CE} (8)

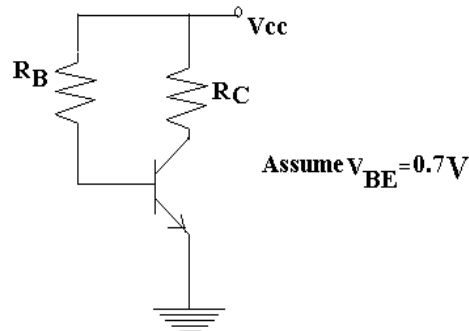


Fig.1

- Q.5** a. Draw the circuit of single stage CE amplifier and explain the function of bypass capacitor and coupling capacitors. (8)
- b. Explain the working of BJT phase shift oscillator with a neat circuit diagram. (8)

PART (B)

Answer at least TWO questions. Each question carries 16 marks.

- Q.6** a. Explain the parallel and serial transmission of information in digital systems. (8)
- b. Explain the parity method for error detection. (8)
- Q.7** a. Write DeMorgan's Theorems and simplify $z = \overline{(\overline{A} + C)} \cdot (\overline{B + D})$. (8)
- b. Explain Exclusive – OR and Exclusive – NOR gates with neat diagrams. (8)
- Q.8** a. Explain BCD adder with an example. (8)
- b. What is a Demultiplexer? Explain with a diagram, the working of a 1 line to 8 line Demultiplexer. (8)
- Q.9** a. Explain the working of a clocked J K flip flop with neat diagram and waveforms. (8)
- b. Draw the diagram of a 4-bit Asynchronous Counter and explain its working along with the waveforms. (8)