

AMIETE – ET {NEW SCHEME}

Time: 3 Hours

DECEMBER 2014

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

- a. An n-type semiconductor material
- (A) is intrinsic
 (B) has trivalent impurity atoms added
 (C) has pentavalent impurity atoms added
 (D) requires no doping
- b. Reverse breakdown is a condition in which a diode
- (A) is subjected to a large reverse voltage
 (B) is reverse-biased and there is a small leakage current
 (C) has no current flowing at all
 (D) is heated up by large amounts of current in the forward direction
- c. What best describes the circuit?

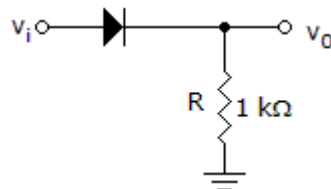


Fig.1

- (A) Full-wave rectifier (B) Half-wave rectifier
 (C) Clipper (D) Clamper
- d. What is the most frequently encountered transistor configuration?
- (A) Common-base (B) Common-collector
 (C) Common-emitter (D) Emitter-collector

- e. Determine the value of α when $\beta = 100$.
- (A) 1.01 (B) 101
(C) 0.99 (D) Cannot be solved
- f. For a JFET, the value of V_{DS} at which I_D becomes essentially constant is the
- (A) Pinch-off voltage (B) Cutoff voltage
(C) Breakdown voltage (D) Ohmic voltage
- g. Determine the peak value of the output waveform.

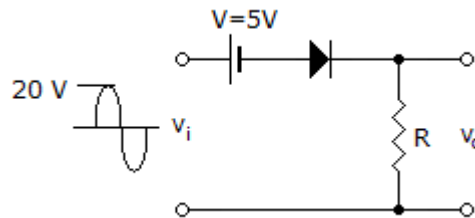


Fig.2

- (A) 25 V (B) 15 V
(C) -25 V (D) -15 V
- h. In a monolithic-type IC
- (A) each transistor is diffused into a separate isolation region
(B) all components are fabricated into a single crystal of silicon
(C) resistors and capacitors of any value may be made
(D) all isolation problems are eliminated
- i. Which type of power amplifier is biased for operation at less than 180° of the cycle?
- (A) Class A (B) Class B or AB
(C) Class C (D) Class D
- j. Identify the type of oscillator whose oscillation frequency is $1/2\pi RC\sqrt{6}$
- (A) Phase-shift (B) Wien bridge
(C) Colpitts (D) Hartley

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

- Q.2 a. State and explain the Reciprocity Theorem and Thevenins Theorem. (6)

- b. In the circuit shown below, determine the value of V_x . (6)

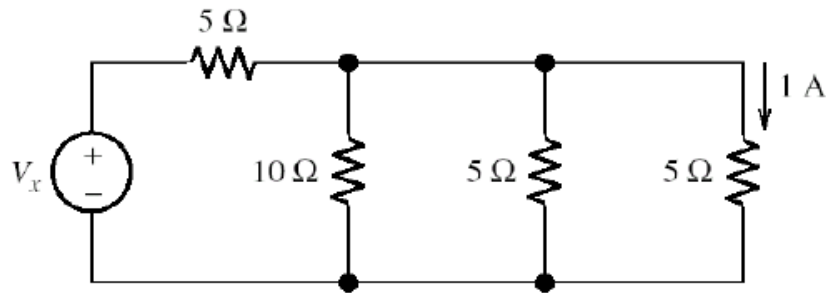


Fig.3

- c. Define the term: electrical current, direct current and alternating current. (4)

Q.3 a. Explain the different biasing of P-N junction diode. Also draw VI characteristics. (10)

- b. For the zener diode network shown in figure below determine V_L , V_R , I_Z , and I . (6)

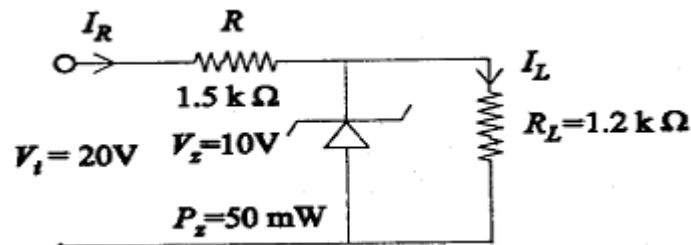


Fig.4

Q.4 a. A transistor used in CE arrangement has the following set of h parameters when the d.c. operating point is $V_{CE} = 10$ volts and $I_C = 1$ mA :

$$h_{ie} = 2000 \Omega; h_{oe} = 10^{-4} \text{ mho}; h_{re} = 10^{-3}; h_{fe} = 50$$

Considering the a.c. load seen by the transistor is $r_L = 600 \Omega$. Determine approximate values of the following using reasonable approximations:

- (i) input impedance (ii) current gain and (iii) voltage gain (8)
- b. Explain the working of BJT as a switch.. (8)

Q.5 a. Draw and explain in brief the output characteristics (V_{DS} Vs I_D) and transfer characteristics of n-channel JFET. Also show that $\mu = r_d \times g_m$. (6)

- b. Assuming Si transistor with $\beta = 100$ Calculate V_{CE} , I_C for the following circuit (4)

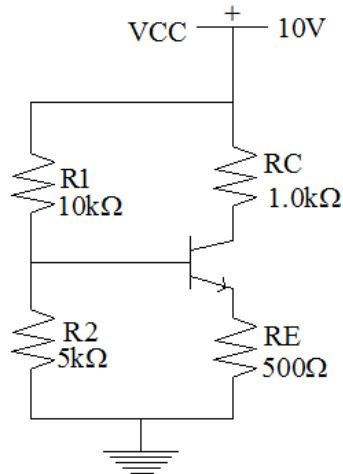


Fig.5

- c. Define the following: Drain to source saturation current of JFET, Pinch off voltage of JFET, Voltage controlled resistance of JFET. (6)
- Q.6** a. Explain the working of Wein Bridge Oscillator. (8)
- b. What are the advantages and disadvantages of negative feedback in amplifier? (8)
- Q.7** a. Draw and explain the Transformer coupled Class A power amplifier. List the advantages and disadvantages also. (8)
- b. With the help of a neat diagram explain the functioning of Class-C power amplifier. (8)
- Q.8** a. A certain BJT transistor has $r_{\pi} = 2 \text{ k}\Omega$ and $\beta = 50$ at 1 MHz and $\beta = 2.5$ at 20MHz. Determine the values of f_T , f_B and c_{π} . (8)
- b. With neat circuit diagram and frequency response, explain two stage RC coupled amplifier. What are its advantages and applications? (8)
- Q.9** a. What do you mean by Integrated Circuits? What are the advantages of ICs as compared to standard printed circuits? (8)
- b. Explain in brief, the various steps involved in fabrication of ICs. (8)