

**AMIETE – ET {NEW SCHEME}**

Time: 3 Hours

**DECEMBER 2014**

Max. Marks: 100

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions selecting at least TWO questions from each part, each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

a. The bandwidth of an ideal Op-Amp is

- |           |              |
|-----------|--------------|
| (A) Zero  | (B) Infinity |
| (C) Small | (D) Large    |

b. The typical value of CMRR for 741C Op-Amp is

- |           |           |
|-----------|-----------|
| (A) 20 dB | (B) 40 dB |
| (C) 60 dB | (D) 90 dB |

c. Operational Transconductance Amplifiers (OTAs) are used in

- |                      |                            |
|----------------------|----------------------------|
| (A) Integrators      | (B) Differentiators        |
| (C) Current switches | (D) Logarithmic Amplifiers |

d. The time period "T" for which the output of Monostable Multivibrator using op-amp goes low is given by

- |              |              |
|--------------|--------------|
| (A) $0.69RC$ | (B) $2.01RC$ |
| (C) $1.69RC$ | (D) $1.09RC$ |

e. The fastest and most expensive Analog to Digital Conversion Technique is

- |                                   |                              |
|-----------------------------------|------------------------------|
| (A) Counter Type                  | (B) Parallel Comparator type |
| (C) Successive Approximation Type | (D) Dual Slope Type          |

f. The code that is used for transfer of alphanumeric information between a computer and external device is

- |                |                     |
|----------------|---------------------|
| (A) ASCII Code | (B) BCD Code        |
| (C) Gray Code  | (D) Excess – 3 Code |

g. The output expression for Y in the circuit shown below in Fig.1 is

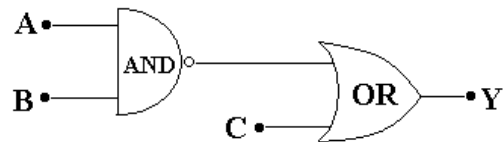


Fig.1

- (A)  $A \cdot B + C$  (B)  $\bar{A} + \bar{B} + C$   
 (C)  $\bar{A} + B + \bar{C}$  (D)  $\bar{A} + \bar{B} + \bar{C}$
- h. The simplified expression for  $x = (\bar{A} + B)(A + B + D)\bar{D}$  is
- (A)  $x = \bar{B}D$  (B)  $x = B\bar{D}$   
 (C)  $x = (\bar{A} + \bar{D})$  (D)  $x = (A + D)$
- i.  $(592)_{16} - (3A5)_{16} = (\quad)_{16}$
- (A) 1ED (B) 1A7  
 (C) 1B7 (D) 1C3
- j. The output frequency of a decade counter which is clocked from a 50 KHz signal is
- (A) 25 KHz (B) 12.5 KHz  
 (C) 6.25 KHz (D) 5 KHz

---

**PART (A)**

Answer at least TWO Questions. Each question carries 16 marks.

---

- Q.2** a. Briefly define monolithic, thin film, thick film and hybrid integrated circuits. (8)
- b. Draw the equivalent circuit, block schematic of an Op-Amp, and list the characteristics of an ideal Op-Amp. (8)
- Q.3** a. Explain Op-Amp circuit bandwidth and slew rate. (8)
- b. Draw the circuit of inverting summing amplifier using Op-Amp and derive the expression for its output. (8)
- Q.4** a. Explain the working of Sample and Hold circuit using Op-Amp with the help of waveforms. (8)
- b. Explain the working of Schmitt Trigger circuit using Op-Amp. (8)
- Q.5** a. Explain the working of Astable Multivibrator using Op-Amp. (8)
- b. Explain the working of Parallel comparator type A/D Converter. (8)

**PART (B)**


Answer at least TWO Questions. Each question carries 16 marks.

**Q.6** a. Describe the relative advantages of parallel and serial transmission of binary data. (6)

b. Perform the following conversions;

- |                                   |                                    |
|-----------------------------------|------------------------------------|
| (i) $(100101)_2 = ( \quad )_{10}$ | (ii) $(372)_8 = ( \quad )_{10}$    |
| (iii) $(5431)_8 = ( \quad )_2$    | (iv) $(2AF)_{16} = ( \quad )_{10}$ |
| (v) $(3A6)_{16} = ( \quad )_2$    | (10)                               |

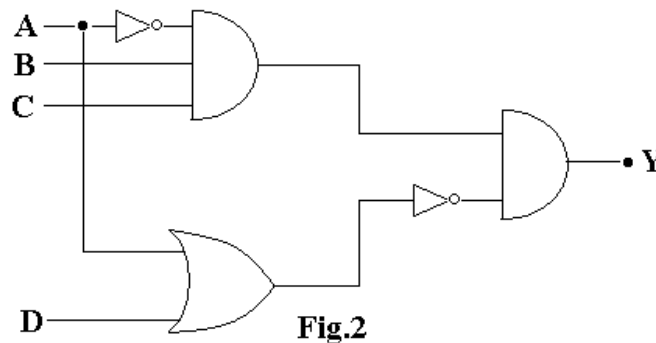**Q.7** a. Determine the output expression for the circuit shown in Fig.2 and find the output, if A=0, B=1, C=1 and D=1. (8)



b. Simplify the expression  $x = \bar{A}\bar{B}\bar{C} + \bar{A}BC + ABC + A\bar{B}\bar{C} + A\bar{B}C$  using Karnaugh map. (8)

**Q.8** a. Draw the block diagram of a 5-bit parallel Adder circuit using full-adders and explain. (8)

b. What is a Multiplexer? Explain with a diagram the working of a 4-input multiplexer. (8)

**Q.9** a. Explain the working of a clocked JK flip flop with neat diagram and waveforms. (8)

b. Draw the diagram of a 4-bit Ring-Counter and explain its working with waveforms. (8)