

AMIETE – ET {NEW SCHEME}

Time: 3 Hours

DECEMBER 2014

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. The equivalent resistance for the circuit shown in Fig.1 across the terminal 'A' and 'B' is

- (A) 15Ω
- (B) 3Ω
- (C) $3/5\Omega$
- (D) $5/3\Omega$

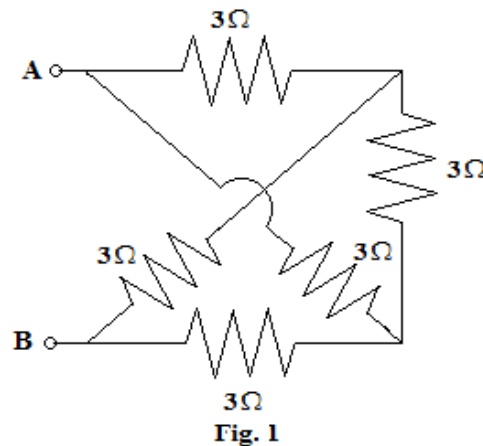


Fig. 1

b. The equivalent voltage source for the circuit shown in Fig.2 across terminal 'x' and 'y' can be represented as _____ resistance.

- (A) 20V in series with 10Ω
- (B) 20V in series with 15Ω
- (C) 30V in series with 10Ω
- (D) 30V in series with 15Ω

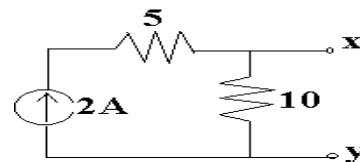


Fig.2

c. A capacitor with zero initial conditions at $t = 0^+$ act as a

- (A) short circuit
- (B) open circuit
- (C) current source
- (D) voltage source

d. A unit ramp function when integrated yields

- (A) unit parabolic function
- (B) unit ramp function
- (C) unit impulse function
- (D) unit step function

e. The Laplace transform of $e^{-at} f(t)$ is

- (A) $-\frac{d}{ds} F(s)$ (B) $F(s + a)$
 (C) $F(s)e^{-at}$ (D) $\frac{F(s)}{s + a}$

f. The maximum power transfer through the load as shown in Fig.3

- (A) 25W
 (B) 30.6W
 (C) 62.5W
 (D) 110W

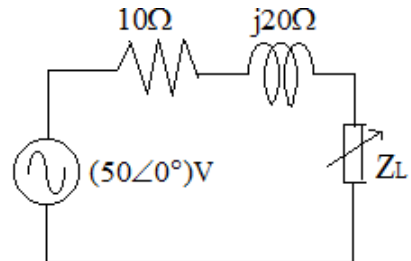


Fig. 3

g. The condition for reciprocity in ABCD-parameter is

- (A) $AD - BC = 1$ (B) $AD = BC$
 (C) $A = D$ (D) $AC - BD = 1$

h. For a prototype high pass filter, the series element is

- (A) Resistive
 (B) Inductive
 (C) Capacitive
 (D) Combination of inductance and capacitance

i. The adjoining figure of synthesized LC circuit in Fig.4 represents.

- (A) Cauer Form I
 (B) Foster Form I
 (C) Foster Form II
 (D) Cauer Form II

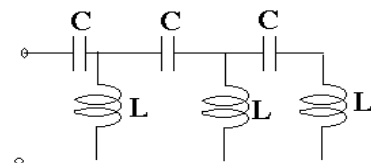


Fig.4

j. $H(s) = \frac{V(s)}{I(s)} = \frac{2(s+3)}{(s+2)^3}$ when $i(t)$ is a unit step function. The value of $v(t)$ in the steady state is given by

- (A) 3/2 (B) 3/4
 (C) 1 (D) 0

**Answer any FIVE Questions out of EIGHT Questions.
 Each question carries 16 marks.**

Q.2 a. Determine V_x in the circuit shown in Fig.5

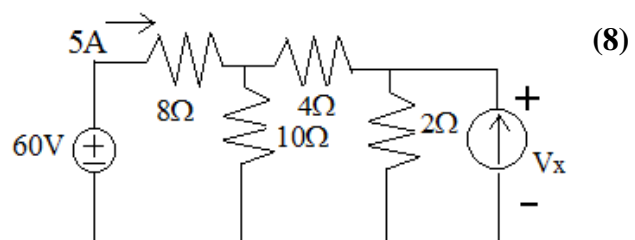


Fig. 5

(8)

- b. For the circuit shown in Fig.6, obtain the value of current through 2Ω resistor. (8)

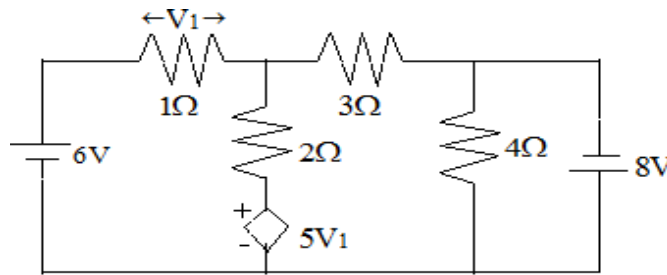


Fig.6

- Q.3 a. In the network shown in Fig.7, if the switch k is opened at $t = 0$, then find the following quantities at $t = 0^+$ (i) v_1 & v_2 (ii) $\frac{dv_1}{dt}$ & $\frac{dv_2}{dt}$. (8)

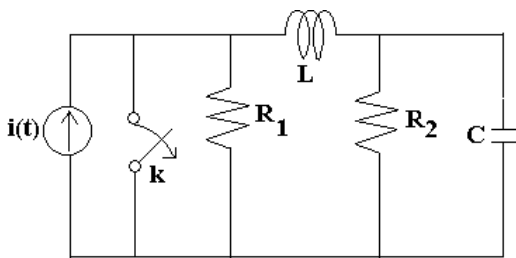


Fig.7

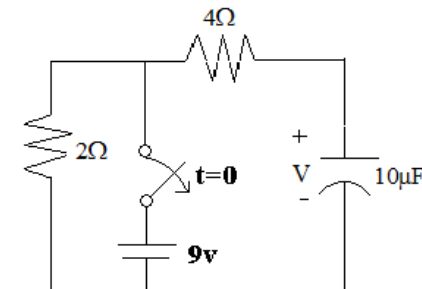


Fig.8

- b. For the circuit shown in Fig.8, find the voltage labelled v at $t = 200 \mu \text{ sec}$. (8)

- Q.4 a. Obtain the Laplace transform of
 (i) The delayed step, function $k[u(t-a)]$. (4)
 (ii) The ramp function $k t u(t)$. (4)
- b. Consider the R-L circuit with $R = 4\Omega$ and $L = 1\text{H}$ excited by a 48V dc source as shown in Fig.9. Assume the initial current through the inductor is 3A. Using Laplace transform method, determine the current $i(t)$; at $t \geq 0$. Also draw the s-Domain representation of the circuit. (8)

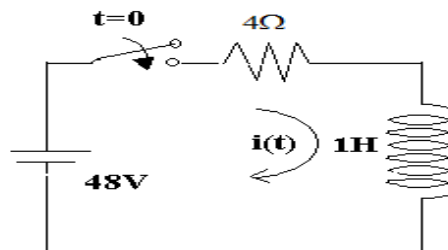


Fig.9

- Q.5 a. Obtain the Thevenin's equivalent circuit across the terminal A & B of ckt shown in Fig.10. (8)

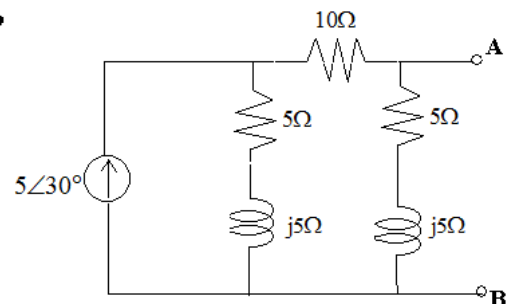


Fig.10

- b. Derive the condition for maximum power transfer to take place at a load impedance $Z_L = R_L + jX_L$, when the source is an ac source having an internal impedance of $Z_{in} = R + jX$. (8)

- Q.6 a. Find the transfer impedance function

$Z_{21}(s) = \frac{V_2(s)}{I_1(s)}$ of the network shown in Fig.11

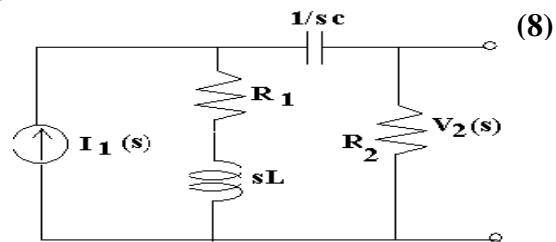


Fig.11

- b. Check whether the given polynomial $P(s)$ is Hurwitz or not.
 $P(s) = s^4 + s^3 + 2s^2 + 4s + 1$ (8)

- Q.7 a. Obtain the condition for reciprocity and symmetry in terms of h-parameters. (8)

- b. Calculate the Z – Parameters of the network shown in Fig.12. Determine whether the network is symmetrical or not? (8)

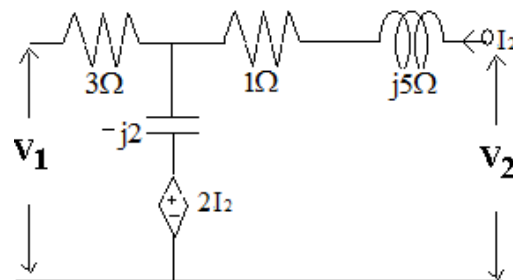


Fig.12

- Q.8 An impedance function given by $Z(s) = \frac{s(s+2)(s+5)}{(s+1)(s+4)}$ find the R-L representation of (16)

- (i) FOSTER I and II forms.
 (ii) CAUER I and II forms.

- Q.9 a. Find the driving point impedance of the network shown in Fig.13. Find the poles and zeros of the network and locate them in s-plane. (8)

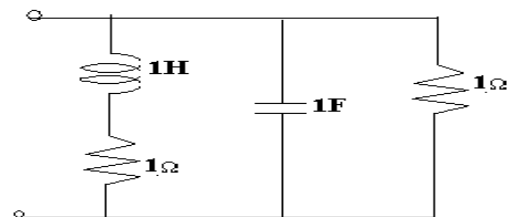


Fig.13

- b. If a T-section of a constant k- low pass filter has series inductance 85 mH and shunt capacitance of $0.025\mu\text{F}$, calculate its cut off frequency and the nominal design impedance R_o . Design an equivalent π -section too. (8)