

Time: 3 Hours

DECEMBER 2014

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions, selecting at least TWO questions from each part, each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. A logic circuit that provides a HIGH output if one input or the other input, but not both, is HIGH, is a(n):

- | | |
|-----------------|---------------|
| (A) Ex-NOR gate | (B) OR Gate |
| (C) Ex-OR Gate | (D) NAND Gate |

b. Determine the values of A, B, C, and D that make the sum term $\bar{A} + B + \bar{C} + D$ equal to zero.

- | | |
|--------------------------------|--------------------------------|
| (A) A = 1, B = 0, C = 0, D = 0 | (B) A = 1, B = 0, C = 1, D = 0 |
| (C) A = 0, B = 1, C = 0, D = 0 | (D) A = 1, B = 0, C = 1, D = 1 |

c. The output of an exclusive-NOR gate is 1. Which input combination is correct?

- | | |
|------------------|-------------------|
| (A) A = 1, B = 0 | (B) A = 0, B = 1 |
| (C) A = 0, B = 0 | (D) none of these |

d. How is a J-K flip-flop made to toggle?

- | | |
|------------------|------------------|
| (A) J = 0, K = 0 | (B) J = 1, K = 0 |
| (C) J = 0, K = 1 | (D) J = 1, K = 1 |

e. A MOD-16 ripple counter is holding the count 1001_2 . What will the count be after 31 clock pulses?

- | | |
|--------------|--------------|
| (A) 1000_2 | (B) 1010_2 |
| (C) 1011_2 | (D) 1101_2 |

- f. Refer to Fig. 1, if the value of R_1 decreases, the voltage gain will _____ and the input impedance will _____.

 


Fig.1

- (A) increase, increase respectively (B) increase, decrease respectively
 (C) decrease, decrease respectively (D) decrease, increase respectively
- g. What is the slew rate of an op-amp if the output voltages change from 2 V to 3 V in 0.2 ms?
- (A) 5 V/ms (B) 3 V/ms
 (C) 2 V/ms (D) 1 V/ms
- h. The _____ is defined as the time the output is active divided by the total period of the output signal.
- (A) on time (B) off time
 (C) duty cycle (D) active ratio
- i. Which mode of operation is being used when a 555 timer chip has two external resistors and an external capacitor?
- (A) monostable (B) pulse stretching
 (C) Schmitt triggering (D) astable
- j. The resolution of a 0–5 V, 6-bit digital-to-analog converter (DAC) is
- (A) 63% (B) 64%
 (C) 1.56% (D) 15.6%

PART (A)

Answer At least TWO questions. Each question carries 16 marks.

Q.2 a. Give the classification of different IC technologies. (4)

b. For a differential amplifier using ideal op-amp(Shown in Fig. 2)

(i) Find the output voltage v_o

(ii) Show that the output corresponding to common-mode voltage

$$v_{CM} = \frac{(v_1 - v_2)}{2} \text{ is zero if } \frac{R'}{R} = \frac{R_2}{R_1}$$

(iii) Find CMRR of the amplifier if $\frac{R'}{R} \neq \frac{R_2}{R_1}$ (12)

 


Fig.2

Q.3 a. Draw and explain the circuit diagram of the voltage to current converter (Transconductance Amplifier). (8)

b. Explain the following non-ideal dc characteristics of real op-amp:

(i) Input bias current

(ii) Input offset current

(iii) Input offset voltage

(iv) Thermal drift (8)

Q.4 a. Design a circuit diagram of non-inverting integrator, also derive it's input output relation. (8)

b. Design a circuit diagram of zero crossing detector using op-amp as comparator. (8)

- Q.5** a. Describe the pin diagram of 555 timer IC and give examples of its application. (4)
- b. Design a circuit diagram of 3 bit R-2R Ladder DAC and also derive it's input output relation. (6)
- c. Explain the working of Series Op-Amp voltage regulator with its circuit diagram. (6)

PART (B)

Answer At least TWO questions. Each question carries 16 marks.

- Q.6** a. What are alphanumeric codes? Give suitable example and numbers of bits in the code? (3)
- b. What is the advantage and disadvantage of encoding a decimal number in BCD as compared with straight binary? (3)
- c. Perform the following conversions:
 (i) $(1011.0011)_2 = (\underline{\quad})_{10}$ (ii) $(204.125)_{10} = (\underline{\quad})_{16}$
 (iii) $(25.25)_{10} = (\underline{\quad})_2$ (iv) $(B4.C9)_{16} = (\underline{\quad})_{10}$
 (v) $(5431.4)_8 = (\underline{\quad})_{16}$ (5×2)
- Q.7** a. What are the advantages of digital systems over analog systems? (4)
- b. Minimize the given expression by using Boolean algebra,
 $Y = B(1 + C)(B + \overline{BC})(B + D)$ (4)
- c. Design a combinational logic circuit with three input variables(say A, B, C) that produce a logic 1 output (say Y)when more than one input variables are logic 1.Draw the truth table and minimize expression using k-map. (8)
- Q.8** a. What is Multiplexer? Draw the logic diagram and functional table for the 4×1 MUX. (8)
- b. Design a Full Adder Circuit using two Half adder circuits and other basic gate? (8)
- Q.9** a. Compare between Synchronous sequential circuits and asynchronous sequential circuits? (4)
- b. Draw the circuit diagram of J-K flip-flop using NAND gate and draw the truth table and excitation table of J-K flip-flop. (6)
- c. Explain and draw 4 bit Serial In / Parallel Out Shift Register, show the status of register at various clock pulses if data 10111 is fed into it. (6)