

Time: 3 Hours

**DECEMBER 2014**

Max. Marks: 100

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE:** There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

a. If the current enters the dotted terminal of the coil, the reference potential of the voltage induced in the other coil is \_\_\_\_\_.

- (A) positive (B) negative  
(C) additive (D) none of these

b. In terms of ABCD parameters, the image parameter  $Z_{12}$  of a two port network is

- (A)  $\sqrt{BD/AC}$  (B)  $\sqrt{AB/CD}$   
(C)  $AB/CD$  (D)  $BD/AC$

c.  $h_{21}$ , in terms of Z parameters can be expressed as

- (A)  $\Delta Z/Z_{22}$  (B)  $\Delta Z/Z_{12}$   
(C)  $Z_{12}/\Delta Z$  (D)  $-Z_{21}/Z_{22}$

d.  $1/s + a$  is Laplace transform of

- (A)  $e^{at}$  (B)  $e^{-at}$   
(C)  $1/e^{-at}$  (D) none of these

e. Reciprocity theorem applies to only one of the following networks

- (A) Linear as well as non linear (B) Linear bilateral  
(C) Linear active (D) all type of networks

f. Higher the Q of a series circuit,

- (A) sharper its resonance (B) greater its bandwidth  
(C) broader its resonance curve (D) narrower its pass band

g. Stub matching is more effective if

- (A) O.C. stub is used (B) done as near source as possible  
(C) done as near load as possible (D) done at any voltage maxima on line


- h. In open circuit line, voltage maxima is at  
 (A) load  
 (B) source  
 (C) any point on the line  
 (D) midpoint between source and load
- i. Neper is equal to  
 (A) 115.1 x attenuation in dB  
 (B) 11.51 x attenuation in dB  
 (C) 1.151 x attenuation in dB  
 (D) 0.1151 x attenuation in dB
- j. An m-derived filter has  
 (A) High attenuation in the entire attenuation band  
 (B) low attenuation in the entire attenuation band  
 (C) High attenuation in entire passband  
 (D) High attenuation at  $f = f_{\infty}$

---

**Answer any FIVE Questions out of EIGHT Questions.**  
**Each question carries 16 marks.**

---

- Q.2** a. Illustrate the condition of reciprocity and symmetry in Z-parameter representation. (8)
- b. Explain with the help of diagram the phenomenon of standing waves in open and short circuit lines. (8)
- Q.3** a. At  $t = 0$ , a pulse of width  $a$  is applied to the RL network of Fig 3. Determine the expression for the current  $i(t)$  using Laplace transformation. (8)

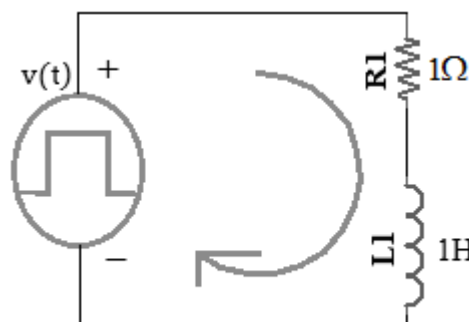

**Fig. 3**

- b. Find the Laplace transform of (8)
- (i) Unit Step Function
- (ii) Exponential Function

- Q.4** a. State Thevenin theorem and find the current in the resistance of 5ohm as shown in circuit in Fig.4. (8)

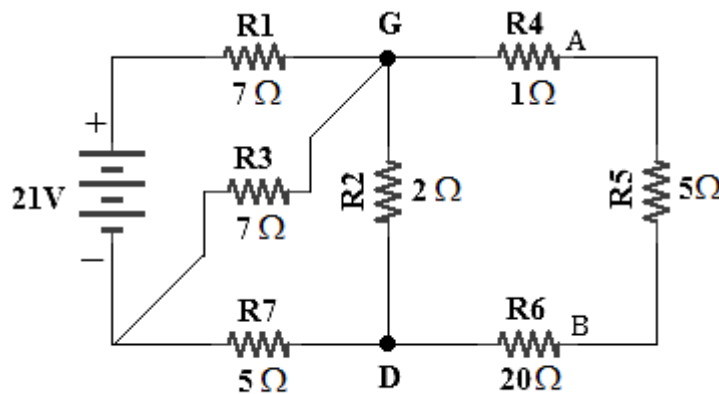


Fig. 4

- b. State superposition theorem and determine the current through each resistor.(8)

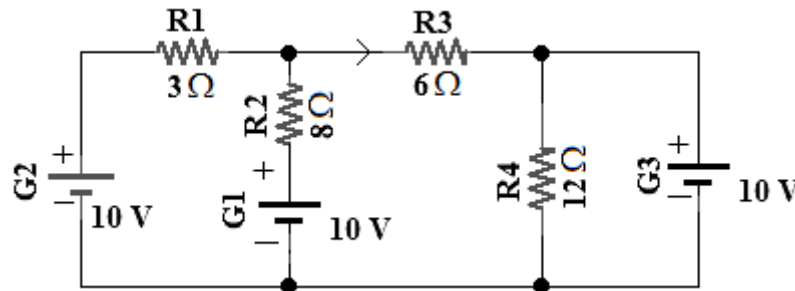


Fig.5

- Q.5** a. Explain the effect of resistance on the frequency response for RLC circuit. (5)  
 b. Explain how impedance of a parallel resonant circuit varies with frequency?(5)  
 c. Show that the frequency of resonance in a parallel RLC circuit differ from that of a series RLC circuit. (6)

- Q.6** a. Derive an expression of characteristics impedance  $Z_0$  of symmetrical T section. (8)  
 b. Derive an expression for the open and short circuit impedance of a symmetrical T network in terms of arm impedance. (8)

- Q.7** a. The Z parameters of a two port network are  $Z_{11} = 10$  ohms,  $Z_{22} = 20$  ohms,  $Z_{12} = Z_{21} = 5$  ohms.  
 (i) Find the ABCD parameters  
 (ii) Also find the equivalent T-network (8)  
 b. What is Reflection Coefficient? Derive the relation between VSWR and Reflection Coefficient. (8)

- Q.8** a. Draw the balance and unbalance circuit for T and  $\pi$  network. (4)
- b. Design a 'T' type symmetrical attenuator which offers 40dB attenuation with a load of  $400\Omega$ . (6)
- c. Design a constant K low pass filter having  $f_c = 2\text{kHz}$  and design impedance  $R_o = 600\Omega$ . Obtain the value of attenuation at 4 kHz (6)
- Q.9** Write Short note on the following: (8×2)
- (i) Losses in transmission Line
- (ii) Smith Chart and its Application