

DiplETE - ET/CS {NEW SCHEME}

Time: 3 Hours

DECEMBER 2014

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. The ASCII code is

- (A) a two bit code (B) a four bit code
(C) a seven bit code (D) an eight bit code

b. A gate in which all inputs must be low to get a high output is called _____ gate.

- (A) AND (B) NOR
(C) NOT (D) NAND

c. Result of binary multiplication 10110 and 101 is

- (A) 1110110 (B) 1011110
(C) 1110010 (D) 1101110

d. A half adder has

- (A) one input and one output (B) two input and one output
(C) two input and two output (D) one input and two output

e. Which of the following is a combinational circuit?

- (A) register (B) decoder
(C) flip flop (D) counter

f. In JK flip flop if we input K with the inverted form of what we input J, the resultant flip flop is

- (A) SR flip flop (B) D flip flop
(C) T flip flop (D) JK flip flop itself

- g. The number of flip flops required to reduce frequency by 32 is _____.
- (A) 3 (B) 4
(C) 5 (D) 6
- h. A reliable method for eliminating the decoding glitches is _____.
- (A) strobing (B) cascading
(C) parallel loading (D) serial loading
- i. Johnson counter is also known as
- (A) up counter (B) down counter
(C) decade counter (D) twisted ring counter
- j. In which of the following memory, stored data can be erased by exposing it to ultraviolet rays for a particular time period.
- (A) PROM (B) EPROM
(C) EEPROM (D) RAM

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

- Q.2** a. Perform the following conversions: (8)
- (i) $(3742)_8 = (?)_{10}$
(ii) $(2A64)_{16} = (?)_2$
(iii) $(2047)_{10} = (?)_{16}$
(iv) $(1101011)_2 = (?)_{10}$
- b. With the help of neat sketch explain serial and parallel transmission. (5)
- c. Draw functional diagram of digital computer. (3)
- Q.3** a. Draw the symbol of AND and NOR gate and explain their working using truth table (6)
- b. Simplify the following expression using K map and implement it using logic gate. (6)
- $$Y = \overline{ABC} + \overline{A}BC + ABC + \overline{A}\overline{B}C + \overline{A}BC$$
- c. Draw the symbols and truth tables of XOR gate and XNOR gates. (4)

- Q.4** a. Draw logic circuit of 4-bit BCD adder and explain its working. (8)
- b. Perform the following operation: (2+2+2+2)
- (i) $(45)_{10} - (23)_{10}$ Using 2's complement method.
- (ii) $(10111)_2 - (100)_2$
- (iii) $(385)_{10} + (118)_{10}$ Using BCD addition.
- (iv) Represent decimal value -12 as an 8-bit signed binary value.
- Q.5** a. Draw the circuit of 4 bit serial in parallel out shift register and explain its working. (8)
- b. Draw logic circuit of 4 bit ring counter and explain its working with the help of truth table, waveforms and state diagram. (8)
- Q.6** a. What is encoder? Explain working of octal to binary encoder. (8)
- b. What is de-multiplexer? Draw logic diagram of 1:8 de-multiplexer and explain its working. (8)
- Q.7** a. Draw the logic diagram NOR gate latch and its working using truth table. (8)
- b. What is frequency division? How can flip flop be used for this application? Also list other applications of flip flop. (2+4+2)
- Q.8** a. Explain working principle of decade counter with suitable logic diagram. (8)
- b. What are synchronous counters? Design a Mod-6 synchronous counter using J-K Flip-Flops. (8)
- Q.9** a. What is RAM? Distinguish between SRAM and DRAM. (2+4)
- b. How many address bits are required to access a 32 K memory? (2)
- c. What is ROM? Draw 16×8 ROM architecture and explain its working. (8)