

**DipIETE – ET/CS**

Time: 3 Hours

**DECEMBER 2014**

Max. Marks: 100

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions, selecting at least TWO questions from each part. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

- a. Barrier potential in a P-N junction is caused by
- (A) Thermally generated electrons and holes  
 (B) Diffusion of majority carriers across the junction  
 (C) Migration of minority carriers across the junction  
 (D) Flow of drift current
- b. Whenever a conductor cuts magnetic flux, an emf is induced in that conductor; the above statement is based on
- (A) Faraday's law (B) Joule's law  
 (C) Weber and Ewing's theory (D) Coulomb's law
- c. One of the common applications of Zener diode is a \_\_\_\_\_.
- (A) rectifier (B) simple voltage reference source  
 (C) clipper (D) emitter follower
- d. Resistance of a wire is  $r$  ohms. The wire is stretched to double its length then its resistance in ohms is
- (A)  $r/2$  (B)  $4r$   
 (C)  $2r$  (D)  $r/4$
- e. In case of DC series motor after saturation of magnetic core the relation between torque and armature current is
- (A)  $T \propto I_a$  (B)  $T \propto I_a^2$   
 (C)  $T \propto \phi I_a$  (D)  $T$  is constant
- f. The CE amplifier circuits are preferred over CB amplifier circuits because they have
- (A) lower amplification factor  
 (B) higher amplification factor  
 (C) high input resistance and low output resistance  
 (D) None of these

- g. The potential divider biasing is used in amplifiers to
- (A) limit the input ac signal going to the base
  - (B) reduce dc base current
  - (C) reduce the cost of the circuit by limiting the number of resistors
  - (D) make the operating point almost independent of  $\beta$
- h. The difference between the synchronous speed & the actual speed of an induction motor is known as
- (A) Regulation
  - (B) Back lash
  - (C) Slip
  - (D) Lag
- i. For BJT to work as an amplifier, the Q-point should be in \_\_\_\_\_ region.
- (A) saturation
  - (B) cut-off
  - (C) active
  - (D) none of these
- j. A phase shift oscillator consists of three \_\_\_\_\_
- (A) RC circuits
  - (B) RL circuits
  - (C) LC circuits
  - (D) RLC circuits

---

**PART A**

**Answer at least TWO questions. Each question carries 16 marks.**

- 
- Q.2** a. Derive an expression for the current flowing at any instant during the discharge of a capacitor C across a resistor R. (8)
- b. The coil of a moving coil instrument is wound with 50 turns of wire. The flux density in the gap is  $0.06 \text{ Wb/m}^2$  and the effective length of the coil side in the gap is 4cm. find the force acting on each side of the coil when the current is 40mA. (8)
- Q.3** a. State and explain Thevenin's Theorem with suitable example. (8)
- b. Three inductive coils each with a resistance of 15 ohms and an inductance of 0.03 H are connected (i) in star and (ii) in delta, to 3-phase, 400V, 50Hz supply. Calculate for each of the above case (i) phase current and line current and (ii) total power absorbed. (8)
- Q.4** a. Draw the connection diagram of shunt and series DC motors and explain. (8)
- b. A 200 V dc shunt motor is taking a current of 70 A and runs at 500 rpm. The motor resistances are  $R_a = 0.2\Omega$  and  $R_{sh} = 100\Omega$ . What resistance must be inserted in the armature circuit to reduce its speed to 350 RPM? Assume armature current is same. (8)
- Q.5** a. A single-phase transformer has 350 primary and 1050 secondary turns. The net cross-sectional area of the core is  $55\text{cm}^2$ . If the primary winding be connected to a 400V, 50Hz single phase supply, calculate:
- (i) maximum value of flux density in the core
  - (ii) voltage induced in the secondary winding (8)

- b. A 3 phase, 4 pole, 50 Hz, 400V, 50hp star-connected induction motor is operating at a slip of 4 per cent, in order to deliver rated output power. Find out the following:
- (i) synchronous speed
  - (ii) speed of rotating air gap field
  - (iii) speed of the induction motor
  - (iv) frequency of the rotor induced emf
- (8)**
- 

**PART B**

**Answer at least TWO questions. Each question carries 16 marks.**

---

- Q.6** a. With the help of energy band diagram explain how conduction takes place in conductors, semiconductors and insulators. **(8)**
- b. What is P-N junction? Explain the formation of potential barrier and depletion layer without external voltage. **(8)**
- Q.7** a. With the help of neat diagram, explain zener diode voltage regulator. **(8)**
- b. Sketch circuit diagram and input-output waveforms of a negative series clipper circuit and positive shunt clipper circuits. **(8)**
- Q.8** a. Sketch and explain the shape of the common emitter input and output characteristics. Explain how the characteristics are determined experimentally **(8)**
- b. Compare the performance and characteristics of CB, CC and CE amplifiers. **(8)**
- Q.9** a. Draw circuit diagram and frequency response curve of single stage CE amplifier. Also discuss its working. **(8)**
- b. Draw the circuit of Colpitt's oscillator and explain its operation. **(8)**