

DiplETE – ET

Time: 3 Hours

DECEMBER 2014

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. Laplace transform of $\sin wt$ is:

(A) $\frac{s}{s^2 + w^2}$

(B) $\frac{s}{s + w}$

(C) $\frac{w}{s^2 + w^2}$

(D) $\frac{s^2}{s^2 + w^2}$

b. Applying maximum power transfer theorem, if the source impedance is equivalent to $R + jX$, the load impedance will be:

(A) $R + jX$

(B) R only

(C) $R - jX$

(D) $-jX$ only

c. For determining h-parameters of a network, the measurements should be under the condition of:

(A) input port short; output port open

(B) both ports open

(C) both ports short

(D) input port open; output port short

d. In a series resonant circuit, the impedance of the circuit at resonance is:

(A) minimum

(B) maximum

(C) infinite

(D) zero

e. The power factor at resonance in parallel RLC circuit is

(A) unity

(B) zero

(C) 0.8 lagging

(D) 0.8 leading

- f. A finite transmission line behave as an infinite line when the load end is:
- (A) terminated by any impedance
 - (B) terminated by characteristic impedance of the line
 - (C) open circuited
 - (D) short circuited
- g. The characteristic impedance of transmission line is given as:
- (A) $\sqrt{\frac{Z_{OC}}{Z_{SC}}}$
 - (B) $\sqrt{Z_{OC} \times Z_{SC}}$
 - (C) $Z_{OC} \times Z_{SC}$
 - (D) $\frac{Z_{OC}}{Z_{SC}}$
- h. A stub matching is more effective if done:
- (A) as close to the source as possible
 - (B) at a voltage maximum
 - (C) as close to the load as possible
 - (D) at a voltage minimum
- i. A band pass filter may be obtained by using a high pass filter followed by a:
- (A) High pass filter
 - (B) RC filter
 - (C) RL filter
 - (D) Low pass filter
- j. A simplest type of attenuator having only two resistors which can be used for matching between two unequal impedances is :
- (A) Symmetrical T attenuator
 - (B) Asymmetrical T attenuator
 - (C) Asymmetrical π attenuator
 - (D) Asymmetrical L attenuator

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

- Q.2** a. Find the value of $v(t)$ using Laplace transform if
- $$V(s) = \frac{s+2}{s(s+1)(s+3)}$$
- What is its value at $t = 0^+$ and $t = \infty$? (4+2+2)
- b. State and prove the shifting theorem of Laplace Transform. (8)
- Q.3** a. State and explain Thevenin's theorem. What are its limitations? (6+2)

- b. Apply the superposition theorem to the network shown in Fig.1 and obtain the current in the $(3 + j4)$ Ohm impedance. (8)

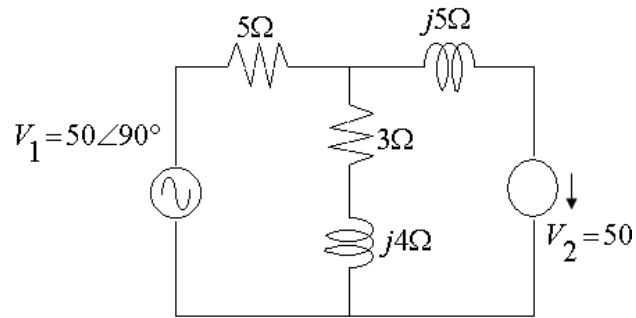


Fig.1

- Q.4 a. Find the z-parameters for the resistive network shown in Fig.2 (8)

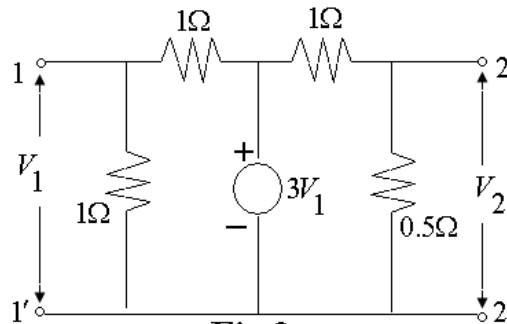


Fig.2

- b. The z-parameters of a two port network are $Z_{11} = 10 \Omega$, $Z_{22} = 20\Omega$, $Z_{12} = Z_{21} = 20\Omega$. Find the ABCD parameters of this two port network. (8)

- Q.5 a. The circuit shown in Fig.3 represents a parallel resonant circuit where R_L is the ohmic resistance of the inductor L. Find the resonant frequency of the circuit. (8)

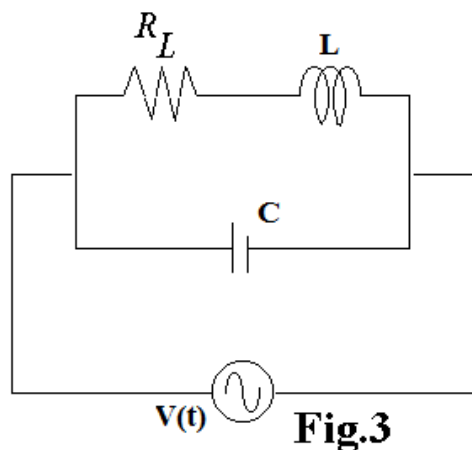


Fig.3

- b. A 220 V, 100 Hz AC source supplies a series LCR circuit with a capacitor and a coil. If the coil has $50 \text{ m}\Omega$ resistance and 5 mH inductance and resonant frequency of the circuit is 100 Hz, then find the value of capacitor. Also calculate Q factor and half power frequencies of the circuit. (4+2+2)
- Q.6** a. Define and explain phase velocity and group velocity of a uniform transmission line. (8)
- b. The primary constants of a line per loop km are $R = 196 \Omega$; $C = 0.09 \mu\text{F}$; $L = 7.1 \text{ mH}$ and leakage conductance is negligible. Calculate the characteristic impedance and the propagation constant at angular frequency of 5000 radians/sec. (8)
- Q.7** a. Derive expression for input impedance of open and short circuited line and show that characteristic impedance $Z_0 = \sqrt{Z_{OC} \times Z_{SC}}$ (8)
- b. A 100 km long transmission line is terminated by a resistance of 200 ohm. It has characteristics impedance $Z_0 = 600 \angle 0^\circ$ ohms, attenuation constant $\alpha = 0.01$ neper / km, phase shift constant $\beta = 0.03$ rad / km. Find the reflection coefficient and the impedance. (8)
- Q.8** a. Explain the operation and use of a quarter wave transformer. (8)
- b. A low loss line with $Z_0 = 70 \Omega$ terminates in an impedance of $Z_R = 115 - j80$. The wave length of the transmission is 2.5 metres; using the smith chart find:
 (i) Standing wave ratio
 (ii) Maximum and minimum line impedance
 (iii) Distance between load and first voltage maximum (8)
- Q.9** a. Draw the circuit of a symmetrical-T attenuator and derive the design equation. (2+6)
- b. Design m-derived low pass filter having a design impedance of 600Ω and cut-off frequency of 5000 Hz. The frequency of infinite attenuation is 6250 Hz. (8)