

DipIETE – ET/CS

Time: 3 Hours

DECEMBER 2014

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. A digital system that uses n-bits can go through _____

- (A) n^2-1 (B) 2^n
(C) 2^n-1 (D) 2^{n-1}

b. The 2's complement of the decimal -4 is _____

- (A) 0100 (B) 1100
(C) 1010 (D) 1011

c. Gray code is _____

- (A) Non weighted code (B) Cyclic code
(C) Reflected code (D) All of these

d. ROM contains _____

- (A) Programmable AND array and programmable OR array
(B) Programmable AND array and non-programmable OR array
(C) Non-programmable AND array and programmable OR array
(D) Non-programmable AND array and non-programmable OR array

e. Using N flip-flops would produce an output frequency from the last flip-flop equal to _____ of the input frequency.

- (A) same (B) one fourth
(C) half (D) three fourth

f. The number of flip-flops required for MOD-16 ring counter are _____

- (A) 2 (B) 4
(C) 16 (D) 32

- g. A four bit binary adder could be constructed with a minimum of
- (A) 3 one-bit full adder and a half adder
 (B) 4 one-bit full adder
 (C) 4 half adders
 (D) None of these
- h. A five bit Johnson counter in cascade with a five bit ring counter produces a frequency divider of _____
- (A) 25 (B) 10
 (C) 50 (D) 15
- i. The decoding glitches are far more likely to occur in the case of _____
- (A) Ripple counter (B) Parallel counters
 (C) Johnson counter (D) Ring counter
- j. Multiplexers are used in
- (A) Data Selection (B) Logic function generation
 (C) Parallel to Serial conversion (D) All of these

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

- Q.2** a. In a base-5 number system, 3 digit representations is used. Find out (i) Number of distinct quantities that can be represented.(ii) Representation of highest decimal number in base-5. (4)
- b. In a signed representation given binary string is $(11101)_2$. What will be the sign and magnitude of the number represented by this string in signed magnitude, 1's complement and 2's complement representation? (6)
- c. Convert the hexadecimal 2AC5.D to decimal, octal and binary. (6)
- Q.3** a. Obtain (a) minimal sum of product (b) minimal product of sum expression for the function $F(w, x, y, z) = \Sigma (0, 2, 3, 6, 7, 8, 10, 11, 12, 15)$. (6)
- b. Implement a three-input EX-NOR function using only two-input EX-NOR gates. (5)
- c. $A'B+C'D$ is a simplified Boolean expression of the expression $A'B'C'D+A'B'C'D+A'B$. Determine if there are any 'don't care' entries. (5)
- Q.4** a. The 100 kHz square waveform of **Fig. 1(a)** is applied to the clock input of the flip-flops shown in **Figs. 1(b)** and **(c)**. If the Q output is initially '0', draw the Q output waveform in the two cases. Also, determine the frequency of the Q output in the two cases. (8)

 


Fig.1(a)

 


Fig.1(b)

 


Fig.1(c)

- b. Design a mod-3 counter using JK flip-flop and explain its operation with the help of waveform. (8)

- Q.5** a. Design a 4 bit serial adder with the help of neat diagram. (8)

- b. Determine the number of half and full adder circuit blocks required to construct a 64-bit binary parallel adder. Also, determine the number and type of additional logic gates needed to transform this 64-bit adder into a 64-bit adder-subtractor. (8)

- Q.6** a. Distinguish between asynchronous and synchronous flip-flops. Design a 4 bit universal synchronous counter using JK flip-flops. (6)

- b. Design a synchronous counter that counts as 000, 010, 101, 110, 000, 010, _ _ _ Ensure that the unused states of 001, 011, 100 and 111 go to 000 on the next clock pulse. Use J-K flip-flops. What will the counter hardware look like if the unused states are to be considered as 'don't care's'. (6)

- c. Determine the modulus of the presettable counter shown in **Fig. 2**. If the counter were initially in the 0110 state, what would be the state of the counter immediately after the eighth clock pulse be? (4)

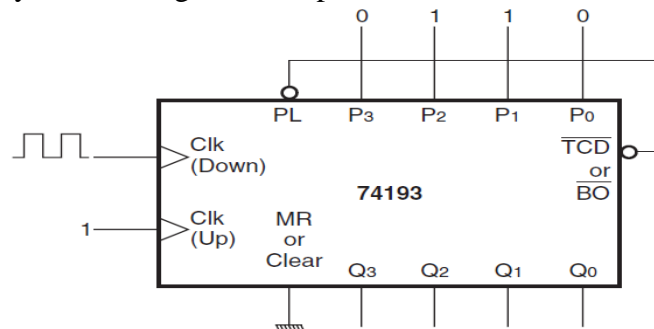


Fig.2

Q.7 a. Use an 8 input MUX to implement the following equation:
 $Y = A'.B'.C'.D' + A'.B'.C.D + A'.B.C'.D + A'.B.C'.D' + A.B'.C'.D + A.B'.C.D' + A.B.C'.D' + A.B.C'.D.$ (8)

b. Implement the functions defined by the following truth table in **Fig.3** using a decoder and NAND gates. (4)

A	B	C	Y ₁	Y ₂
0	0	0	0	1
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	0	0

Fig.3

c. What is priority encoder? Design a 4x2 priority encoder. (4)

Q.8 a. Draw the diagram of four bit universal shift register and explain its operation. (8)

b. Refer to the logic circuit of **Fig.3**. Determine the modulus of this counter and write its counting sequence. (8)

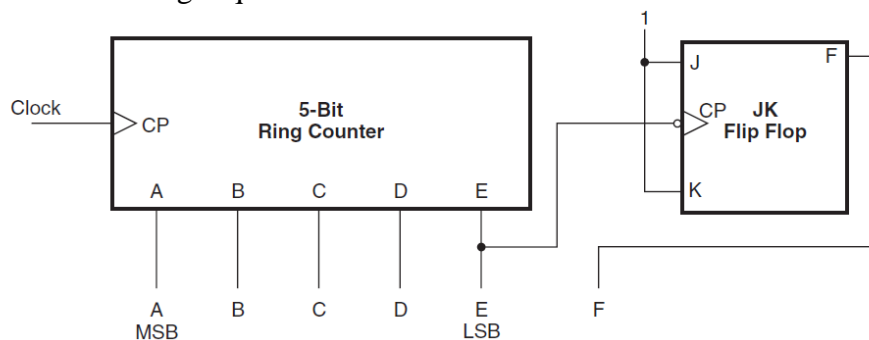


Fig.4

Q.9 a. It is required to obtain an 8K × 8 memory system for 8085 microprocessor system that has an addressing capability of 64K locations. Given memories are 2K × 8 ROM ICs and 2K × 8 RAM ICs. Obtain the exhaustive decoded system, which maps the 8K-memory system to begin from 8000H. (8)

b. Draw the general structure of DRAM and explain it. Also compare it with SRAM. (8)