

Subject: CIRCUIT THEORY & DESIGN

Time: 3 Hours

Max. Marks: 100

JUNE 2011**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

- a. If 'l' is number of links and 'b' is number of branches, then the size of the Tie-set matrix of a graph is _____ and the number of Tie-sets will be _____.
- (A) $l + b, b$ (B) $l \times b, l$
(C) $l - b, l \times b$ (D) $l / b, l + b$
- b. When uncharged capacitor is connected to a energy source, the conditions of the capacitor at $t = 0$ and at $t = \infty$ is
- (A) Short circuit and Short circuit (B) Open circuit and Short circuit
(C) Short circuit and Open circuit (D) Open circuit and Open circuit
- c. The Laplace transform of the function $\sin \omega t$ is
- (A) $\frac{\omega}{S^2 + \omega^2}$ (B) $\frac{1}{S^2 + \omega^2}$
(C) $\frac{S}{S^2 + \omega^2}$ (D) $\frac{1}{S + \omega}$
- d. In the analysis of networks using Thevenin's theorem, the equivalent impedance between the open circuited terminals (Z_{Th}) is calculated by
- (A) Open circuiting all voltage sources and current sources.
(B) Short circuiting current sources and Open circuiting voltages sources.
(C) Short circuiting all voltage sources and current sources
(D) Short circuiting voltage sources and Open circuiting current sources
- e. The value of Z_{11} for the network shown in Fig.1 is

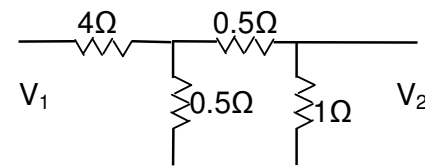


Fig.1

b. For the network shown in Fig.5, find the power dissipated by 50V source. (8)

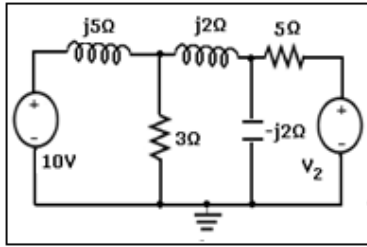


Fig.4

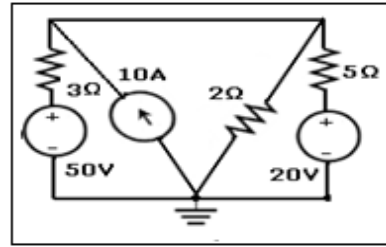


Fig.5

Q.4 a. Explain the terms (i) RMS value (ii) Duty cycle (8)

b. In the network shown in Fig.6, the switch K is closed at time $t=0$. Find the values of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0+$, given $R=10\Omega$, $L=1H$, $C=10\mu f$ and $V=10V$. (8)

Q.5 a. State and Prove Initial and Final value theorems. (8)

b. Find the Laplace transformation of the waveform shown in Fig.7. (8)

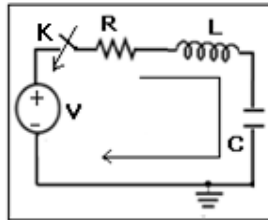


Fig.6

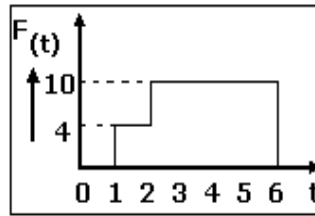


Fig.7

Q.6 a. What is Super Position Principle (SPP)? Explain. (6)

b. Using Thevenin's theorem find the current flowing through the galvanometer of the bridge network shown in Fig.8. (10)

Q.7 a. What are the restrictions laid on the location of poles and zeros of a system transfer function in the S-plane? (8)

b. For the network shown in Fig.9, obtain the dual network. (8)

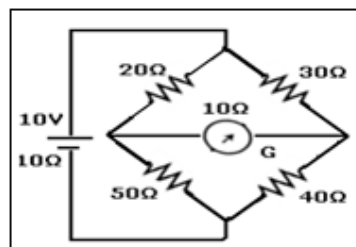


Fig.8

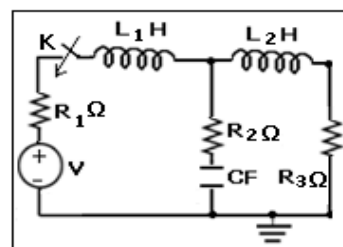


Fig.9

Q.8 a. Draw the h-parameter equivalent circuit and hence define different h-parameters (6)

b. Find Z and Y parameters for the network shown in Fig.10. (10)

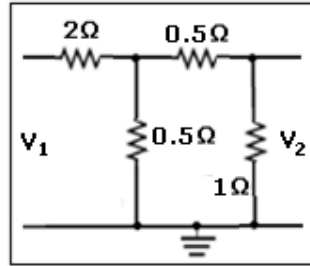


Fig.10

- Q.9** a. Draw the pole-zero diagram of a driving point function $Z(s) = \frac{s^4 + 10s^2 + 9}{s^2 + 4s}$. (6)
- b. Synthesize the following functions in Cauer form and show the synthesized network.

$$Z(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)} \quad (10)$$