

Subject: VLSI DESIGN

Time: 3 Hours

JUNE 2011

Max. Marks: 100

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. Substrate in nMOS FET is

- (A) N type (B) P type
(C) PN type (D) None

b. In depletion mode FET devices channel is established when

- (A) $V_{gs} = V_{DD}$ (B) $V_{gs} > V_t$
(C) $V_{gs} = 0$ (D) $V_{gs} > V_{DD}$

c. Transit time τ_{sd} is

- (A) $\frac{\text{Valocity}}{\text{Channel length}}$ (B) $\frac{\text{Channel length}}{\text{Velocity}}$
(C) $\frac{\text{Charge}}{\text{Electric field}}$ (D) $\frac{\text{Channel length}}{\text{Electric field}}$

d. Pull-up to Pull-down ratio $\frac{Z_{pu}}{Z_{pd}}$ for nMOS inverter driven by another nMOS inverter is

- (A) 8:1 (B) 4:1
(C) 6:1 (D) 16:1

e. Implant in depletion type transistor is indicated by dotted square of dimension

- (A) $6\lambda \times 6\lambda$ (B) $8\lambda \times 8\lambda$
(C) $4\lambda \times 4\lambda$ (D) $16\lambda \times 16\lambda$

f. Total channel resistance of nMOS inverter when it is ON is

- (A) 20 k Ω (B) 30 k Ω
(C) 40 k Ω (D) 50 k Ω

g. Static power dissipation is low in _____ inverter.

- (A) PMOS (B) nMOS
(C) CMOS (D) nMOS & CMOS

h. Scaling factor for Gate Area is

- (A) $1/\beta^2$ (B) $1/\alpha^2$
(C) $1/\beta$ (D) $1/\alpha$

i. In nMOS pass Transistor _____ level output is degraded.

- (A) Tristate (B) High and low
(C) Low (D) High

j. D-algorithm is used to test _____ circuit

- (A) Combinational (B) Sequential
(C) Both (A) and (B) (D) Flip-Flops

**Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.**

Q.2 a. Write the cross-sectional view of nMOS enhancement and depletion mode Transistor indicating all the layers and terminals. (6)

b. With neat sketch explain the P-Well Fabrication process. (10)

Q.3 a. Derive the expression for I_{ds} starting from transit time. (8)

b. What are the different types of pull-ups are used in MOS circuit? Explain briefly with neat sketch. (8)

Q.4 a. Draw & explain the circuit diagram and stick diagram for logic function $\bar{f} = x + yz$ (8)

b. With neat diagram explain design rules for wires and contact? (8)

Q.5 a. Define sheet resistance and standard unit of capacitance. (4)

b. Derive the expression for total delay when N inverters are cascaded to drive large capacitive load (6)

c. Calculate the total capacitance for the Fig.1. (6)

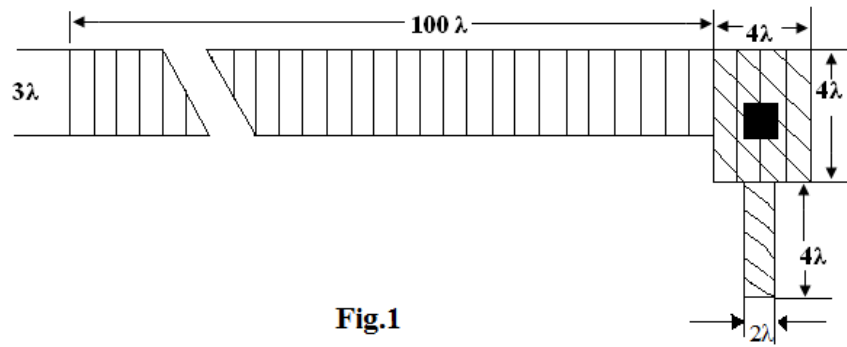


Fig.1

- Q.6** a. Derive the scaling factors for
 (i) Gate capacitance
 (ii) Operating frequency
 (iii) Power dissipation (8)
- b. Explain how transmission gate eliminates degradation of output levels.
 Write the circuit of 4:1 MUX using Transmission gate. (8)
- Q.7** a. Explain design methodology steps to design complex VLSI circuit. (6)
- b. Design a 4 bit adder and obtain the expression for Sum, Carry & Half Sum.(10)
- Q.8** a. Draw and explain the circuit and stick diagram of nMOS-pseudo static memory cell. (8)
- b. Discuss the methods for optimisation of area, power dissipation and time of CMOS inverter. (8)
- Q.9** a. Explain the method for detection of stuck at faults using sensitized path based testing technique. Determine the test vector for SA1 detection for the circuit shown in Fig.2. (8)

 


Fig.2

- b. Draw the circuit of BILBO and explain briefly. (8)