

## DipIETE – ET (OLD SCHEME)

---

Code: DE08  
Time: 3 Hours

**JUNE 2011**

Subject: ANALOG ELECTRONICS  
Max. Marks: 100

**NOTE:** There are 9 Questions in all.


- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
  - The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
  - Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
  - Any required data not explicitly given, may be suitably assumed and stated.
- 

**Q.1 Choose the correct or the best alternative in the following:** **(2×10)**

- a. A transistor is said to be in quiescent stage when
- (A) emitter junction bias is just equal to collector junction bias.  
(B) no currents are flowing.  
(C) no signal is applied to the input.  
(D) it is unbiased.
- b. The main component responsible for lowering of gain in an R-C coupled amplifier in low frequency range is
- (A) Biasing system. (B) resistor  $R_E$ .  
(C) Coupling capacitor  $C_C$  (D) transistor itself.
- c. Which of the following classes of amplifiers has maximum distortion?
- (A) Class A (B) Class B  
(C) Class AB (D) Class C
- d. Feedback in amplifier always helps in
- (A) controlling its output. (B) increasing its gain.  
(C) reducing its input impedance. (D) stabilizes its gain.
- e. A crystal oscillator provides very stable frequency because of
- (A) high stability of the crystal (B) the rigid crystal structure  
(C) low  $X_L/R$  ratio of the crystal (D) high Q of the crystal
- f. Stagger tuning is achieved by
- (A) double tuned circuit.  
(B) tuned circuits which are tuned to same frequency.  
(C) tuned circuits which are tuned to slightly different frequencies.  
(D) circuits tuned at harmonic frequencies.

- g. In a JFET, increase in applied external bias to the gate causes
- (A) decrease in size of depletion regions.
  - (B) increase in drain current.
  - (C) decrease in channel resistance.
  - (D) decrease in drain current to achieve pinch-off voltage.
- h. Schmitt trigger is basically
- (A) an astable multivibrator
  - (B) a monostable multivibrator
  - (C) a bistable multivibrator
  - (D) an oscillator
- i. For faster switching action of a transistor
- (A) a capacitor may be connected across the base resistance.
  - (B) a capacitor may be connected in series with the base resistance.
  - (C) a capacitor may be connected across  $R_E$ .
  - (D) the value of the coupling capacitor may be increased


j. The circuit shown in Fig.1 is

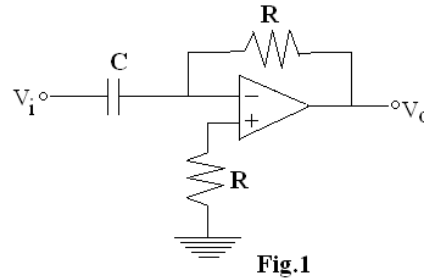


- (A) an adder
- (B) a differentiator.
- (C) an integrator
- (D) comparator

**Answer any FIVE Questions out of EIGHT Questions.  
Each question carries 16 marks.**

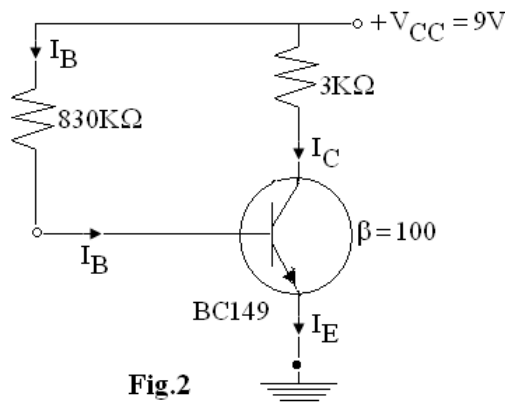- Q.2** a. Draw the circuit diagram of self Biasing and explain how does this circuit provides bias stabilization automatically. (10)
- b. Calculate the operating point for the Fixed Biasing transistor circuit shown in Fig.2 and draw its dc load line. (6)



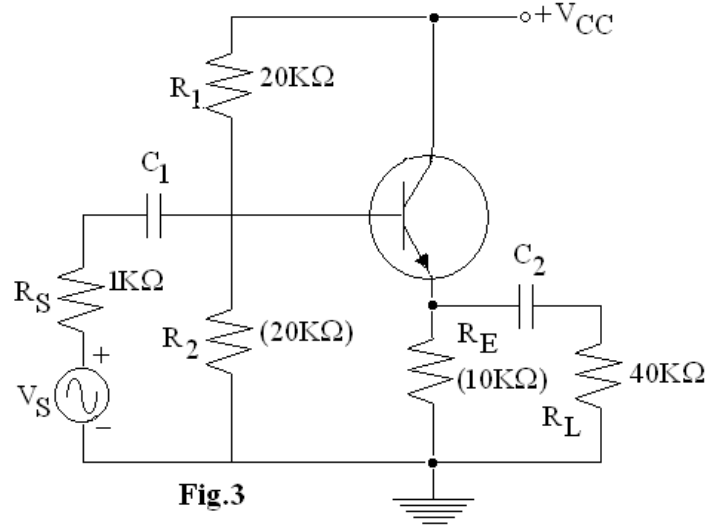
- Q.3** a. Draw the hybrid Pi model for transistor in CE configuration at lower frequency and briefly explain the components of the model. (9)
- b. Calculate the current gain ( $A_I$ ), voltage gain ( $A_V$ ) and power gain ( $A_P$ ) for the common collector amplifier shown in Fig.3. The given transistor h-parameters are  $h_{ic} = 1.4K\Omega$ ,  $h_{fc} = 100$  and  $h_{rc} = 20\mu A/V$ . (7)



- Q.4** a. Compare the characteristic performances of CE, CB, CC configurations with their applications. (7)
- b. Draw the circuit diagram of single tuned voltage amplifier and explain its working. What are its limitations? (9)
- Q.5** a. Draw the circuit of class-B Push-Pull amplifier and explain its operation with neat waveforms. (10)
- b. A transformer-coupled class-A Power amplifier draws a current of 200 mA from a collector supply of 10V, when no signal is applied to it. Determine
- Maximum output power,  $P_{out}$
  - DC power input,  $P_{in}$
  - Maximum collector efficiency,  $\eta_{max}$
- (6)
- Q.6** a. What is an oscillator? Draw the circuit diagram of RC-phase shift oscillator using BJT and explain its operation. Mention its applications. (10)
- b. The R-C circuit of a Wein-bridge oscillator consists of  $R_1 = R_2 = 220K\Omega$  and  $C_1 = C_2 = 250PF$ . Determine the frequency of oscillation. (6)
- Q.7** a. Draw the circuit of zero-crossing detector using Op-Amp and explain its operation with the help of input and output waveforms. (8)

- b. An Op-Amp inverting amplifier has  $R_f = 500\text{K}\Omega$  and  $R_1 = 5\text{K}\Omega$ . Determine its
- Voltage gain ( $A_v$ )
  - Input resistance ( $R_{in}$ )
  - Output resistance ( $R_o$ )
  - Output voltage ( $V_{out}$ )
- (8)**

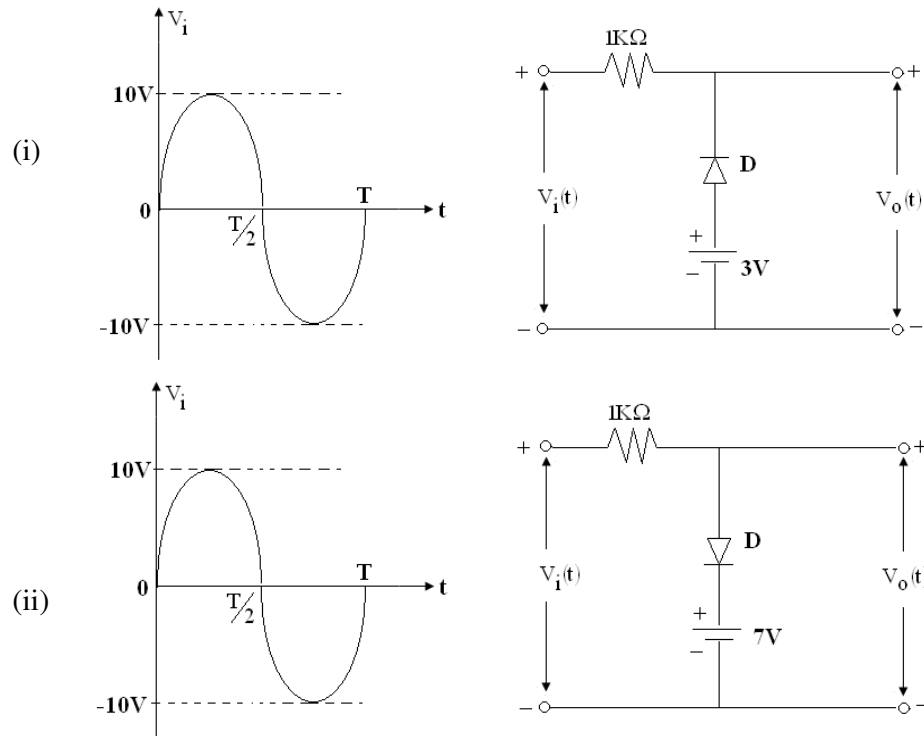- Q.8** a. Determine the output voltages for the following biased clipping circuits. Assume ideal diodes. **(6)**



- b. Draw the circuit of monostable multivibrator using Bipolar Junction Transistors and explain its working. What are its applications? **(10)**

- Q.9** a. What is Thermal Run-away in Transistors? How to avoid it? **(4)**
- b. Why harmonic distortion is prominent in Power amplifiers? Support your answer with mathematical expressions. **(6)**
- c. What is Input offset voltage and explain its significance in Op-Amp? **(6)**