

DipIETE – ET (OLD SCHEME)

Code: DE09
Time: 3 Hours

JUNE 2011

Subject: DIGITAL ELECTRONICS
Max. Marks: 100

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

- a. The parity of the binary number 11001110
- (A) is even. (B) is not known
(C) is odd (D) is same as the number of zeros
- b. The most suitable gate for comparing two bits is
- (A) AND (B) OR
(C) NAND (D) EX-OR
- c. The digital logic family has the maximum logic swing is
- (A) I^2L (B) ECL
(C) CMOS (D) TTL
- d. The number of 4-line-to-16-line decoders required to make an 8-line-to-256-line Decoder is
- (A) 16 (B) 17
(C) 32 (D) 64
- e. A twisted-ring counter consisting of six FLIP-FLOPS will have
- (A) 6 states (B) 12 states
(C) 64 states (D) 128 states
- f. When representing in the following code the consecutive decimal numbers differ only in one bit is
- (A) Excess-3 (B) Gray
(C) BCD (D) Hexadecimal
- g. The speed of conversion is maximum in
- (A) Successive-Approximation A/D converter
(B) Parallel-Comparator A/D converter
(C) Counter ramp A/D converter
(D) Dual-slope A/D converter

- h. In an R-2R Ladder D/A converter, the input resistance is
- (A) not same for all digital inputs (B) R for each input
(C) 2R for each input (D) 3R for each input
- i. It is desired to have a 64X8 memory. The memories available are of 16X4 size. The number of memories required will be
- (A) 8 (B) 6
(C) 4 (D) 2
- j. The minimum number of bits required to represent negative numbers in the range of -1 to -9 using twos complement representation is
- (A) 2 (B) 3
(C) 4 (D) 5

**Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.**

- Q.2** a. Solve the equation $23.6_{10} = X_2$ for X (6)
- b. Add -20 with +26 using 8 bit 2's complement arithmetic (6)
- c. Convert the Decimal number 430 to its Excess-3 equivalent (4)
- Q.3** a. Show that $XY + \overline{XZ} + X\overline{Y}Z$ ($XY + Z$) = 1 using Boolean Algebraic Theorems (8)
- b. State and prove De-morgan's Theorems. (8)
- Q.4** a. What is a Tri-state Logic? Draw the logic diagram of Tri-state Logic Inverter and explain its operation with the help of truth table. (8)
- b. Draw the K-map for the following function and reduce it.
 $F(A, B, C, D) = \sum m(1,3,5,8,9,11,15) + d(2,13)$ (8)
- Q.5** a. What is full adder? Design the logic circuit for it using NAND gates only. (10)
- b. Implement the following function using a 4 to 1 multiplexer
 $F(A,B,C) = \sum m(1,3,5,6)$ (6)
- Q.6** a. What is an Encoder? Design a 10 line to 4 line Decimal to BCD encoder. (8)
- b. Explain the operation of 4 bit digital comparator. (8)
- Q.7** a. Design a Mod-5 Synchronous counter. (8)
- b. Give the circuit diagram of 4-bit SISO shift register and explain its working (8)

- Q.8** a. Differentiate between Static RAMs and Dynamic RAMs. Draw the logic diagram of a Static RAM cell and explain its operation. **(10)**
- b. Compare ROM, PROM, EPROM, UVEPROM, EEPROM. **(6)**
- Q.9** a. Explain the operation of Successive Approximation A/D Converter. List out its main Features. **(8)**
- b. A 6 bit R-2R ladder D/A converter has a reference voltage of 6.5 V. It meets Standard linearity. Find
- (i) The Resolution in Per cent
 - (ii) The Resolution in Volts
 - (iii) The Full Scale Voltage
 - (iv) The Output Voltage for the code 011100 **(8)**