

DiplETE – ET (OLD SCHEME)

Code: DE22
Time: 3 Hours

Subject: INDUSTRIAL ELECTRONICS
Max. Marks: 100

JUNE 2011

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

a. An SCR can be operated

- (A) Only under reverse biased condition
- (B) Only under forward biased condition
- (C) Both forward & reverse bias conditions
- (D) Without biasing

b. A 3-phase full wave fully controlled bridge rectifier uses

- (A) 4 SCR's
- (B) 6 SCR's
- (C) 8 SCR's
- (D) 3 SCR's

c. According to their connections inverters are classified as

- (A) Series inverters
- (B) Parallel inverters
- (C) Bridge inverters
- (D) All of the above

d. Average output of a dc chopper is given by

- (A) $V_O = V_{dc} / \text{duty cycle}$
- (B) $V_O = V_{dc} \times \text{duty cycle}$
- (C) $V_O = \text{duty cycle} / V_{dc}$
- (D) none of these

e. A cycloconverter is a device which

- (A) Measures frequency of A.C. mains.
- (B) Converts A.C. of one frequency to A.C. of other frequency.
- (C) Converts A.C. into D.C.
- (D) Converts D.C. into A.C.

f. UJT is used for

- (A) Controlling the power.
- (B) Triggering a triac.
- (C) Triggering an SCR.
- (D) Triggering a Diac.

- g. In dielectric heating process the supply requires
- (A) Low frequency. (B) Very low frequency.
(C) High frequency. (D) Very high frequency.
- h. ON and OFF frequency of a chopper depends on
- (A) Applied voltage. (B) The load current.
(C) Type of the chopper. (D) Output voltage.
- i. Induction heating is used for
- (A) Melting (B) Annealing
(C) Forging (D) All the above.
- j. Induction heating requires
- (A) A.C. input. (B) High frequency A.C. input
(C) D.C. input. (D) Both A.C. and D.C. input

**Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.**

- Q.2** a. Explain the Principle of operation & V-I Characteristics of an SCR. (8)
- b. Explain light triggering and dv/dt triggering circuit of an SCR. (4+4)
- Q.3** a. Explain the circuit of a three - phase bridge inverter for 180° conduction. Also draw the waveforms. (8)
- b. A three - phase bridge inverter is fed by a 400 volts battery. The load is star connected and has a resistance of 10 ohms per phase. Find rms load current, power output, and average and rms thyristor current. Assume 120° mode of operation. (8)
- Q.4** a. Explain the circuit of a single-phase fully controlled bridge rectifier with resistive R- load. Also draw the waveforms. (8)
- b. Explain the principle of operation and application of a single-phase cyclo - converter. (8)
- Q.5** a. Explain the different commutation methods for choppers. (8)
- b. A dc chopper has an input voltage of 230 V and an output voltage of 150 V. It is operating at a frequency of 1 kHz. Find the periods of conduction and blocking in each cycle. (8)

- Q. 6** a. In a dielectric heating process a voltage of 230 V is applied at 30kHz .if the electrodes used have area of 4 cm^2 separated by 8 cm what is the dielectric loss filled between the electrodes? Assume phase angle of dielectric = 30° and dielectric constant is 10. (8)
- b. Explain the process of resistance welding with a suitable diagram. Also give the applications of resistance welding. (8)
- Q. 7** a. What is meant by thermal loss in dielectric heating? Explain the process of dielectric heating. (8)
- b. Give the classification of inverters and applications of series and parallel inverters. (4+4)
- Q. 8** a. Explain the circuit of the single-phase fully controlled rectifier with RL load and with freewheeling diode. Discuss the function of the diode? Also draw the waveforms. (8)
- b. Why induction heating is preferred over other types of heating? Where all is it used? (8)
- Q.9** Write notes on: -
- (i) D.C. motor speed control. (5)
- (ii) Application of choppers. (5)
- (iii) SCR rating. (6)