

**Subject: NETWORKS AND TRANSMISSION LINES**

Time: 3 Hours

**JUNE 2011**

Max. Marks: 100

**NOTE: There are 9 Questions in all.**

- **Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.**
- **The answer sheet for the Q.1 will be collected by the invigilator after 45 Minutes of the commencement of the examination.**
- **Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.**
- **Any required data not explicitly given, may be suitably assumed and stated.**

---

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

a. Identify the passive element among the following:

- |                    |                    |
|--------------------|--------------------|
| (A) Voltage source | (B) Current source |
| (C) Inductor       | (D) Transistor     |

b. The power dissipation in each of 3 parallel branches is 1W, what is the total power dissipation of the current?

- |        |        |
|--------|--------|
| (A) 1W | (B) 4W |
| (C) 3W | (D) 0  |

c. Mesh analysis is based on

- |                            |                            |
|----------------------------|----------------------------|
| (A) Kirchoff's current law | (B) Kirchoff's voltage law |
| (C) Both                   | (D) None                   |

d. If a network has B branches, N nodes, then the number of mesh current equations would be

- |                   |                   |
|-------------------|-------------------|
| (A) $B - (N - 1)$ | (B) $N - (B - 1)$ |
| (C) $B - N - 1$   | (D) $(B + N) - 1$ |

e. Superposition theorem is not valid for

- |                       |                       |
|-----------------------|-----------------------|
| (A) Voltage responses | (B) Current responses |
| (C) Power responses   | (D) All of the above  |


f. When the superposition theorem is applied to any circuit, the dependent voltage source in the circuit is always

- |            |                       |
|------------|-----------------------|
| (A) Opened | (B) Shorted           |
| (C) Active | (D) None of the above |


- g. Thevenin's impedance  $Z_{TH}$  is found by
- (A) short circuiting the given 2 terminals
  - (B) between any two open terminals
  - (C) removing voltage sources along with terminal resistances
  - (D) between same open terminals as  $V_{th}$
- h. The transient response occurs
- (A) Only in resistive circuits
  - (B) Only in inductive circuits
  - (C) Only in capacitive circuits
  - (D) Both (B) and (C)
- i. Transient current in an RLC circuits is oscillatory when
- (A)  $R = 2\sqrt{\frac{L}{C}}$
  - (B)  $R=0$
  - (C)  $R > 2\sqrt{\frac{L}{C}}$
  - (D)  $R < 2\sqrt{\frac{L}{C}}$
- j. Which parameters are widely used in transmission line theory?
- (A) Z-parameters
  - (B) Y-parameters
  - (C) ABCD parameters
  - (D) H-parameters

**Answer any FIVE Questions out of EIGHT Questions.  
Each question carries 16 marks.**

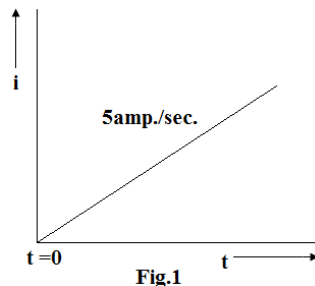- Q.2** a. The current in a 3 henry inductor varies as shown in Fig.1. Find the following quantities after the current has flown for two seconds:
- (i) flux linkage in the system
  - (ii) the time rate of change of flux linkages in the system
  - (iii) the quantity of charge having passed through the inductor. (8)



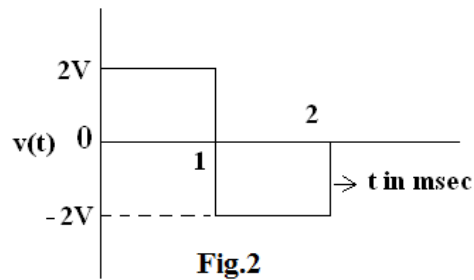
- b. Consider a waveform of voltage given in Fig.2 applied to an inductor of 2 mH. Obtain the waveforms of current in the inductor. Assume that at  $t=0$  the energy and thus current in it to be 0. (8)



**Q.3** a. A voltage pulse of width  $b$  and magnitude 8 volts is applied at time  $t = 0$  to a series R-C circuit comprising a resistor  $R = 1\Omega$  and capacitor  $C = \frac{1}{4}$  farad. Find the current  $i(t)$ . Assume zero charge across the capacitor  $C$  before application of voltage pulse. (8)


b. State and prove initial and final value theorems. (8)

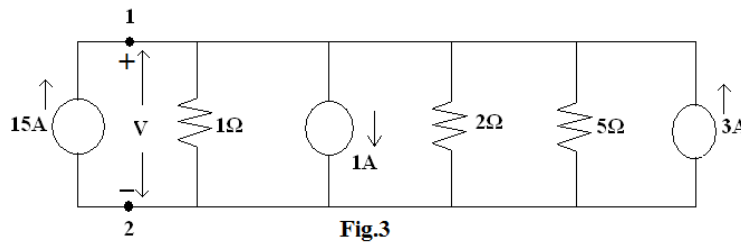**Q.4** a. Consider the network reduce it to a single current source and single resistor network at the terminals 1 and 2. Also find the voltage  $V$  across them (Fig.3). (8)




b. State and prove superposition theorem. Also give its significance. (8)

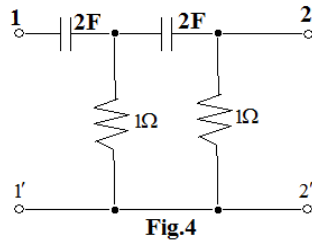**Q.5** a. Find the y-parameters for the given R.C. ladder network. (Fig.4) (8)



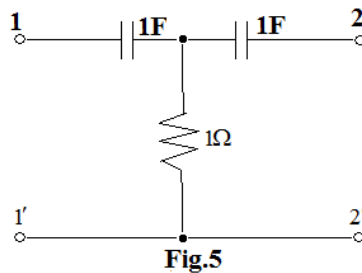b. Find the transmission parameters for the given R-C network shown in Fig.5. (8)



- Q.6** a. Find the current  $i(t)$  in the network (Fig.6), if the switch is closed at  $t = 0$ . The voltage across capacitor at  $t(0^-)$  is 5V. (8)

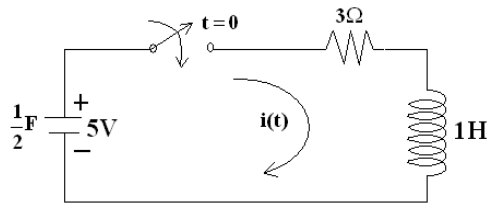


Fig.6

- b. Draw the phasor diagram and derive the condition for resonance in a parallel RLC circuit shown in Fig.7. (8)

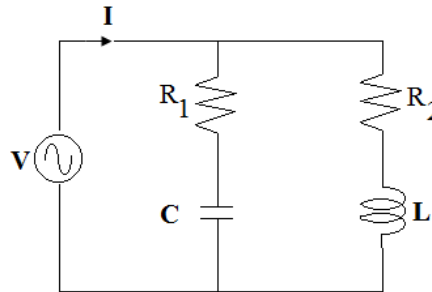


Fig.7

- Q.7** a. A lossless line of  $400\Omega$  of length 150 cm is excited by an ac source at 600MHz frequency. The I voltage minima was observed at a distance of 28 cm from the load. If the VSWR is 2.077. Find the input impedance and load impedance. (8)

- b. The characteristic impedance of a certain line is  $710\sqrt{14}$  and the propagation constant is  $0.007 + j0.028/\text{km}$ . The line is terminated in a  $300\Omega$  resistor. Calculate the input impedance of the line if its length is 100 km. (8)

- Q.8** Write short notes on any **TWO** of the following:

- (i) Quarter wave short circuit line.
- (ii) Half wave short circuited line
- (iii) Quarter wave open circuited line.
- (iv) Half wave open circuited line.

(8+8)

- Q.9** a. Derive equations for phase shift and attenuation constant for constant K LPF and HPF. (8)

- b. Design the elements of a symmetrical Bridged T attenuator. (8)