

Code: AE53/AC53/AT53/AE103
Subject: ELECTRONIC DEVICES & CIRCUITS

AMIETE – ET/CS/IT {Current & New Scheme}

Time: 3 Hours

JUNE 2016

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

- a. A loop that does not contain any other loop in it is called

(A) Node	(B) Branch
(C) Mesh	(D) Junction
- b. In a Half – Wave rectifier with resistive load, the output DC voltage is (Where V_m is peak voltage across transformer secondary)

(A) $\frac{V_m}{\pi}$	(B) $\frac{V_m}{2}$
(C) $\frac{V_m}{\sqrt{2}}$	(D) $\frac{2V_m}{\pi}$
- c. If Emitter - Base junction is reverse biased and Collector – Base junction is forward biased in a BJT, then the device is said to be in

(A) Forward Active	(B) Saturation
(C) Cut off	(D) Reverse Active
- d. The main advantage of CMOS circuit is

(A) High voltage gain	(B) Low Power Consumption
(C) Large Current	(D) Large bandwidth
- e. If the individual gains of a two stage RC coupled amplifier are A and B, then the overall gain is equal to (Where A and B are in dB)

(A) A+B	(B) A-B
(C) A×B	(D) A/B
- f. The maximum theoretical efficiency of series fed class A amplifier is

(A) 50%	(B) 25%
(C) 78.5%	(D) 85%
- g. The type of feedback configuration in which input impedance decreases and output impedance increases is

(A) Voltage Series	(B) Voltage Shunt
(C) Current Series	(D) Current Shunt

Code: AE53/AC53/AT53/AE103
Subject: ELECTRONIC DEVICES & CIRCUITS

- h. The frequency of oscillation of Wien Bridge Oscillator is given by
 (A) $\frac{1}{2\pi RC}$ (B) $2\pi RC$
 (C) $\frac{1}{2\pi\sqrt{6}RC}$ (D) $2\pi\sqrt{6}RC$
- i. The epitaxial growth process is carried out in a reactor at about
 (A) $10000^\circ C$ (B) $5000^\circ C$
 (C) $1000^\circ C$ (D) $100^\circ C$
- j. In class A amplifier, the Q-point, on the load line, lies at
 (A) Cut off point (B) Centre
 (C) Above cut off point (D) Beyond cut off point


Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

- Q.2** a. State and explain KCL & KVL. (8)
 b. Derive the expression for the equivalent resistance when resistances R_1, R_2 and R_3 are connected in series and in parallel. (8)

- Q.3** a. Draw the circuit of Half-wave Rectifier explain its working assuming ideal diode. (8)
 b. Explain the working of voltage multiplier circuits. (8)

- Q.4** a. Explain the operating modes of BJT with suitable diagram. (8)

 - b. Calculate the values of I_B, I_C and V_{CE} for the circuit shown in Fig.1, if the transistor has $\beta = 100$. Assume $V_{BE} = 0.7V$.



- Q.5** a. Explain hybrid Π – model of BJT. (8)

- b. Explain the circuit of Emitter-Coupled Pair with a neat diagram. (8)

- Q.6** a. Explain
 (i) Frequency distortion (ii) Phase distortion
 (iii) Amplitude distortion in amplifier (9)

- b. Explain the effect of Bypass Capacitor in a BJT amplifier circuit. (7)

Code: AE53/AC53/AT53/AE103
Subject: ELECTRONIC DEVICES & CIRCUITS

- Q.7** a. Explain the working of a series – fed class A amplifier and derive the expression for its efficiency. **(10)**
- b. Explain how the push – pull signals are produced for class B operation. **(6)**
- Q.8** a. Explain the effect of negative feedback on
(i) Non linear distortion & noise
(ii) Gain & Bandwidth **(8)**
- b. Draw the circuit of UJT Relaxation Oscillator and derive the expression for its frequency of oscillation. **(8)**
- Q.9** a. Write the advantages of IC technology. **(4)**
- b. Explain the Photolithography process in IC fabrication. **(6)**
- c. Explain the PNP transistor fabrication. **(6)**