

AMIETE – ET (Current & New Scheme)

Time: 3 Hours

JUNE 2016

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions selecting at least TWO questions from each part, each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2 × 10)

a. An ideal operational amplifier has

- | | |
|-------------------------------|--------------------------|
| (A) Infinite output impedance | (B) zero input impedance |
| (C) Infinite bandwidth | (D) All of these |

b. What is the output waveform of the following network?

 


Fig. 1

- | | |
|---------------------|--------------------|
| (A) Sine wave | (B) Square wave |
| (C) Triangular wave | (D) Saw tooth wave |

c. What starts a free-running multivibrator?

- | | |
|-------------------------|---------------------|
| (A) a trigger | (B) an input signal |
| (C) an external circuit | (D) nothing |

d. What will be the binary equivalent of the decimal number 151.75?

- | | |
|-----------------|-----------------|
| (A) 10000111.11 | (B) 11010011.01 |
| (C) 00111100.00 | (D) 10010111.11 |

- e. The 555 timer can be used in which of the following configurations?
 (A) astable, monostable (B) monostable, bistable
 (C) astable, toggled (D) bistable, tristable
- f. When both inputs of a J-K flip-flop reset, the output will:
 (A) be invalid (B) not change
 (C) change (D) toggle
- g. A 4-bit R/2R digital-to-analog (DAC) converter has a reference of 5 volts. What is the analog output for the input code 1010.
 (A) 0.3125 V (B) 3.125 V
 (C) 0.78125 V (D) -3.125 V
- h. Which of the following expressions is in the sum-of-products (SOP) form?
 (A) $Y = (A + B)(C + D)$ (B) $Y = AB(CD)$
 (C) $Y = AB + \bar{A}B$ (D) $Y = (\bar{A} + \bar{B}).(A + B)$
- i. A basic S-R flip-flop can be constructed by cross-coupling of which of the basic logic gates?
 (A) AND or OR gates (B) XOR or XNOR gates
 (C) NOR or NAND gates (D) AND or NOR gates
- j. The Schmitt trigger is a two-state device that is used for:
 (A) pulse shaping (B) peak detection
 (C) input noise rejection (D) filtering

PART (A)

Answer at least TWO Questions. Each question carries 16 marks.

- Q.2** a. Classify ICs on the basis of application, devices used and chip complexity. (6)
 b. Calculate the output voltage from the circuit of Fig.2 for an input of $120 \mu\text{V}$. (4)

 


Fig. 2

- c. Draw and explain the block diagram of op-amp. Also explain the basic differential amplifier. (6)

Q.3 a. For the Instrumentation amplifier as shown in Fig 3. Verify that

$$V_0 = \left[1 + \frac{R_2}{R_1} + \frac{2R_2}{R} \right] (V_2 - V_1) \quad (8)$$

 


Fig. 3

b. The output of op-Amp Voltage follower is a Triangular wave as shown in Fig.4 for a square wave input of frequency 2MHz and 8 V peak to peak amplitude. What is the slew rate of op-Amp? (8)

 


Fig. 4

Q.4 a. Draw a sample and hold circuit. Explain its operation and indicate its uses. (8)

b. Explain the following: (8)

- (i) Transconductance Amplifier
- (ii) Schmitt Trigger

Q.5 a. Draw and explain the operation of triangular wave generator. (8)

b. What do you understand by DAC techniques? List its various types and explain any one of these. (8)

PART (B)

Answer at least TWO Questions. Each question carries 16 marks.

- Q.6** a. Explain the following: (8)
- (i) De Morgan's theorem
 - (ii) Universal logic gates
 - (iii) Alphanumeric codes
 - (iv) Advantages of digital techniques over analog
- b. Represent each of the following signed decimal numbers as a signed binary numbers in the 2's complement system. Use a total of five bits, including the sign bit. (8)
- (i) +13 (ii) -9 (iii) +3 (iv) -8

- Q.7** a. Reduce the combinational logic circuit given in the Fig. 5 to a minimum form. (6)

 


Fig.5

- b. Design a logic circuit that has three inputs, A, B, and C and whose output will be HIGH only when a majority of inputs are HIGH. (4)
- c. Draw K-map and simplify the given expression: (6)
- $$f(A,B,C) = AB + A(B + C) + B(B + C)$$
- Q.8** a. Explain the designing of full adder with a neat diagram. (4)
- b. Implement Full Adder using multiplexers. (4)
- c. Explain the working of a J-K flip flop? Design DFF using JKFF. (8)
- Q.9** a. Explain with a neat diagram, the working of synchronous MOD-16 counter. List the advantages of synchronous counters over asynchronous counters. (8)
- b. Explain **any two** of the following: (8)
- (i) Ring counter
 - (ii) D latch
 - (iii) Serial in parallel out Shift Register
 - (iv) Propagation delay in Ripple Counter