

Time: 3 Hours

**JUNE 2016**

Max. Marks: 100

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

- a. A parallel RLC circuit ( $R=1$  ohm,  $L=1H$ ,  $C=1F$ ) is excited by a unit step current. The steady state current through L will be  
 (A) Zero (B)  $1/3$  unit  
 (C)  $2/3$  unit (D) 1 unit
- b. The Laplace transform of the unit impulse is  
 (A) s. (B) 0.  
 (C)  $s e^{-s}$ . (D) 1.
- c. Norton's theorem results in  
 (A) Current source in parallel with an impedance  
 (B) A current and an impedance in series  
 (C) A voltage source only  
 (D) A current source only
- d. The VSWR lies in the range of  
 (A) 0 to 1 (B) 1 to infinite  
 (C) 0 to infinite (D)  $-1$  to  $+1$
- e. A Smith Chart is used for solving problems in  
 (A) Radio wave propagation (B) Transmission line  
 (C) Antenna system (D) Power transfer problems
- f. The characteristics impedance of a distortion-less line is  
 (A) Real (B) inductive  
 (C) capacitive (D) complex
- g. Thevenin's theorem is valid for a network containing only  
 (A) Non-linear network (B) linear elements  
 (C) resistances (D) reactive elements
- h. A parallel resonant circuit can be used  
 (A) as a high impedance  
 (B) to reject a small band of frequencies  
 (C) Both (A) and (B)  
 (D) to amplify certain frequency

**Code: DE107**

**Subject: NETWORKS AND TRANSMISSION LINES**

- i. One neper is equal to  
 (A) 0.8686 db (B) 8.686 db  
 (C) 118.686 db (D) 86.86 db
- j. When 3 equal resistances of 5 ohm are connected in delta, what is the resistance in one of the arms of the equivalent star circuit  
 (A) 5 ohm (B) 1.33 ohm  
 (C) 15 ohm (D) 10 ohm

**Answer any FIVE Questions out of EIGHT Questions.  
 Each question carries 16 marks.**

- Q.2** a. Explain common singularity functions. (3)  
 b. Find the inverse Laplace transform of the following function (5)  

$$F(s) = \frac{s+4}{2s^2+5s+3}$$
- c. State and prove Initial and Final value theorem. (8)
- Q.3** a. State & prove  $\pi$ -T equivalent theorem. (8)  
 b. A network function has a zero at 3 mega radians/sec and poles at 2 and 4 mega-radians/sec. It is required to give a driving point impedance of +j 100 ohms at 1 mega-radians/sec. Determine the schematic diagram of a series type Foster network & the values of the elements. (8)
- Q.4** a. Find the relationship between two-port Z, Y, h and ABCD parameters. (8)  
 b. Explain the application to the analysis of typical two-port networks. (8)
- Q.5** a. Explain the characteristic curves of series RLC & parallel RLC resonance circuit. (8)  
 b. A 100mH inductor with 500 ohm self resistance is in parallel with a 5nF capacitor. Find the resonance frequency of the combination. Sketch the variation of impedance with frequency. (4)  
 c. Compare the series & parallel resonance circuit. (4)
- Q.6** a. Derive transmission line equations & find its constants. (8)  
 b. A generator of 1 volt, 1000Hz, supplies power to 1000 km long open wire line terminated in  $Z_0$  (Characteristic impedance) & having following parameters :  
 $R=10.4$  ohms,  $L=0.0037$  henry,  $G=0.8$  micromhos,  $C=0.00835$ mfd.  
 Calculate the phase velocity, Characteristic impedance, propagation constant & power delivered at the receiving end. (8)
- Q.7** a. Define reflection and derive the relation for reflection coefficient. (8)  
 b. Derive expression for Input Impedance of open and short circuited lines. Also find secondary line constants in terms of  $Z_{OC}$  &  $Z_{SC}$ . (4+4)
- Q.8** a. Explain the basis for construction of Smith chart. Illustrate as to how it can be used as an admittance chart. (10)  
 b. A lossless transmission line in air has a characteristic impedance of 300 ohms & is terminated by unknown impedance. When the frequency is 200 Mhz, the standing wave ratio is 4.48 and first voltage minima is situated at 6 cm from the load. Determine the complex reflection co-efficient and terminating impedance of the line. (6)
- Q.9** a. Define Band pass filter and explain constant-k filter and m-derived filter. (8)  
 b. Draw and explain asymmetrical L and  $\pi$  attenuator. (8)