

**DiplETE – ET (NEW SCHEME)**

Time: 3 Hours

**June 2018**

Max. Marks: 100

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

- a. According to the time-shifting property of Laplace Transform, shifting the signal in time domain  $x(t - t_0)$  corresponds to the \_\_\_\_\_
  - (A) Multiplication by  $e^{-st_0}$  in the time domain
  - (B) Multiplication by  $e^{-st_0}$  in the frequency domain
  - (C) Multiplication by  $e^{st_0}$  in the time domain
  - (D) Multiplication by  $e^{st_0}$  in the frequency domain
- b. The Laplace transform of  $e^{-5t} u(t-1)$  is
  - (A)  $e^{-(5s)}/s+5$
  - (B)  $e^{-s}/s+5$
  - (C)  $e^{-(s+5)}/s+5$
  - (D)  $e^{-(5s+1)}/s+5$
- c. The initial value for the function  $x(t) = 4-2e^{3t}$  is
  - (A) 0
  - (B) 2
  - (C) 1
  - (D)  $\infty$
- d. Which operation is likely to get executed or performed by Millman's theorem in terms of converting the voltage or current sources into a single equivalent voltage or current source?
  - (A) Subtraction
  - (B) Combination
  - (C) Differentiation
  - (D) Integration
- e. Superposition theorem is not applicable in
  - (A) voltage responses
  - (B) power responses
  - (C) current responses
  - (D) All of these
- f. A constant current source of 5mA with shunted internal resistance of 500 $\Omega$  is equivalent to a voltage source of
  - (A) 2.5 volts in parallel with 500  $\Omega$
  - (B) 5 volts in series with 500  $\Omega$
  - (C) 2.5 volts in series with 500  $\Omega$
  - (D) 25 volts in series with 500  $\Omega$

- g. Which among the following is regarded as short circuit forward transfer admittance?  
 (A)  $Y_{11}$  (B)  $Y_{12}$   
 (C)  $Y_{22}$  (D)  $Y_{21}$
- h. If the two ports are connected in cascade configuration, then which arithmetic operation should be performed between the individual transmission parameters in order to determine overall transmission parameters?  
 (A) addition (B) subtraction  
 (C) multiplication (D) division
- i. A two-port network is reciprocal if and only if  
 (A)  $AD - BC = 1$  (B)  $Z_{11} = Z_{22}$   
 (C)  $Y_{12} = Y_{21}$  (D)  $h_{12} = h_{21}$
- j. The dynamic impedance  $Z_T$  of a parallel resonance circuit is given by  
 (A)  $L / RC$  (B)  $LRC$   
 (C)  $R / LC$  (D)  $C / LR$

**Answer any FIVE Questions out of EIGHT Questions.  
 Each question carries 16 marks.**

- Q.2** a. Find the inverse Laplace transform of the following function:  
 $F(s) = (S+4) / (2S^2+5S+3)$  (8)
- b. In the circuit shown in Fig. 1, the switch K is moved from position 1 to position 2 at a time  $t=0$ , the steady state current having previously established in the circuit. Find  $i(t)$  after switching. (8)

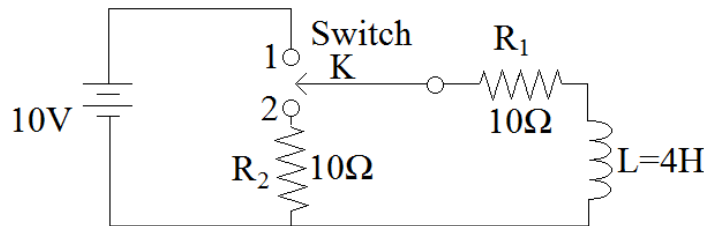


Fig.1

- Q.3** a. Apply the superposition theorem to the network shown in Fig. 2 and obtain the current in the  $(3+j4)$  ohm impedance (8)

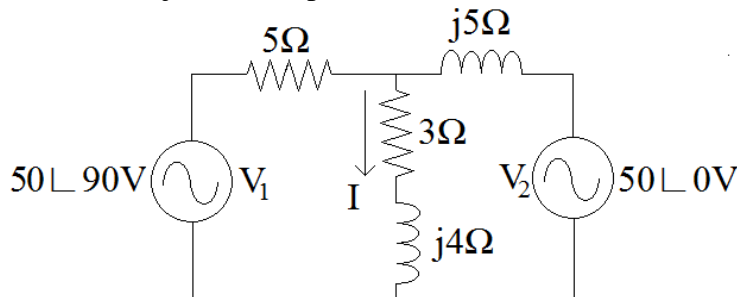


Fig.2

- b. State and prove Maximum Power Transfer Theorem. (2+6)

Code: DE107

Subject: NETWORKS AND TRANSMISSION LINES

- Q.4** a. Find the Z and Y parameters of a symmetrical T-network having  $200\Omega$ ,  $200\Omega$  and  $500\Omega$  resistances. (4+4)
- b. Derive the condition of reciprocity and symmetry in ABCD parameters. (4+4)
- Q 5** a. A resistor and capacitor are in series with a variable inductor when the circuit is connected to  $220V$ ,  $50Hz$  supply. The maximum current obtained by varying inductance is  $0.314A$ . The voltage across the capacitor is  $300V$ . Find the circuit values in this condition. (2+3+3)
- b. Find the value of 'L' for which the circuit shown in Fig. 3 is resonant at a frequency of  $\omega=5000$  rad/sec. (8)

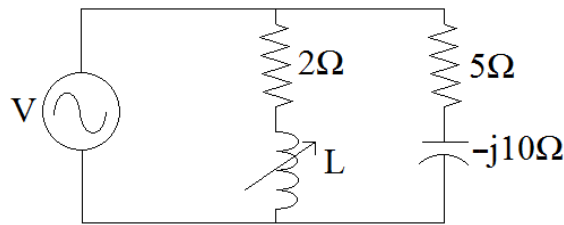


Fig.3

- Q.6** a. A generator of  $1$  Volt,  $1000$  Hz, supplies power to  $1000km$  long open wire line terminated in  $Z_o$  (characteristic impedance) and having following parameters:  $R=10.4$  ohms,  $L=0.0037H$ ,  $G=0.8$  micromhos,  $C=0.00835mf$ . Calculate the characteristic impedance, propagation constant and phase velocity. (3+3+2)
- b. Prove that a line of a finite length and terminated by its characteristic impedance  $Z_o$  is equivalent to a line of an infinite length. (8)
- Q.7** a. Draw and explain the voltage and current distribution along an open circuited and a short-circuited line. (4+4)
- b. A certain low loss line has a characteristic impedance of  $400\Omega$ . Determine the standing wave ratio with the following receiving and impedances. (4+4)
- (i)  $Z_R = 70 + j0 \Omega$
- (ii)  $Z_R = 650 + j475 \Omega$
- Q.8** a. Define Voltage Standing Wave ratio. Derive the relationship between VSWR and reflection coefficient. (3+5)
- b. A UHF lossless transmission line working at  $1GHz$  is connected to an unmatched line producing a voltage reflection coefficient of  $0.5 \angle 30^\circ$ . Calculate after deriving necessary relations the length and the position of the stub to match the line (8)
- Q.9** a. Design a Composite filter (H.P.) to operate into a load of  $600$  ohms and have a cut-off frequency of  $1.2$  kHz. The filter is to have one constant-K section, one m-derived section with  $f_\infty = 1.1$  kHz and suitable terminating half section. (3+3+2)
- b. What is an Attenuator? Derive the design equations for a Symmetrical T-type Attenuator. (2+6)