

**DiplETE – ET (Current Scheme)**

Time: 3 Hours

**June 2018**

Max. Marks: 100

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.


**Q.1 Choose the correct or the best alternative in the following: (2×10)**

- a. Transmission will be distortionless if  
 (A)  $LG = CR$  (B)  $LG = 1/CR$   
 (C)  $LC = GR$  (D)  $LR = GC$
- b. The Laplace transform of  $e^{-at}u(t)$  is  
 (A)  $\frac{s}{s+a}$  (B)  $\frac{s}{s-a}$   
 (C)  $\frac{1}{s+a}$  (D)  $\frac{1}{s-a}$
- c. For the symmetrical two-port network  $Z_1 = 30\Omega$  and  $Z_2 = 10\Omega$ , then the values of A and D  
 (A)  $A=1/4$   $D=4$  (B)  $A=4$   $D=1/4$   
 (C)  $A=1/4$   $D=1/4$  (D)  $A=4$   $D=4$
- d. A Series RLC circuit resonates at 3MHz and has a 3dB bandwidth of 10kHz. The Q of the circuit at resonance is  
 (A) 300 (B) 30  
 (C)  $300\sqrt{2}$  (D)  $\frac{300}{\sqrt{2}}$
- e. Which one of the following is a passive element?  
 (A) BJT (B) FET  
 (C) Inductor (D) Op-Amp
- f. In a series resonant circuit, the impedance of the circuit at resonance is:  
 (A) maximum (B) minimum  
 (C) infinite (D) zero

g. A circuit has Thevenin's voltage of 10V, Thevenin's resistance of  $2\Omega$  and load resistance of  $3\Omega$ , then its load voltage is \_\_\_\_\_.

- (A) 3V (B) 5V  
(C) 10 (D) 6V

h. The filter shown below is:

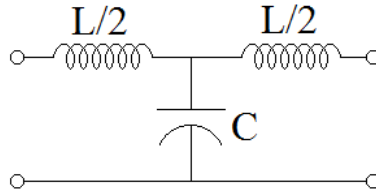

- (A) LPF (B) HPF  
(C) BPF (D) None of these

i. Calculate half power frequencies  $f_1$  &  $f_2$  of a series resonating circuit where the resonance frequency is 150 kHz and the bandwidth is 75 kHz.

- (A)  $f_1=117.5$  kHz &  $f_2=127.5$  kHz (B)  $f_1$  &  $f_2=10$  KHz  
(C)  $f_1=180$  kHz &  $f_2=120$  kHz (D)  $f_1=117.5$  kHz &  $f_2=192.5$  kHz

j. The h parameters  $h_{11}$  and  $h_{21}$  are obtained

- (A) by shorting output terminals (B) by opening output terminals  
(C) by shorting input terminals (D) by opening input terminals

**Answer any FIVE Questions out of EIGHT Questions.  
Each question carries 16 marks.**

- Q.2** a. A series RLC circuit consists of resistance  $R=25\ \Omega$ , inductance  $L=0.01$ H and Capacitance  $C=0.04\ \mu$ F. Calculate (2+3+3)  
(i) The frequency of resonance  
(ii) If a 10V voltage of frequency equal to the frequency of resonance is applied to this circuit, calculate the values of  $V_L$  and  $V_C$  across L and C.  
(iii) Find the frequencies at which these voltages  $V_L$  and  $V_C$  are maximum

b. Explain in detail different types of network elements. (8)

- Q.3** a. Find the Initial and Final values for the following: (4+4)

$$X(s) = \frac{s+4}{s^2+3s+5}$$

b. Discuss the advantages of Laplace Transform method over classical method. (4)

c. Find the convolution integral when  $f_1(t) = e^{-at}u(t)$  and  $f_2(t) = t u(t)$ , using Laplace transform. (4)

- Q.4** a. Determine the current through the resistor of  $2\Omega$  connected across AB for the network as shown in Fig.1 using Thevenin's theorem. (8)

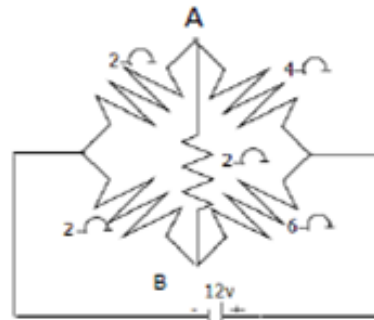


Fig.1

- b. State and prove Thevenin's theorem. (8)
- Q.5** a. Find out the Z parameters and hence the ABCD parameters of the network shown in Fig.2. Check if the network is symmetrical or reciprocal. (10)

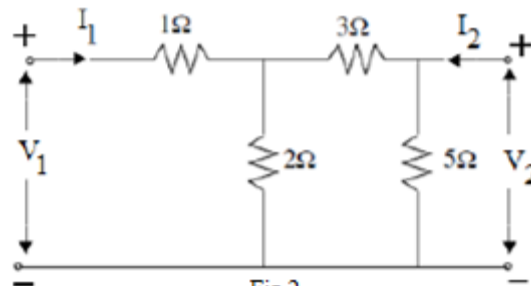


Fig.2

- b. Derive the equations for the elements of an m derived T &  $\pi$  sections. (6)
- Q.6** a. Derive the relationship between the resonance frequency  $f_n$  and half power frequencies  $f_1$  and  $f_2$  in series resonant circuit. (8)
- b. The primary constants of a line per loop km are  $R = 196 \Omega$ ;  $C = 0.09 \mu\text{F}$ ;  $L = 7.1\text{mH}$  and leakage conductance is negligible. Calculate the characteristic impedance and the propagation constant at angular frequency of 5000 radians/sec. (8)
- Q.7** a. Define Frequency and Delay distortions in a transmission line. Explain the methods to minimize the distortions in a transmission line. (3+5)
- b. Explain primary constants of a transmission line and draw the equivalent circuit of transmission line using these constants. (8)
- Q.8** a. What is stub? Explain the different type of stub matching used in transmission lines. (8)
- b. Write short notes on the following: (4x2)
- (i) Quarter wave short circuit line      (ii) Half wave open circuited line
- Q.9** a. Design a Constant-K Low pass filter to have a cut-off frequency of 2kHz and terminating impedance of  $600\Omega$ . Design for both T and  $\pi$  sections. (8)
- b. Write short notes on: (4+4)
- (i) Constant-K Low-pass filter and its approximation/design
- (ii) Symmetrical Lattice attenuator