

**DiplETE – ET (Current & New Scheme)**

Time: 3 Hours

**June 2018**

Max. Marks: 100

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

- a. Which triggering is the most reliable?  
 (A) Thermal triggering (B)  $dV / dt$  triggering  
 (C) Forward voltage triggering (D) Gate triggering
- b. An AC Voltage Controller is used for \_\_\_\_\_  
 (A) induction heating  
 (B) high voltage DC transmission  
 (C) speed control of induction motors  
 (D) speed control of DC motors
- c. Switching frequency of a Chopper is given by \_\_\_\_\_  
 (A)  $1 / TON + TOFF$  (B)  $TOFF / TON$   
 (C)  $TON / TOFF$  (D)  $TON + TOFF$
- d. If the frequency of output voltage of a CSI is  $f$  Hz, then frequency of input voltage to CSI is \_\_\_\_\_  
 (A)  $f$  (B)  $f/2$   
 (C)  $3f$  (D)  $2f$
- e. A single phase semi converter is feeding highly inductive load and has a freewheeling diode across the load. The wave shapes of output voltage and output current \_\_\_\_\_  
 (A) may be similar or dissimilar  
 (B) are not similar  
 (C) are similar only if firing angle is zero  
 (D) are similar

Code: DE71/DE110

Subject: POWER ELECTRONICS

- f. A single phase full bridge inverter can operate in load commutation mode, in case load consists of:
- (A) R-L-C under damped                      (B) R-C ckt  
(C) R-L-C critically damped                (D) R-L-C over damped
- g. A UJT contains\_\_\_\_\_.
- (A) three pn junction                      (B) two pn junction  
(C) one pn junction                        (D) four pn junction
- h. A Cycloconverter can be\_\_\_\_\_.
- (A) step down                                (B) step up  
(C) Neither (A) nor (B)                    (D) Both (A) and (B)
- i. UJT is a\_\_\_\_\_
- (A) two-terminal two-junction semiconductor device.  
(B) three-terminal two-junction semiconductor device.  
(C) three-terminal one-junction semiconductor device.  
(D) two-terminal one-junction semiconductor device.
- j. The \_\_\_\_\_ is a commonly used device in power electronics.
- (A) PIN Diode                                (B) UJT  
(C) PV Cell                                    (D) SCR

---

**Answer any FIVE Questions out of Eight Questions.**  
**Each question carries 16 marks.**

---

- Q.2** a. What is power loss in an ideal switch? Explain the conduction losses in a bipolar junction transistor with the help of circuit diagram. (8)
- b. What is the basic difference between a PN junction power diode and an ordinary PN junction diode? Discuss various principal ratings for power diodes. (8)
- Q.3** a. Give classification of power transistors. Explain the three operating regions of BJT and draw its output characteristics. (8)
- b. Explain with the help of suitable diagram, the construction and working principle of UJT. Also site few examples where UJT is used. (8)
- Q.4** a. What is commutation? What are the different types of communication? Classify the types of communication techniques by which the SCR can be turned off. (8)
- b. List out the types of thyristors and explain briefly the operation of Fast-Switching thyristor. (8)

Code: DE71/DE110

Subject: POWER ELECTRONICS

- Q.5** a. Explain the circuit diagram and output waveforms of Single Phase, Full Wave, fully Controlled Bridge Rectifier with Resistive load. (8)
- b. Explain the working principle of single-phase dual converter with neat circuit diagram. (8)
- Q.6** a. A three-phase half-wave controlled rectifier, connected to a three-phase, 280 V, 60 Hz AC source, supplies power to a  $10 \Omega$  resistive load. If the delay angle is  $20^\circ$ . Find  
(i) maximum output current  
(ii) average output voltage  
(iii) average output current  
(iv) SCR average current (2×4)
- b. Explain the working of three phase half-wave controlled rectifier with an inductive load and a Freewheeling diode. Draw relevant circuit diagram and waveforms. (8)
- Q.7** a. What is a DC Chopper? Explain the operating principle of dc chopper with the help of suitable diagram and waveforms. What are its various industrial applications? (8)
- b. What is Step-Down chopper? Draw its circuit diagram and relevant waveforms to explain its operation for the ON state and OFF state. (8)
- Q.8** a. The single phase half-bridge inverter has resistive load of  $R=2.4\Omega$ , and the dc source voltage  $V_s=48V$ . Determine :  
(i) The RMS voltage at the fundamental frequency  $V_1$ .  
(ii) The output power  $P_0$ .  
(iii) Peak thyristor current  
(iv) Peak reverse blocking voltage  $V_{BR}$  of each thyristor. (2×4)
- b. Draw the circuit diagram of single-phase full-bridge Voltage Source Inverter (VSI) with R-L load and briefly explain its working showing relevant waveforms. (8)
- Q.9** a. What are solid state relays? How these are different from electromagnetic relays? Explain solid state relays by giving suitable circuit diagrams. (8)
- b. What is a Cycloconverter? What are the advantages and disadvantages of Cycloconverters? What are its industrial applications? (8)