

AMIETE – ET/CS/IT (Current & New Scheme)

Time: 3 Hours

June 2019

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions, answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.


Q.1 Choose the correct or the best alternative in the following: (2×10)

- a. What kind of diode is formed by joining a doped semiconductor region with a metal?
 (A) Tunnel (B) Laser
 (C) Schottky (D) LED
- b. In high-frequency response of RC coupled amplifier bypass capacitor acts as _____ and coupling capacitor as _____.
 (A) Open, Open (B) Short, Open
 (C) Open, Short (D) Short, Short
- c. Complex microprocessor chips are categorized under
 (A) SSI (B) MSI
 (C) LSI (D) VLSI
- d. Depending upon whether the voltage or current is fed back either in series or in parallel, there are _____ types of feedback connection(s).
 (A) One (B) Two
 (C) Three (D) None of these
- e. The Quality Factor (Q) of Tuned Amplifier is
 (A) $\frac{\omega_0}{RC}$ (B) $\omega_0 RC$
 (C) $\frac{\omega_0}{RLC}$ (D) $\omega_0 RLC$
- f. Maximum power dissipation $P_{D(max)}$ of a BJT is
 (A) $V_{CE} I_C$ (B) $V_{BE} I_B + V_{CE} I_C$
 (C) $V_{BE} I_B$ (D) $V_{BE} I_E + V_{CE} I_C$
- g. A germanium diode carries a current of 10 mA when a forward bias of 0.2 V is applied. The reverse saturation current (I_S) is
 (A) 100 mA (B) 100 μ A
 (C) 3.355 mA (D) 3.355 μ A


- h. A BJT is a:
 (A) current controlled & bipolar device
 (B) voltage controlled & bipolar device
 (C) current controlled & unipolar device
 (D) voltage controlled & unipolar device
- i. In common base (CB) configuration of BJT which relation(s) is valid
 (A) $\alpha = \frac{\beta}{1+\beta}$ (B) $i_b = \frac{i_e}{1+\beta}$
 (C) $i_c = \alpha i_e$ (D) All of these
- j. Zener diode is
 (A) Heavily doped (B) lightly doped
 (C) Moderately doped (D) Undoped

Answer any FIVE Questions out of EIGHT Questions
Each question carries 16 marks

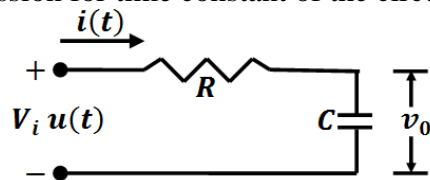- Q.2** a. Deduce the frequency criterion of RLC parallel circuit for the generation of Resonance. (6)
- b. Consider the RC series circuit of Figure below which is excited by step of magnitude V_i , that is $V_i u(t)$ and the output v_o is taken across the capacitor C. Derive the expression for time constant of the circuit. (4)



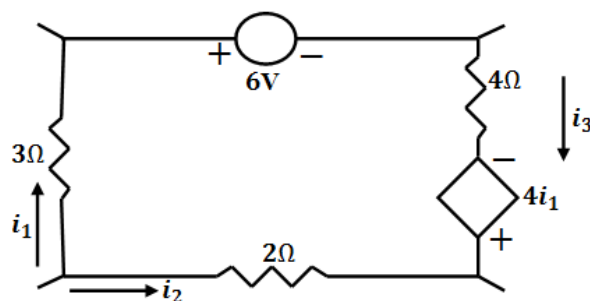
- c. Consider the loop of Figure below which forms parts of an electric circuit. Find i_3 , given $i_1 = 2A$, $i_2 = 4A$ (6)



- Q.3** a. Explain the formation of P-type Semiconductor. (3)
- b. Compare Zener Diode and PN junction Diode. (5)
- c. Calculate the ripple factor of a full-wave rectifier with a 120mF capacitor connected to a load of 60mA. Assume frequency of ac source = 50Hz. (8)


Q.4 a. Explain construction, operation and characteristics of JFET. (8)

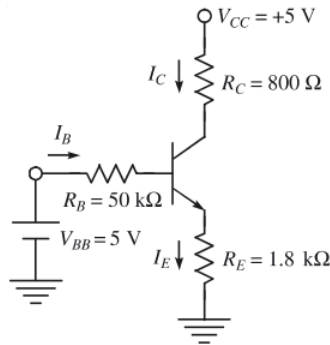b. Consider the transistor ($\beta = 50$) circuit of Figure given below which has a resistance included between emitter and ground. Show that the transistor is operating in active mode. Calculate I_C , I_E and I_B . (8)



Q.5 a. Draw and explain the construction, operation and drain characteristic of N-channel JFET. (8)

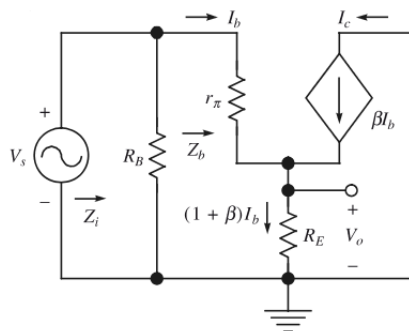
b. The emitter-follower circuit of Figure below has $\beta = 98$, $r_{\pi} = 1.275\text{k}\Omega$, $R_B = 220\text{k}\Omega$, $R_E = 3.3\text{k}\Omega$ and $V_{CC} = +12\text{V}$. Calculate voltage gain and input & output impedances. (8)



Q.6 a. Explain principle of operation of tuned amplifier. (7)

b. What are the reasons of frequency distortion during the amplification process? (3)

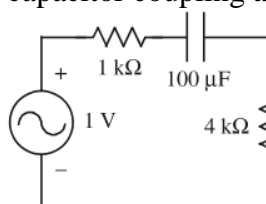c. Figure below shows a capacitor coupling a signal from a generator to a load.



- (i) What is the maximum current? (2)
- (ii) What is the critical frequency? (2)
- (iii) The lowest frequency at which the capacitor begins to act as a short-circuit? (2)

- Q.7** a. Draw and explain working of Class C power amplifier. (8)
- b. A transistor supplies 2W for a $5K\Omega$ load. The zero-signal dc collector current is 35mA and it rises to 49mA when the signal is applied. Determine the percent second harmonic distortion. (8)
- Q.8** a. Sketch the block diagram of a current series feedback amplifier and derive relation for its closed loop gain. (8)
- b. A feedback amplifier comprises two amplifying blocks in tandem; each block having a gain of 100. What should be the gain of the feedback block in order for overall gain to be 100? If the gain of each amplifier block reduces to 50% due to parameter variations, what is the % change in the gain of the complete feedback unit? (8)
- Q.9** a. Explain the various steps involved in fabrication of Monolithic Diodes. (8)
- b. A thin-film capacitor has a capacitance of $0.4 \text{ pF}/(\mu\text{m})^2$. The thickness of the film is 400\AA . Calculate the relative dielectric constant of SiO_2 layer. (8)