

DiplETE – ET (Current Scheme)

Time: 3 Hours

June 2019

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

- a. If $A^2 - BC = 1$, the circuit is
 (A) Balanced (B) Reciprocal
 (C) symmetrical and reciprocal (D) Reciprocal and Bilateral
- b. h_{21} , in terms of z-parameters can be expressed as
 (A) $\Delta z/z_{22}$ (B) $\Delta z/z_{12}$
 (C) $z_{12}/\Delta z$ (D) $-z_{21}/z_{22}$
- c. In RLC circuit $R = 45\Omega$ $L=0.06H$ and $C=0.6\mu F$, the power factor will be
 (A) Unity (B) Zero
 (C) Lagging (D) Leading
- d. In a series resonant circuit, the impedance of the circuit will be
 (A) Minimum (B) Maximum
 (C) Infinite (D) Zero
- e. $\frac{1}{s+a}$ is the Laplace transform of
 (A) e^{at} (B) e^{-at}
 (C) $\frac{1}{e^{-at}}$ (D) None of these
- f. A BPF may be obtained by using a high pass filter followed by a
 (A) LPF (B) HPF
 (C) RC filter (D) None of these
- g. Distortion-less condition of a transmission line is given by
 (A) $Z_0 = \sqrt{L/C}$ (B) $R/G = L/C$
 (C) $R \cdot G = L \cdot C$ (D) $Y = \sqrt{\frac{1}{LC}}$

- h. A Smith chart is used in solving problems in
 (A) Radiowave propagation (B) Transmission lines
 (C) Aerial system (D) any where in the line
- i. The characteristic impedance of a transmission line is
 (A) Real (B) Inductive
 (C) Capacitive (D) Complex
- j. Propagation constant parameter is used in
 (A) symmetrical network (B) asymmetrical networks
 (C) Both types as in (A) and (B) (D) Inverse networks

**Answer any FIVE Questions out of EIGHT Questions.
 Each question carries 16 marks.**

- Q.2** a. Explain π -T Equivalent theorem with the help of suitable example. (8)
- b. Find the current following through 12Ω resistor as shown in Fig.1 using Thevenin's Theorem. (8)

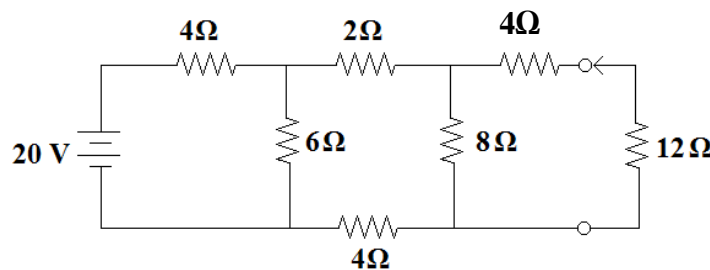


Figure 1

- Q.3** a. Derive the Laplace transform of unit impulse function. (8)
- b. Voltage $V(s) = \frac{1 + 2e^{-s} - e^{-2s}}{s^2}$ is applied as input to a series RL circuit with $R=3\Omega$ and $L=3H$. Calculate $i(t)$ using Laplace transform through the circuit. [Assume $i(0^+)=0$] (8)
- Q.4** a. Explain the characteristic curve of a parallel R-L-C circuit. (8)
- b. A series RLC circuit has $R=2\Omega$ and $X_C=5\Omega$ and inductance is impure having its resistance 3Ω and inductive reactance of 1Ω . Find the input impedance and circuit current. Also calculate the frequency of resonance. Supply is $100V, 50$ Hz. (8)
- Q.5** a. Explain the term characteristic impedance and propagation constant of a transmission line. (8)
- b. A lossless transmission line has a shunt capacitance of 100 pF/m and a series inductance of $4\mu H/m$. What is its characteristic impedance? (8)

- Q.6** a. Explain significance of Poles and Zeros in network functions. (8)
- b. The Z-parametrs of a two port are: (8)
 $Z_{11} = 10\Omega$, $Z_{22} = 20\Omega$, $Z_{12} = Z_{21} = 5\Omega$
Find the ABCD parameters.
- Q.7** a. Determine the input impedance of a lossless short circuited line. (8)
- b. Explain the term Quarter wave transformer in transmission lines. (8)
- Q.8** a. Draw T & π sections of a constant K high pass filter. Derive an expression for cut-off frequency. (4+4)
- b. Design a symmetrical bridge T-attenuator with attenuation of 40 dB and design impedance of 600 Ω . (8)
- Q.9** a. Define: (2×4)
(i) Bilateral and unilateral elements
(ii) Linear and nonlinear elements
(iii) Resistance parameter
(iv) Ideal voltage source
- b. What is Mutual Induction? Explain working principle of two mutually coupled Inductor. (8)