

DiplETE – ET/CS (Current & New Scheme)

Time: 3 Hours

June 2019

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

- a. Which of the following number systems is not a positional number system?
 (A) Roman (B) Decimal
 (C) Hexadecimal (D) Binary
- b. The following code(s) is (are) not a BCD code
 (A) Gray code (B) XS-3 code
 (C) 8421 code (D) All of these
- c. How many NOR gates are required to obtain AND operation?
 (A) 2 (B) 3
 (C) 4 (D) 5
- d. Which of the following gates cannot be used as an inverter?
 (A) NAND (B) NOR
 (C) AND (D) X-NOR
- e. An 8-square is called
 (A) A pair (B) A quad
 (C) A cube (D) An octet
- f. A multiplexer is also known as
 (A) A data accumulator (B) A data restorer
 (C) A data selector (D) A data distributor
- g. A flip-flop can store
 (A) One bit of data (B) Two bits of data
 (C) Three bits of data (D) Any number of bits of data
- h. The toggle mode for a J-K flip-flop is
 (A) J=0, K=0 (B) J=1, K=1
 (C) J=0, K=1 (D) J=1, K=0

- i. The characteristics equation of a D flip-flop is
 (A) $Q_{n+1} = D$ (B) $Q_{n+1} = Q_n$
 (C) $Q_{n+1} = 1$ (D) $Q_{n+1} = D + Q_n$
- j. A sequential circuit with ten states will have _____ flip-flops
 (A) 10 (B) 5
 (C) 3 (D) 4

**Answer any FIVE Questions out of EIGHT Questions.
 Each question carries 16 marks.**

- Q.2** a. Explain the operation of digital computer with block diagram (8)
 b. Perform the following conversions: (4+4)
 (i) $(378.98)_{10}$ to Octal (ii) $(2598.675)_{10}$ to Hexadecimal
- Q.3** a. Draw the logic circuit for the Boolean expression $F = X'Y' + XY + X'Y$ (4)
 b. Write the truth table for Exclusive OR gate with logic diagram. (3)
 c. Simplify the following expressions and implement them with NAND gate circuits.
 $F = AB' + ABD + ABD' + A'C'D' + A'BC'$ (9)
- Q.4** a. Distinguish between combinational and sequential logic circuits. (8)
 b. Draw the circuit diagram of master-slave JK Flip -Flop and explain its Operation with the help of truth table. (8)
- Q.5** a. Design a combinational circuit that accepts a 3-bit BCD number and generates an output binary number equal to the square of the input number. (8)
 b. Explain the working of BCD adder with logic diagram. (8)
- Q.6** a. Explain in details the operation of MOD-6 Johnson counter, with logic diagram and state diagram. (8)
 b. Design a MOD-10 Asynchronous counter using Flip-Flops. (8)
- Q.7** a. Design a 4 x 1 Multiplexer, and list any four of its applications. (8)
 b. Design a 4-bit Gray-to-Binary Code converter. (8)
- Q.8** a. Design a MOD-3 Synchronous Counter and draw its logic diagram. (8)
 b. Draw the logic diagram for 4-bit Serial Input and Serial Output Shift Register and explain its working with timing waveform. (8)
- Q.9** a. Define the following terms with respect to memory devices: (8)
 (i) Access time (ii) Address (iii) Read only memory (iv) Volatile memory
 b. What is RAM? What are its various types and explain each type.? (8)