

DiplETE – ET (Current & New Scheme)

Time: 3 Hours

June 2019

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

- Q.1 Choose the correct or the best alternative in the following: (2×10)**
- a. Power diode is generally constructed from
 (A) Silicon (B) Germanium
 (C) Both (D) None of these
- b. Power MOSFET IS
 (A) Bipolar (B) Voltage controlled
 (C) Unipolar (D) Both (B) & (C)
- c. The minimum value of current required to maintain conduction in a thyristor is called the
 (A) Latching current (B) Holding current
 (C) Gate current (D) Breaking voltage
- d. A 3-phase to 3-phase cycloconverter is not popular because
 (A) It requires 18 thyristors (B) Complicated firing circuit
 (C) Both (A) & (B) (D) None of these
- e. A step - up chopper is connected to 100 V dc supply. For a duty cycle of 0.5 the output voltage in volts will be
 (A) 100/1.5 (B) 100/0.5
 (C) 100 (D) 200
- f. Feedback diodes are required in inverters which are
 (A) CSI (B) VSI
 (C) Both (D) None of these
- g. Six SCRs in a 3-phase full rectifier are fired at an interval of____.
 (A) 180° (B) 120°
 (C) 60° (D) 90°

Code: DE71/DE110

Subject: POWER ELECTRONICS

- h. SCR's di/dt protection is achieved by connecting SCR in _____ with _____.
 (A) Parallel, RC (B) Parallel, L
 (C) Series, L (D) Series, RC
- i. An AC voltage of 70.7 volts is applied to a single-phase bridge controlled rectifier. The PIV rating of each thyristor should be
 (A) 70.7 V (B) 100 V
 (C) 141.4 V (D) 35.35 V
- j. In case of a inverter, PWM is used to control
 (A) Harmonic (B) Voltage
 (C) Current (D) Both (A) & (B)

Answer any FIVE Questions out of EIGHT Questions.
Each question carries 16 marks.

- Q.2** a. What are the various types of power electronics circuits? Explain briefly with their area of applications. 8
- b. Explain conduction loss w.r.t. a transistor. 4
- c. Explain the V-I characteristics of a Power Diode. 4
- Q.3** a. Draw symbol & V-I characteristics of (i) IGBT and (ii) N-Channel POWER MOSFET. 8
- b. How a thyristor can be triggered using a UJT? 8
- Q.4** a. In context of an SCR, explain the following:
 (i) Commutation
 (ii) Line commutation
 (iii) Commutation by resonance
 (iv) Turn-off time. 8
- b. Explain in brief (i) GTO and (ii) MCT 8
- Q.5** a. Draw the circuit of a half wave controlled rectifier with an inductive load and a FWD. Also, explain its working in detail. 8
- b. Explain with the help of waveforms the operation of a full-wave center tap rectifier with RL load firing angle of 135° . 8
- Q.6** a. A three-phase half wave controlled rectifier is connected to a 220 V source. If the delay angle is 45° and the load resistance $R = 10 \Omega$, determine:
 (i) the average output voltage
 (ii) average SCR current
 (iii) average power dissipation in the SCR
 (iv) maximum reverse voltage rating. 8

Code: DE71/DE110**Subject: POWER ELECTRONICS**

- b. Explain with the help of circuit diagram, the working principle of three phase full wave half controlled bridge rectifier. **8**
- Q.7** a. What is step-up chopper? Draw its circuit diagram and explain its operation for the on state and off state. **10**
- b. How the average output voltage of a DC chopper can be varied? **6**
- Q.8** a. What is an inverter? Why PWM is used in an inverter circuit? List out its various industrial applications. **6**
- b. Draw the circuit of single-phase Current Source Bridge Inverter and explain its working with the help of load current waveform. **10**
- Q.9** a. For the application of heating loads, choose Integral Cycle Control or Phase Control and Justify the same. **4**
- b. What is cycloconverter? State its applications. **4**
- c. Explain briefly: (i) Solid State Relay and (ii) Static AC switch using TRIAC. **8**