

**AMIETE – ET (OLD SCHEME)**

Time: 3 Hours

**JUNE 2012**

Max. Marks: 100

*PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.*

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.


**Q.1 Choose the correct or the best alternative in the following: (2×10)**

- a. The main advantage of using a three op-amp instrumentation amplifier over a single op-amp differential amplifier lies in
- (A) higher value of CMRR  
(B) lower noise figure  
(C) Elimination of the need for accurate matching of resistors  
(D) Simplicity of gain adjustment
- b. A major advantage of active filters is that they can be realized without using
- (A) op-amps (B) inductors  
(C) resistors (D) capacitor
- c. The number of comparisons carried out in a four bit flash type A/D converter is
- (A) 16 (B) 15  
(C) 4 (D) 3
- d. Logarithmic amplifier are used in
- (A) Adders (B) Dividers  
(C) Multipliers (D) All of the above
- e. A TTL circuit with totem pole output has
- (A) Higher output impedance (B) Low output impedance  
(C) Very high output impedance (D) Any of the above

- f. Which of the following circuit can be used as parallel to series converter?
- (A) Digital converter (B) Decoder  
(C) De-multiplexer (D) Multiplexer
- g. Which of the following flip-flop is used as latch?
- (A) JKFF (B) DFF  
(C) SRFF (D) TFF
- h. If an NMOS acting as a switch in depletion mode then
- (A) The device is cut-off for  $V_{GS}=0$   
(B) The device is cut-off for low  $V_{DS}$   
(C) The device is cut-off for large negative  $V_{GS}$   
(D) The device is in saturation high values of  $V_{DS}$
- i. The internal structure of PLA is similar to
- (A) RAM (B) ROM  
(C) Both ROM and RAM (D) Neither RAM nor ROM
- j. RAM can be expanded to
- (A) Increase word size (B) Increase word number  
(C) Both (A) and (B) (D) None of the above

Answer any FIVE Questions out of EIGHT Questions.  
Each question carries 16 marks.

 - Q.2 a. Draw and explain the architecture of an NMOS op-amp. Give three reasons as why this architecture is employed. (8)
- b. For the circuit shown in Fig. 1, find the differential voltage gain  $A=V_o/(V_1-V_2)$ . (8)



**Q.3** a. Find the Chebyshev transfer function for the low pass filter that meets the specification  
 $f_p=10$  kHz,  $A_{max}=1$  dB,  $f_s=15$  kHz,  $A_{min}=25$  dB, dc gain=1 (8)

b. What are the advantages of switched capacitor filter? Draw the switched-capacitor form of an active BP filter. (8)

**Q.4** a. Draw the block diagram of dual slope A/D converter and explain its operations. (10)

b. Find  $V_0/V_1$  for the op-amp circuit if  $n \neq 1$  in Fig. 2.

 


Fig. 2 (6)

**Q.5** a. Explain how an FET can be used as a switch (8)

b. Explain the working of (i) CMOS NAND gate (ii) CMOS NOR gate. (8)

**Q.6** a. Explain how a BJT act as an inverter. (10)

b. Explain the following:  
 (i) Bipolar logic family and unipolar logic family  
 (ii) Saturated and non saturated logic  
 (iii) Tristate logic (2×3)

**Q.7** a. Simplify the following logic expression using Boolean Algebra:  
 (i)  $F=AB+A(B+C)+B(B+C)$   
 (ii)  $f = \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}D + B\overline{C}D + \overline{A}B + \overline{B}C$  (4×2)

b. Design BCD to Gray code converter using 4:1 mux. (8)

**Q.8** a. Design a synchronous mod-6 counter using JK flip-flop. (10)

b. What are the different forms of triggering in flip-flop? Explain each one with an example. (6)

**Q.9** Write short note on any **TWO**:  
 (i) CCD  
 (ii) PLA  
 (iii) EPROMS (8×2)