

## AMIETE – ET/CS/IT

Time: 3 Hours

**JUNE 2014**

Max. Marks: 100

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE: There are 9 Questions in all.**

- **Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.**
- **The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.**
- **Out of the remaining EIGHT Questions, answer any FIVE Questions. Each question carries 16 marks.**
- **Any required data not explicitly given, may be suitably assumed and stated.**

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

- a. Energy band gap in pure germanium is \_\_\_\_\_
- (A) 1.1eV (B) 0.5eV  
(C) 0.67eV (D) 1eV
- b. In p-type material, the majority carriers and minority carriers are \_\_\_\_\_
- (A) holes, electron (B) holes, neutron  
(C) electron, neutron (D) None of these
- c. Most popular used transistor biasing circuit is \_\_\_\_\_
- (A) fixed bias (B) feedback bias  
(C) potential divider bias (D) None of these
- d. In multistage amplifier \_\_\_\_\_
- (A) Gain increases and BW increases  
(B) Gain decreases and BW increases  
(C) Gain decreases and BW decreases  
(D) Gain increases and BW decreases
- e. The change in output voltage from no load to full load condition is called \_\_\_\_\_
- (A) Rectification (B) Regulation  
(C) Efficiency (D) Filtering
- f. An UJT can be used in the construction of \_\_\_\_\_
- (A) an oscillator (B) an amplifier  
(C) Both (A) & (B) (D) a rectifier
- g. For a SCR, the two transistor analogy holds good when the SCR is in \_\_\_\_\_
- (A) Forward blocking state (B) Condition state  
(C) Both (A) & (B) (D) None of these

h. An amplifier has an open loop gain of 40dB and a bandwidth of 100kHz. Bandwidth need to increase 0.6MHz by providing suitable negative feedback. The amount of negative feedback should be \_\_\_\_\_

- (A) 0.5% (B) 0.05%  
(C) 50% (D) 5%

i. Maximum efficiency of a Class-B push pull amplifier is


- (A) 75% (B) 50%  
(C) 95% (D) 78.5%

j. LSI technology includes \_\_\_\_\_ number of gates on chip

- (A) less than 200 (B) 200-2000  
(C) more than 2000 (D) None of these

**Answer any FIVE Questions out of EIGHT Questions.**  
**Each question carries 16 marks.**

**Q.2** a. For the circuit shown in Fig.1, find the voltage across 2 mho conductance using Nodal analysis (8)

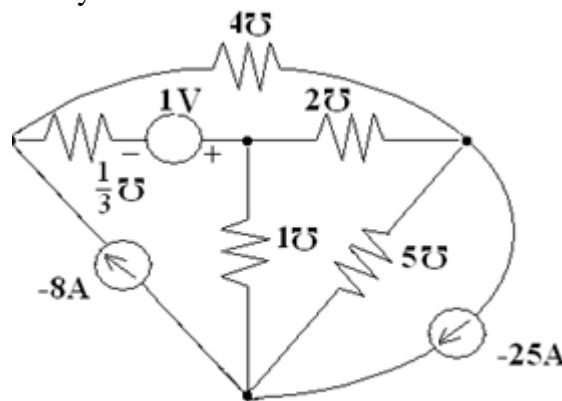

**Fig.1**

b. State and explain the Norton and Reciprocity Theorem with one example of each. (8)

**Q.3** a. A full-wave rectifier with a centre-tapped transformer supplies a dc current of 100mA to a load resistance of  $R=20\Omega$ . The secondary resistance of the transformer is  $1\Omega$ , each diode has a forward resistance of  $0.5\Omega$ . Determine the following:

- (i) RMS value of signal voltage across each half of the secondary.
- (ii) DC power supplied to the load.
- (iii) PIV rating of each diode.
- (iv) AC power input to the rectifier.
- (v) Conversion efficiency.
- (vi) Voltage regulation.

(8)

- b. Compare performance of a halfwave rectifier, a centre tapped full wave rectifier and a bridge type full wave rectifier. (8)

**Q.4** a. Draw and explain the transfer characteristics of FETs. (8)

- b. What are four layer devices? Explain the switching action of Silicon Controlled Rectifier (SCR). (8)

**Q.5** a. Explain the need of biasing in transistor circuit and determine the stability factor of fixed bias circuit. (8)

- b. What is h-parameter model? Draw and explain a BJT h-parameter models. (8)


**Q.6** a. Draw & explain the circuit diagram and frequency response of a Single stage RC-coupled amplifier. (8)

- b. A BJT transistor amplifier stage has  $R_E=R_C=1.5k\Omega$ ,  $R_S=600\Omega$ ,  $R_L=2k\Omega$  and transistor parameter  $\beta=100$  and  $r_\pi=1k\Omega$ . Determine the value of  $C_{C1}$ ,  $C_{C2}$  and  $C_E$  needed to obtain  $f_L=50Hz$  and also

draw

the circuit. (8)

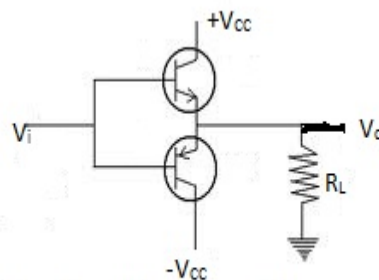**Q.7** a. In the ideal class-B amplifier with complimentary symmetry shown in figure having  $V_{CC}=15V$ ,  $R_L=10\Omega$ . The input is sinusoidal. Determine the maximum signal output power, the corresponding collector dissipation and conversion efficiency. (8)



Class-B amplifier with complimentary symmetry

**Fig.2**

- b. With the help of suitable diagram, explain the following: (8)  
 (i) Class-C power amplifier (ii) Class-AB power amplifier

**Q.8** a. Explain Wein bridge Oscillator. (8)

- b. What are the effect of negative feedback on gain and bandwidth of an amplifier? Explain. (8)

**Q.9** a. Explain photolithography masking and Etching. (6)

- b. What is the width required to fabricate  $5k\Omega$  resistor whose length is  $25\mu m$ . Given  $R_S=200\Omega/square$  (4)

c. Briefly explain the steps involved in IC fabrication.

(6)