

Time: 3 Hours

**JUNE 2014**

Max. Marks: 100

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

- a. To a highly inductive circuit, a moderate value capacitance is added in series. The angle between voltage and current will
- (A) decrease (B) remain same  
(C) increase (D) indeterminist
- b. Kirchoff's first law is used in the formation of
- (A) Loop equation (B) Nodal equation  
(C) Duality (D) Convolution integral
- c. Superposition theorem is not applicable in
- (A) voltage responses (B) current responses  
(C) power responses (D) none of these
- d. The current in circuit changes according to  $i = 2e^{-t}$  Ampere for  $t \geq 0$  and  $i = 0$  for  $t < 0$ . The total charge passes to the circuit in Coulombs is
- (A) 8 (B) 4  
(C) 1 (D) 2
- e. The circuit shown in Fig.1 is

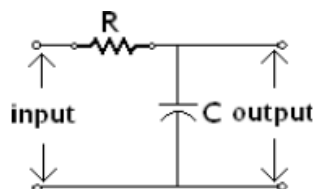


Fig.1

- (A) High pass filter (B) Low pass filter  
(C) All pass filter (D) An attenuator


Code: AE59

Subject: CIRCUIT THEORY & DESIGN


- f. An L-C immittance function  
 (A) has simple poles and zeros in the left half of the s-plane  
 (B) has no zero or pole at the origin or infinity  
 (C) is an odd rational function  
 (D) has all poles on the negative real axis of the s-plane
- g. A network function can be completely specified by  
 (A) Poles, zeros and a scale factor    (B) zeros and a scale factor  
 (C) Poles and zeros    (D) Poles and a scale factor
- h. Laplace transform of a unit impulse function is  
 (A)  $1/s^2$     (B) 1  
 (C)  $1/s$     (D) s
- i. An RLC series circuit is said to be inductive if  
 (A)  $\omega L = 1/\omega C$     (B)  $\omega L < 1/\omega C$   
 (C)  $\omega L = \omega C$     (D)  $\omega L > 1/\omega C$
- j. For a two - port reciprocal network, the three transmission parameters are given as  $A = 4$ ,  $B = 7$  and  $C = 5$ . The value of D is equal to  
 (A) 8    (B) 9  
 (C) 3    (D) 5.8

**Answer any FIVE Questions out of EIGHT Questions.  
 Each question carries 16 marks.**

- Q.2** a. For the circuit shown in Fig.2, determine (i) its graph (ii) its oriented graph (iii) trees. (1+1+2)

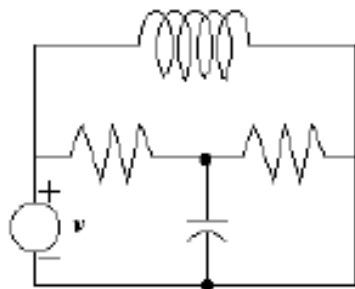

**Fig.2**

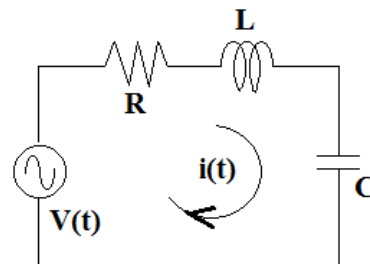

**Fig.3**

- b. Define duality. Obtain dual of network shown in Fig.3. Write integro-differential equation for both. (1+3)
- c. Write various steps involved for loop analysis. Find the power dissipated in the  $4\Omega$  resistor in the circuit shown in Fig.4 using loop analysis. (4+4)

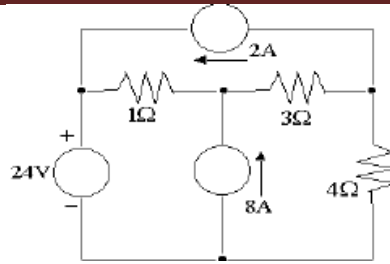


Fig. 4

- Q.3** a. After steady-state current is established in the R-L circuit shown in Fig.5 with Switch S in position 'a' the switch is moved to position 'b' at  $t = 0$ . Find  $i_L(0^+)$  and  $i(t)$  for  $t > 0$ . What will be the value of  $i(t)$  when  $t = 4$  seconds? (8)

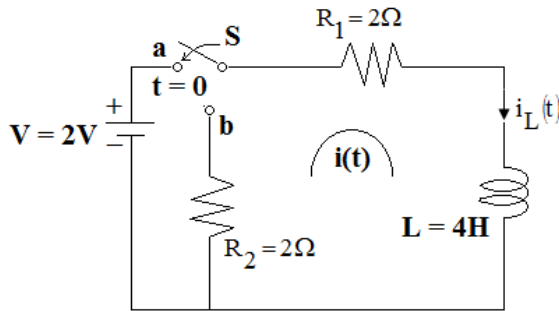


Fig.5


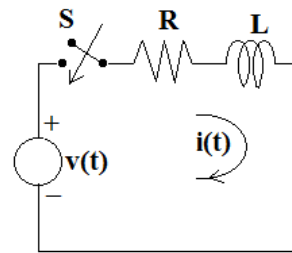


Fig.6

- b. In the given network of Fig.6, the switch S is closed at  $t=0$ . The voltage source follows the law  $v(t) = Ve^{-\alpha t}$ , where  $\alpha$  is a constant. Solve for the current assuming that (i)  $\alpha \neq R/L$  (ii)  $\alpha = R/L$ . (8)
- Q.4** a. At  $t = 0$ , a switch is closed, connecting a voltage source  $V$  to a series RC circuit. Find the expression for current by using method of Laplace transform. Assume capacitor has no initial charge. (8)
- b. State and prove initial value theorem and final value theorem for Laplace transform. Obtain initial value for the function  $F(s) = 2(s+1) / (s^2+2s+5)$  (8)
- Q.5** a. State and prove reciprocity theorem. Write its application. (8)
- b. Obtain the transform impedance representation for a capacitor and an inductor. For initial conditions in the network, how they are transformed? (8)
- Q.6** a. Discuss the time domain behaviour from the pole and zero plot. (10)
- b. Determine whether the polynomial are Hurwitz or not.  
 (i)  $F(s) = s^3 + 2s^2 + s + 2$   
 (ii)  $F(s) = s^4 + s^3 + 2s^2 + 2s + 1 = 0$  (2×3)
- Q.7** a. State the condition of two port network to be reciprocal and symmetrical in terms of  $Z, h, ABCD$  &  $Y$  parameters. (4)
- b. Explain twin-T network. (4)

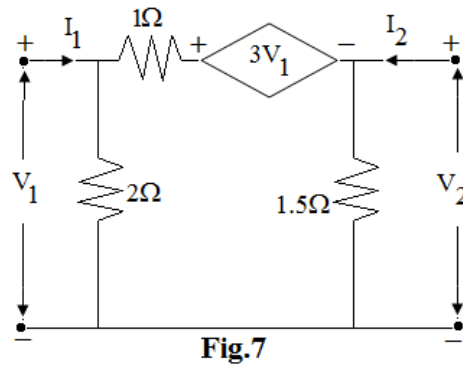- c. For the circuit as shown in Fig.7, find the Y-parameters. (8)



- Q.8** a. Obtain (i) Foster –I form realization and (ii) Cauer –II form realization for  
 $Z(s) = 2(s+1)(s+3) / s(s+2)$  (8)
- b. Synthesize  $Z(s) = (s^2 + 5s + 4) / (s^2 + 5s + 6)$  using partial fraction expansion method. (8)
- Q.9** a. Discuss how the element change in Frequency Transformations used for filter design. (8)
- b. Realise  $H(s) = s / \{s^3 + s^2 + 3s + 1\}$  as a network terminated by  $1\Omega$  resistor. (8)