

**AMIETE – ET (Current & New Scheme)**

Time: 3 Hours

**JUNE 2015**

Max. Marks: 100

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

a. Which of the following is not a passive element?

- (A) Resistance (B) Capacitance  
(C) Inductance (D) Transistor

b. If any network has 'b' branches & 'n' nodes then minimum number of equations required to solve this network are

- (A)  $b - n$  (B)  $b - n - 1$   
(C)  $b - n + 1$  (D)  $2(b - n)$

c. Laplace transform of  $e^{-at} \cos \omega t$  is


- (A)  $\frac{s+a}{(s+a)^2 + \omega^2}$  (B)  $\frac{s}{s^2 + \omega^2}$   
(C)  $\frac{s-a}{(s-a)^2 + \omega^2}$  (D)  $\frac{\omega^2}{(s+a)^2 + \omega^2}$

d. Final value of function  $X(s) = \frac{7s+20}{s(s+5)}$

- (A) 0 (B)  $\infty$   
(C) 4 (D)  $7/5$

e. What is Thevenin's voltage ( $V_{TH}$ ) & Thevenin Resistance ( $R_{TH}$ ) at 'ab' of the network shown in Fig.1?

- (A) 6V,  $4\Omega$   
(B) 10V,  $4\Omega$   
(C) 14V,  $4\Omega$   
(D) 16V,  $4\Omega$

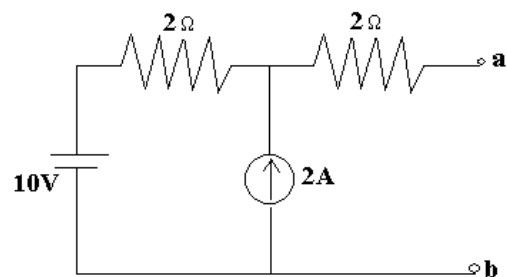

**Fig.1**

f. Z Parameters of network shown in Fig.2 are

- (A)  $Z = \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}$  (B)  $\begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}$   
 (C)  $\begin{bmatrix} R & R \\ R & R \end{bmatrix}$  (D) Does not exist

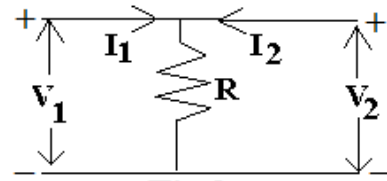


Fig.2

g. What is transfer function of network which has pole – zero plot as shown in Fig.3 is

- (A)  $(s + 1)(s + 2) / s(s^2 + 4)$   
 (B)  $s(s^2 + 4) / (s + 1)(s + 2)(s^2 + 4)$   
 (C)  $s(s + 1)(s + 2) / (s^2 + 4)$   
 (D)  $\frac{s(s + 2)}{(s + 1)(s^2 + 4)}$

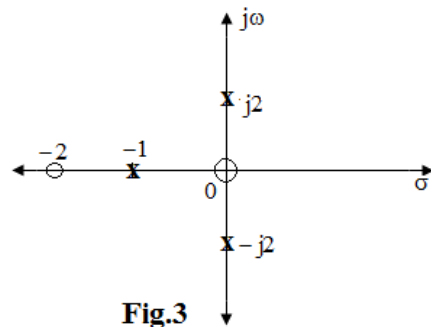


Fig.3

h. Which of the following statement is wrong regarding positive real function,  $\frac{N(s)}{D(s)}$

- (A) All coefficients in N(s) & D(s) must be real & positive  
 (B) D(s) must be Hurwitz Polynomial  
 (C) Residues may be negative  
 (D)  $M_1 M_2 - N_1 N_2 \geq 0$  for all  $\omega$

i. Inverse Laplace transform of  $\frac{1}{(s + 1)(s + 2)}$

- (A)  $\frac{1}{2}(e^{-t} - e^{-2t})$  (B)  $e^{-t} - e^{-2t}$   
 (C)  $e^{-t} + e^{-2t}$  (D)  $e^{-t} + 2e^{-2t}$

j. Which of the following is II order butterworth Polynomial?

- (A)  $s^2 + 1.414s + 1$  (B)  $s^2 + s + 1$   
 (C)  $s^2 + 1.618s + 1$  (D)  $s^2 + 0.636s + 1$

Answer any FIVE Questions out of EIGHT Questions.

Each question carries 16 marks.

Q.2 a. Calculate current 'I' in circuit shown in Fig.4 using Loop analysis. (8)

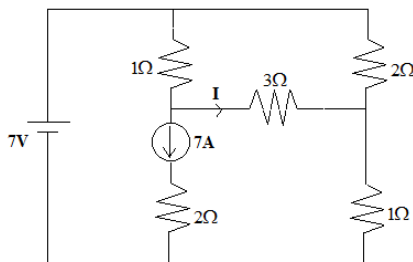


Fig.4

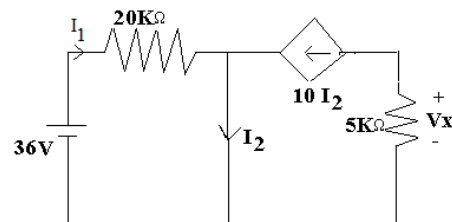


Fig.5

b. Calculate  $I_1, I_2$  and  $V_x$  in the circuit shown in Fig.5. (8)

- Q.3** a. For the circuit as shown in Fig.6 switch S is changed from position 'a' to 'b' at  $t = 0$ . Find values of  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0$ . (8)

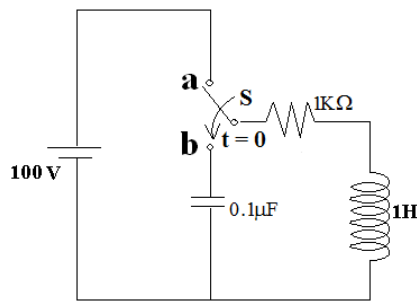


Fig.6

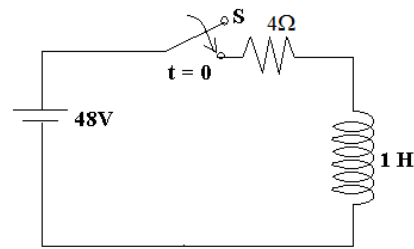


Fig.7

- b. In a series R-C circuit, the value of  $R = 10\Omega$  &  $C = 25 \text{ nF}$ , A sinusoidal voltage of 50 MHz is applied and the maximum voltage across the capacitor is 2.5V, find the maximum voltage across the series combination. (4)
- c. Find the solution of the equation  $\frac{dx}{dt} + 2x = 10$  with initial value  $x(0) = 2$ . (4)
- Q.4** a. Consider R-L series circuit as shown in Fig.7 here  $i(0) = 3\text{A}$ . using Laplace transform find current  $i(t)$  at  $t \geq 0$ . (8)
- b. Find the current  $i(t)$  for the network using Laplace Transform shown in Fig.8. (8)

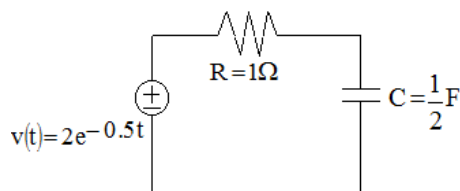


Fig.8

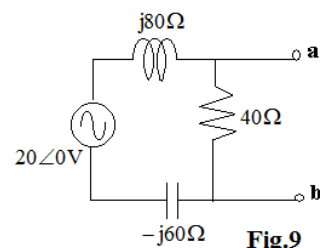


Fig.9

- Q.5** a. Find Norton's equivalent along a, b terminals for the network shown in Fig.9 (8)
- b. Find  $Z(s)$  for the network shown in Fig.10 (8)
- Q.6** a. For the circuit shown in Fig.11 obtain voltage transfer function. (4)
- b. Draw Pole- Zero Plot for  $Z(s) = \frac{s+1}{s^2+2s+2}$  (4)
- c. Test the positive realness of  $F(s) = \frac{2s^2+2s+1}{s^3+2s^2+s+2}$  (8)

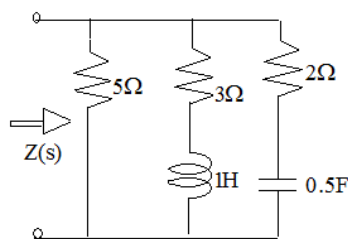


Fig.10

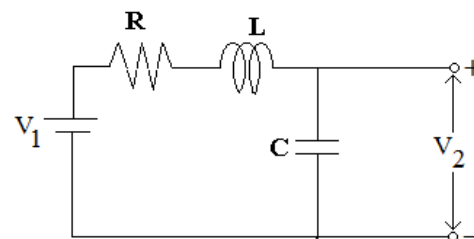


Fig.11

**Q.7** a. Obtain h –parameter for the circuit shown in Fig.12 (4)

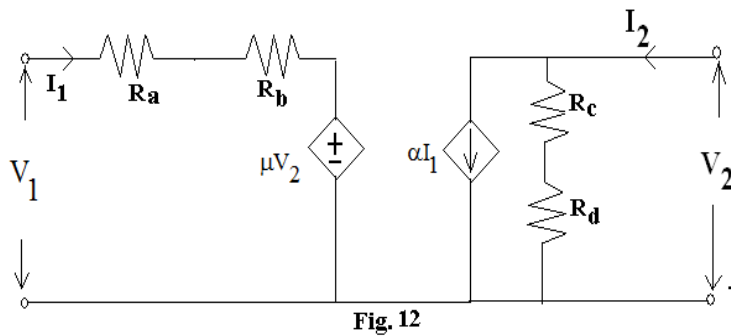


Fig. 12

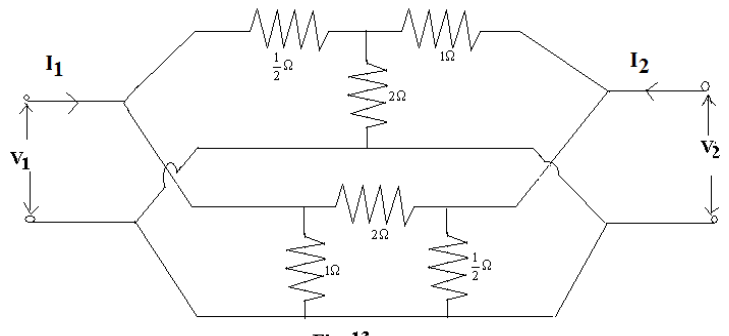


Fig. 13

b. The Y Parameter of the network are  $Y = \begin{bmatrix} 2 & 4 \\ 3 & 1 \end{bmatrix}$ . Obtain h Parameters. (4)

c. The network shown in Fig.13 consists of a resistive T and a resistive π network connected in parallel. Determine Y parameter for overall network. (8)

**Q.8** An Impedance function has the pole & zero pattern shown in the Fig.14. If  $Z(-2) = -\frac{136}{16}$  obtain Foster – I & Cauer – I forms of this impedance function. (here 0 shows zeros and X shows poles). (16)

**Q.9** a. Show that the  $\frac{V_2}{V_g}$  for Double terminated lattice shown in Fig. 15 is

$$\frac{V_2}{V_g} = \frac{\frac{1}{2}(Z_b - R)}{Z_b + R} \quad (8)$$

b. Draw optimum filter for the transfer impedance.

$$Z_{21}(s) = \frac{0.577}{s^3 + 1.37s^2 + 1.359s + 0.577} \quad (8)$$

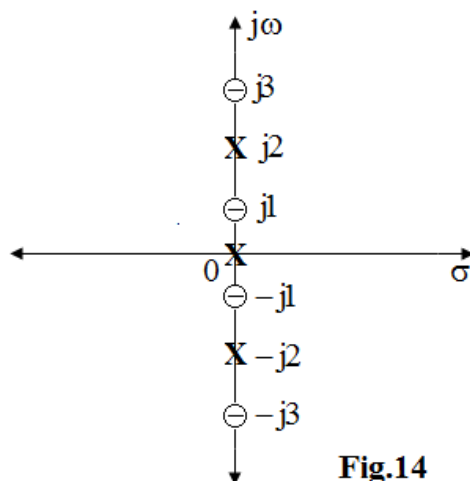


Fig.14

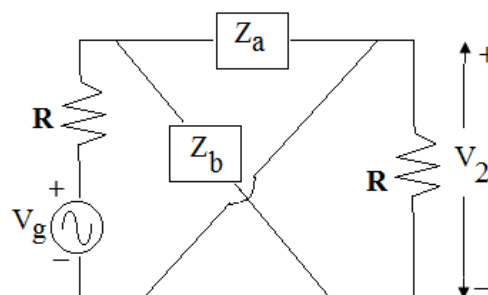


Fig.15