

DiplETE – ET (Current & New Scheme)

Time: 3 Hours

JUNE 2015 - SPECIAL

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Q2 TO Q8 CAN BE ATTEMPTED BY BOTH CURRENT AND NEW SCHEME STUDENTS.
- Q9 HAS BEEN GIVEN INTERNAL OPTION FOR CURRENT SCHEME (CODE DE56) AND NEW SCHEME (CODE DE106) STUDENTS.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

- a. The ion implantation technique used to introduce impurities into a silicon wafer carried at _____.
(A) low temperature (B) high temperature
(C) moderate temperature (D) very high temperature
- b. In a Common Emitter amplifier circuit with an unbypassed emitter resistor
(A) voltage gain decreases (B) current gain increases
(C) input resistance decreases (D) output resistance increases
- c. Field Effect Transistor (FET) is _____ controlled device.
(A) current (B) voltage
(C) resistance (D) capacitor
- d. Class AB power amplifier _____.
(A) increases efficiency (B) increases power output
(C) eliminates crossover distortion (D) consumes more DC power
- e. The diode designed to be sensitive illumination is known as _____.
(A) Zener diode (B) Tunnel diode
(C) Gunn diode (D) Photo diode
- f. The output impedance of an ideal Op – Amp is _____.
(A) Zero (B) Infinity
(C) Low (D) High

- g. The offset current (I_{os}) for BJT Op – Amp is _____.
 (A) 20 nA (B) 200 nA
 (C) 10 pA (D) 200 pA
- h. The slew rate of 741C Op-Amp is
 (A) 5V/ μ S (B) 0.5V/ μ S
 (C) 10V/ μ S (D) 70V/ μ S
- i. Which of the following is an application of a comparator using Op-Amp
 (A) window detector (B) integrator
 (C) differentiator (D) subtractor
- j. The number of comparators required for a 3-bit parallel comparator type A to D converter is _____.
 (A) 3 (B) 5
 (C) 4 (D) 7

Answer any FIVE Questions out of EIGHT Questions.

Each question carries 16 marks.


Q.2 a. With the help of neat diagrams, explain the fabrication of multi-emitter transistor and Schottky transistor. (8)

b. Explain the fabrication of MOSFET with neat diagrams. (8)

Q.3 a. Draw the h – parameter equivalent circuit of Common Emitter circuit with unbypassed emitter resistor. Derive the expressions for
 (i) Input Impedance (ii) Output Impedance
 (iii) Voltage Gain (10)

b. For the circuit shown in **Fig.1** with $h_{ie} = 2.1 \text{ k}\Omega$, $h_{fe} = 75$ and $h_{oe} = 1 \mu\text{S}$. Calculate:

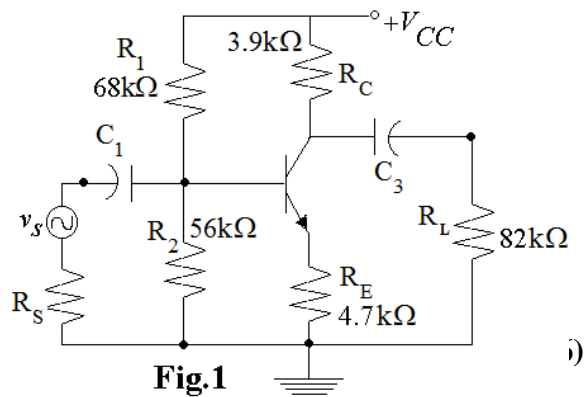- (i) Input Impedance (Z_i),
 (ii) Output Impedance (Z_o)
 (iii) Voltage Gain (A_v)



- Q.4** a. Explain the construction, working and characteristics of Enhancement type MOSFET with the help of suitable diagrams. **(10)**
- b. What are the special precautions necessary to protect MOSFETs from electrostatic discharge? **(6)**
- Q.5** a. Draw the circuit of a transformer-coupled class A power amplifier and explain its operation. **(8)**
- b. Explain the operation and characteristics of photo diode with neat sketches. **(8)**
- Q.6** a. Explain the frequency response of an Operational Amplifier with suitable characteristics. **(10)**
- b. Write the typical values of the following parameters with respect to 741C Op-Amp;
- | | |
|--------------------------|------------------------|
| (i) Input Offset Voltage | (ii) CMRR |
| (iii) SVRR | (iv) Output Resistance |
| (v) Power Consumption | (vi) Slew Rate |
- (6)**
- Q.7** a. Draw the circuit of Op – Amp as subtractor and derive an expression for its output voltage. **(6)**
- b. Write the important features of an Instrumentation Amplifier. **(4)**
- c. Draw and explain Current to Voltage converter using OP-AMP. **(6)**
- Q.8** a. Draw the circuit of Monostable Multivibrator using OP-AMP and derive an expression for the time period ‘T’. **(8)**
- b. Draw and explain the functional diagram of **555** Timer. **(8)**
- Q.9 (For Current Scheme students i.e. DE56)**
- a. Write the characteristics of 3 – Terminal IC voltage regulator. **(8)**
- b. With the help of diagram, explain the working of R-2R ladder digital to analog converter. **(8)**
- Q.9 (For New Scheme students i.e. DE106)**
- a. Draw and explain the circuit of Differential amplifier. **(8)**
- b. With the help of neat diagram, explain the working of weighted resistor type digital to analog converter. **(8)**