

**DiplETE – ET (Current & New Scheme)**

Time: 3 Hours

**JUNE 2015**

Max. Marks: 100

**PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.**

**NOTE: There are 9 Questions in all.**

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Q2 TO Q8 CAN BE ATTEMPTED BY BOTH CURRENT AND NEW SCHEME STUDENTS.
- Q9 HAS BEEN GIVEN INTERNAL OPTIONS FOR CURRENT SCHEME (CODE DE56) AND NEW SCHEME (CODE DE106) STUDENTS.
- Any required data not explicitly given, may be suitably assumed and stated.

**Q.1 Choose the correct or the best alternative in the following: (2×10)**

a.  $\text{SiO}_2$  is an extremely hard protective coating and is unaffected by almost all reagents except \_\_\_\_\_

(A) Hydrofluoric acid

(B) Hydrochloric acid

(C) Sulphuric acid

(D) Cupric acid

b. The voltage gain in a common emitter configuration with bypass capacitor is given by \_\_\_\_\_

(A)  $-R_C/R_E$

(B)  $R_C/R_E$

(C)  $-R_C/r_e$

(D)  $R_C/r_e + R_E$

c. The amplification factor of JFET is equal to \_\_\_\_\_

(A) Sum of  $g_m$  and  $r_d$

(B) Difference of  $g_m$  and  $r_d$

(C) Product of  $g_m$  and  $r_d$

(D) Division of  $g_m$  and  $r_d$

d. The maximum collector efficiency of transformer coupled power amplifier is \_\_\_\_\_

(A) 25%

(B) 78.5%

(C) 50%

(D) 90%

- e. The intensity of light produced by LED is \_\_\_\_\_  
 (A) Directly proportional to the current  
 (B) Inversely proportional to the current  
 (C) Doesn't depend on current  
 (D) Proportional to the square of current
- f. In an op-amp, which of the following adjusts dc voltages so that output voltage is zero for zero inputs?  
 (A) Differential amplifier (B) Level shifter  
 (C) Output stage (D) Input stage
- g. Ideal Op-amps are rarely used in open loop because of its \_\_\_\_\_  
 (A) Infinite Input resistance (B) Zero output resistance  
 (C) Infinite Voltage gain (D) None of these
- h. Which of the following is known as time delay circuit as it generates a fast transition at a predetermined time T after the application of trigger input?  
 (A) Monostable multivibrator (B) Astable multivibrator  
 (C) Bistable multivibrator (D) Schmitt trigger
- i. Which of the following is the application of 555 timer as monostable multivibrator  
 (A) FSK Generator (B) Pulse position Modulator  
 (C) Schmitt trigger (D) Missing pulse detector
- j. The output voltage produced by a D to A converter whose output range is 0 to 10 V and whose input binary number is 0110 (for a four bit DAC) \_\_\_\_\_  
 (A) 5V (B) 3.75V  
 (C) 6V (D) 4.25V

**Answer any FIVE Questions out of EIGHT Questions.  
 Each question carries 16 marks.**

- Q.2** a. Explain with diagrams, the fabrication process of a typical circuit. **(12)**  
 b. Write the advantages of ICs over discrete circuits. **(4)**
- Q.3** a. Draw the circuit of transistor common emitter amplifier with coupling and bypass capacitors and draw its h-parameter equivalent circuit and derive the expression for:  
 (i) Input Impedance (ii) Output Impedance  
 (iii) Voltage gain (iv) Current gain **(12)**  
 b. Define h-parameters. **(4)**

- Q.4** a. Explain the process of amplification using FET. (8)
- b. Explain constructional features and working of Enhancement type MOSFET. (8)
- Q.5** a. Explain the working of class B amplifier and show that its maximum collector efficiency is 78.5%. (10)
- b. Explain the working of phototransistor? (6)
- Q.6** a. What is slew rate of an op-amp and derive an expression for  $f_{\max}$  (maximum input frequency at which undistorted output is obtained) (8)
- b. Draw the voltage follower circuit and write its use. (4)
- c. Design an amplifier with a gain of +5V using one op-amp. (4)
- Q.7** a. Draw the circuit of Non-inverting summing amplifier for 2 inputs using an op-amp and derive the expression for its output voltage. (8)
- b. Draw the circuit of Practical Differentiator and derive the expression for its output voltage. (8)
- Q.8** a. Explain the working of Square Wave Generator using op-amp and derive the expression for its time period (T). (8)
- b. Draw the functional block diagram of 555 IC and explain. (8)
- Q.9 (For Current Scheme students i.e. DE56)**
- a. What is meant by a voltage regulator? Draw the block diagram of a regulated power supply and explain the function of its various components. (8)
- b. Explain the parallel comparator A to D converter with the help of suitable diagram and give its applications. (8)
- Q.9 (For New Scheme students i.e. DE106)**
- a. Explain how a solar cell differs from a photodiode. Sketch the typical solar cell characteristics and explain. (8)
- b. Draw the functional diagram of the successive approximation A to D converter and explain its operation. (8)