

Time: 3 Hours

JUNE 2013

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q. 1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions, selecting at least TWO questions from each part, each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

- a. An Op-amp act as a voltage follower has a voltage gain of
- | | |
|--------------|---------------------|
| (A) Infinity | (B) Zero |
| (C) Unity | (D) Less than unity |
- b. A bistable multivibrator is a
- | | |
|------------------------------|--------------------------|
| (A) Free running oscillator | (B) Triggered oscillator |
| (C) Saw tooth wave generator | (D) Crystal oscillator |
- c. A virtual ground
- | | |
|-----------------------------|---|
| (A) is a ground for voltage | (B) is a ground for both voltage and current |
| (C) is ground for current | (D) is a ground for voltage but not for current |
- d. An ideal differential amplifier has CMRR equaling
- | | |
|--------------|-----------------------|
| (A) Unity | (B) – 1 (minus unity) |
| (C) Infinity | (D) Zero |
- e. When a sinusoidal voltage wave is fed to a Schmitt trigger, the output will be
- | | |
|---------------------|----------------------|
| (A) triangular wave | (B) square wave |
| (C) d.c. | (D) trapezoidal wave |
- f. The large signal bandwidth of an opamp is limited by its
- | | |
|----------------------|---------------------|
| (A) Loop gain | (B) slew rate |
| (C) output impedance | (D) input frequency |
- g. A 'literal' in Boolean Algebra means
- | | |
|--|---|
| (A) a variable in its uncomplemented form only | (B) a variable ORed with its complement |
| (C) a variable in its complemented form only | (D) a variable in its complemented or uncomplemented form |

- h. Simplified expression of $xy + xyz + \bar{x}y + x\bar{y}z$ is
- (A) $\bar{y} + x\bar{z}$ (B) $\bar{x} + \bar{y}z$
 (C) $y + xz$ (D) $y + \bar{x}z$
- i. In an SR flip flop $S = 1$ and $R = 1$ gives
- (A) Set state (B) Reset state
 (C) Indeterminate state (D) None of these
- j. The logic gate which detects equality of two bits is
- (A) EX-OR (B) EX-NOR
 (C) NOR (D) NAND

PART (A)

Answer At least TWO questions. Each question carries 16 marks.

- Q.2** a. Classify ICs on the basis of applications, devices used and chip complexity. (8)
- b. In the differential amplifier circuit shown below, the transistors have identical characteristics and their $\beta = 100$. Determine the (8)
- (i) output voltage
 (ii) the base currents and
 (iii) the base voltages taking into account the effect of the R_B and V_{BE} .
 Assume $V_{BE} = 0.7$ Volts, $R_B = 25K\Omega$, $R_C = 12K\Omega$ and $R_E = 8K\Omega$.
 $V_{EE} = -12V$, $V_{CC} = +12V$

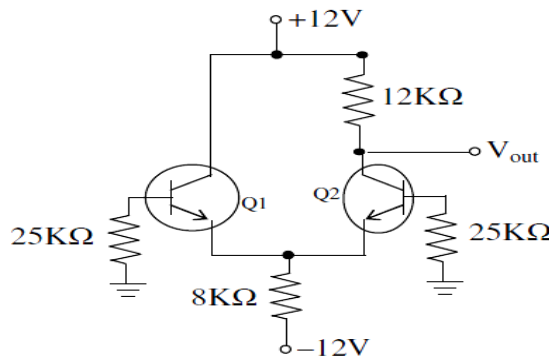


Fig.1

- Q.3** a. Explain what you understand by 'offset voltage' and 'offset current' of op-amp. Discuss with a neat circuit diagram the technique used for minimizing offset voltage and offset current in an inverting amplifier. (10)
- b. Calculate the output voltage ' V_0 ' for the following non-inverting op-amp summer with $V_1 = 2V$ and $V_2 = -1V$ (6)

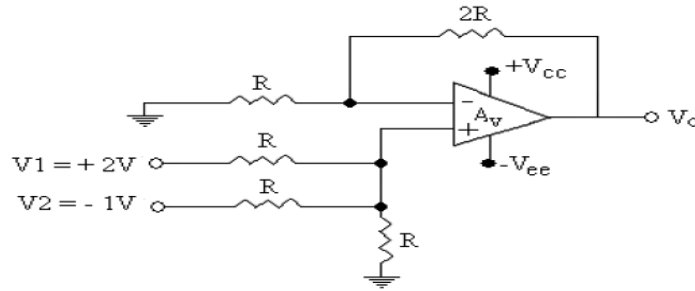


Fig.2

- Q.4**
- Explain Schmitt trigger with the help of transfer characteristics. Also obtain the expression of hysteresis voltage V_H and output waveform for sinusoidal input signal. (8)
 - The input to an op-amp differentiator circuit is a sinusoidal voltage of peak value $10\mu\text{V}$ and frequency of 2 kHz. If the values of differentiating components are given as $R = 40\text{ k}\Omega$ and $C = 3\mu\text{F}$, determine the output voltage of differentiator circuit. (8)
- Q.5**
- Explain the working of R-2R Ladder Digital to Analog Converter. (6)
 - Explain Monostable multivibrator circuit operation using 555 timers. Also, determine the frequency of output signal. (6)
 - Explain the working of Series Op-Amp Regulator. (4)

PART (B)

Answer At least TWO questions. Each question carries 16 marks.

- Q.6**
- Differentiate between analog and digital signals. (4)
 - Explain the concept of Parity bits with reference to error detection. (6)
 - Convert the following: (6)
 - $(5A34F)_{16}$ to binary
 - $(56)_{10}$ to Gray Code
 - $(93)_{10}$ to Excess-3 Code
- Q.7**
- Simplify the Boolean function 'F' together with don't care conditions 'd' in sum of Products
 $F(w, x, y, z) = \sum(0,1,2,3,7,8,10)$
 $d(w, x, y, z) = \sum(5,6,11,15)$ (6)
 - State and prove De Morgan's theorem using truth table. (6)
 - Show that NAND gate is a Universal gate. (4)
- Q.8**
- Explain the 4-bit parallel binary adder. (8)
 - Write a short note on 8: 1 Multiplexers. (8)
- Q.9**
- Draw and explain the working of NAND-gate latch. (6)
 - Distinguish between synchronous and asynchronous counters. Design a 3-bit UP-DOWN synchronous counter. (10)