

AMIETE – ET

Time: 3 Hours

JUNE 2013

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.


Q.1 Choose the correct or the best alternative in the following: (2×10)

a. A 100Ω resistance is connected across a 10V battery. The energy consumed in 5 secs is

- (A) 3 Joules (B) 4 Joules
(C) 5 Joules (D) 6 Joules

b. The current I_{ab} in the circuit shown in Fig.1 is

- (A) 1A (B) 2A
(C) 3A (D) 4A

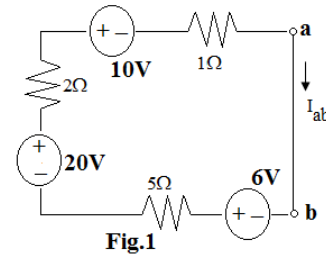

c. The correct statement is _____

- (A) $V_L = L \frac{di}{dt}$ and $i_c = C \frac{dv}{dt}$ (B) $i_L = L \frac{dv}{dt}$ and $V_c = C \frac{di}{dt}$
(C) $V_L = L \frac{di}{dt}$ and $i_L = C \frac{dv}{dt}$ (D) $V_c = L \frac{dv}{dt}$ and $i_c = C \frac{di}{dt}$

d. Laplace transform of $f(t) = e^{at} u(t)$ is

- (A) $\frac{1}{s^2}$ (B) $\frac{1}{s+a}$
(C) $\frac{1}{s-a}$ (D) $\frac{1}{(s+a)^2}$

e. The Quality factor of a purely resistive circuit is

- (A) 0 (B) 1
(C) 1.5 (D) infinite

f. The impedance of one port network $Z(s) = \frac{15(s^3 + 2s^2 + 3s + 2)}{s^4 + 6s^3 + 8s^2}$ indicates

- (A) Double pole at origin (B) Double zeros at origin
(C) Single pole at origin (D) Single zero at origin

g. The current $i(t)$ corresponding to transform current $I(s) = \frac{1}{s(s+1)}$ is

(A) $i(t) = (1 - e^{-t})u(t)$

(B) $i(t) = (1 + e^{-t})u(t)$

(C) $i(t) = e^t u(t)$

(D) $i(t) = e^{-t} u(t)$

h. The Thevenin resistance as seen at ab of the circuit in Fig.2 is

(A) 5Ω

(B) 8Ω

(C) 10Ω

(D) 12Ω

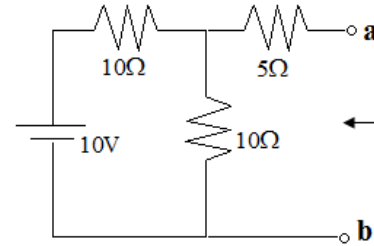


Fig.2

i. The duty cycle of a square wave is

(A) 40%

(B) 50%

(C) 60%

(D) All of these

j. The minimum phase function has zeros of transmission on

(A) $j\omega$ axis only

(B) $j\omega$ axis or in left half of s -plane

(C) $j\omega$ axis or right half of s -plane

(D) in left half of s -plane only

Answer any FIVE Questions out of EIGHT Questions.

Each question carries 16 marks.

Q.2 a. A battery has an internal resistance of 0.5Ω and open circuit voltage of 12V. What is power lost in the battery and terminal voltage on full load if a resistance of 3Ω is connected across the terminals of the battery? (4)

b. In the Fig.3, find the current in the resistances using node analysis. (6)

c. Find v_o using Kirchhoff's laws in the circuit as shown in Fig.4. Given that $r_1 = 1000\Omega$, $r_2 = 500\Omega$, $r_3 = 50\Omega$, $r_4 = 5\Omega$, $\alpha = 0.5$, $\beta = 2$ and $v_s = 10V$. (6)

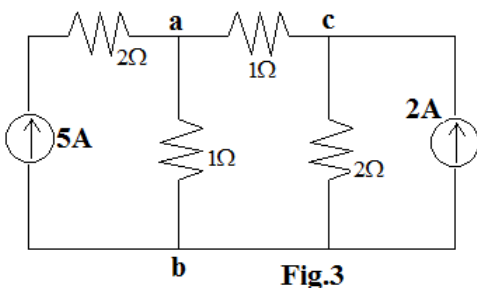


Fig.3

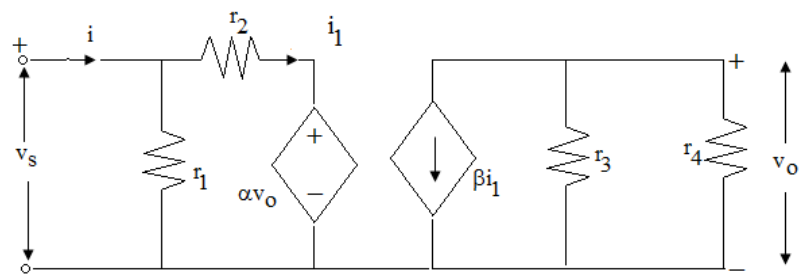


Fig.4

- Q.3** a. For the circuit given in Fig.5, switch K is closed at $t = 0$. Find the i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$. (6)

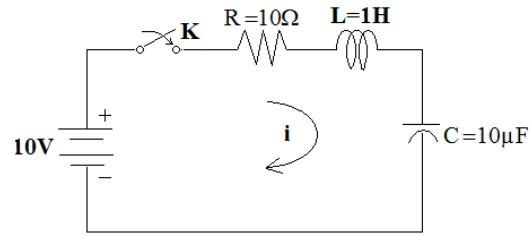


Fig.5

- b. Find the general solution of the equation $2\frac{di}{dt} + i(t) = 2i(t)$ with initial condition at $t = 0$, $i = 5A$. (4)
- c. A voltage of $v = 200 \sin(314t - 30^\circ)$ is applied to a $50mH$, 15Ω coil; calculate the current and the power factor for the arrangement. (6)

- Q.4** a. Using Laplace transform technique, find i_2 at $t = 0^+$ when switch k is closed at $t = 0$ in Fig.6. (8)

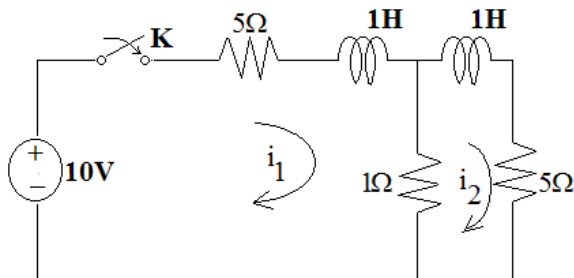


Fig.6

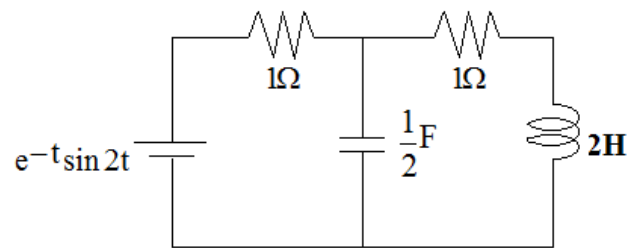


Fig.7

- Q.5** a. Determine $Z(s)$ and $I(s)$ for the network shown in Fig.7 using transform network. (8)
- b. Consider the network shown in Fig.8. Calculate $i_1(t)$ using Thevenin's theorem. (8)

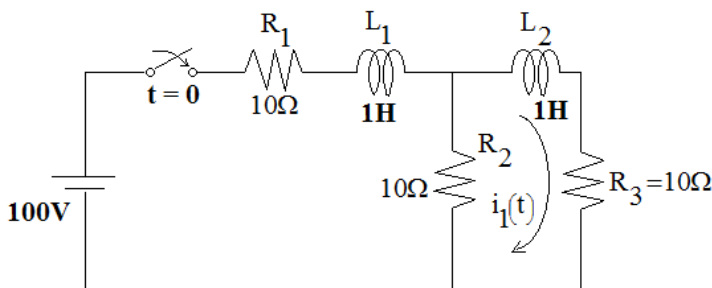


Fig.8

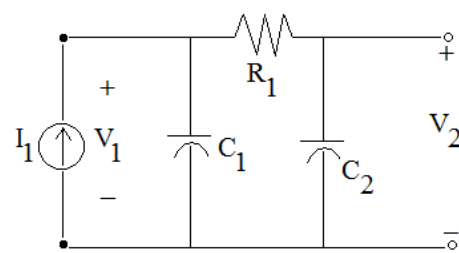


Fig.9

Q.6 a. Compute the current gain $\alpha_{12}(s)$ and driving point impedance $Z_{12}(s)$ for the network shown in Fig.9 with $C_1 = 1F$, $R_1 = 1\Omega$ and $C_2 = 2F$. (8)

b. A network function is given by $H(s) = \frac{2s}{(s+2)(s^2+2s+2)}$. Obtain pole-zero diagram. (4)

c. Check the positive realness of the function $F(s) = \frac{s^2+10s+4}{s+2}$. (4)

Q.7 a. Determine the Z-parameter of the network shown in Fig.10. (6)

b. The Z-parameter of a circuit are given by $\begin{bmatrix} 4 & 1 \\ 3 & 3 \end{bmatrix}$. Obtain the transmission line ABCD parameters. (4)

c. Establish the relation between Impedance parameters (Z) and hybrid parameters (h). (6)

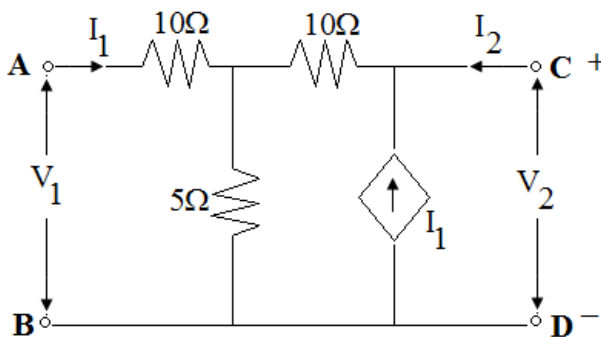


Fig.10

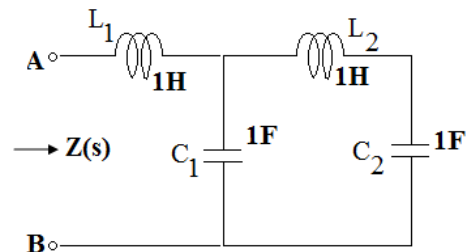


Fig.11

Q.8 a. Obtain the driving point impedance of the given network across A-B shown in Fig.11 using Transform network. (8)

b. The driving point impedance of an LC network is $Z(s) = \frac{10(s^2+4)(s^2+16)}{s(s^2+9)}$. Obtain Foster form of network. (8)

Q.9 a. What are the error criteria in any approximation problem in network theory? Derive amplitude approximation for maximally flat low pass filter approximation. (8)

b. Synthesize the voltage ratio $\frac{V_2}{V_1} = \frac{s^2+1}{s^2+2s+1}$ as a constant resistance bridged-T network terminated in a 1Ω resistor. (8)