

AMIETE – ET (Current & New Scheme)

Time: 3 Hours

JUNE 2017

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct or the best alternative in the following: (2×10)

- a. If there are 'b' branches and 'n' nodes the number of equations will be:
 (A) n-1 (B) b
 (C) b-n-1 (D) b-n+1
- b. Kirchoff's laws are applicable to circuits with:
 (A) Distributed parameters (B) Lumped parameters
 (C) Passive elements (D) Non-linear resistances
- c. The electrical energy required to raise the temperature of a given amount of water is 200kwh. If the heat losses are 20%., total energy required is:
 (A) 250 kwh (B) 240 kwh
 (C) 160 kwh (D) None of these
- d. An independent voltage source in series with an impedance $Z_s = R_s + jX_s$ delivers a maximum average power to a load impedance Z_L when
 (A) $Z_L = R_s + jX_s$ (B) $Z_L = R_s$
 (C) $Z_L = jX_s$ (D) $Z_L = R_s - jX_s$
- e. The first and the last critical frequencies (singularities) of a driving point impedance function of a passive network having two kinds of elements, are a pole and a zero respectively. The above property will be satisfied by
 (A) RL network only (B) RC network only
 (C) LC network only (D) RC as well as RL networks
- f. Consider the following statements S1 and S2
 S1: At the resonant frequency the impedance of a series *RLC* circuit is zero.
 S2: In a parallel *GLC* circuit, increasing the conductance *G* results in increase in its *Q* factor.
 Which one of the following is correct?
 (A) S1 is FALSE and S2 is TRUE (B) Both S1 and S2 are TRUE
 (C) S1 is TRUE and S2 is FALSE (D) Both S1 and S2 are FALSE
- g. The period of the signal $x(t) = 8 \sin(0.8\pi t + \pi/4)$ is
 (A) 0.4π s (B) 0.8π s
 (C) 1.25s (D) 2.5s

- h. The initial current through the inductor is zero, while the initial capacitor voltage is 100V. The switch is closed at $t=0$. The current i through the circuit is:
- (A) $5\cos(5 \times 10^3 t)$ A (B) $5\sin(10^4 t)$ A
 (C) $10\cos(5 \times 10^3 t)$ A (D) $10\sin(10^4 t)$ A
- i. If we double the voltage in a simple dc circuit and cut the resistance to half, then the current will
- (A) Become four times (B) Become twice
 (C) Stay the same as it was before (D) Become half as great
- j. The average power delivered to an impedance $(4 - j3)\Omega$ by a current $5\cos(100\pi t + 100\pi)$ A is
- (A) 44.2W (B) 50W
 (C) 62.5W (D) 125W

**Answer any FIVE Questions out of EIGHT Questions.
 Each question carries 16 marks.**

- Q.2** a. Find V_a , V_b , and V_c in the network of Fig.2 (a) using nodal analysis. (10)

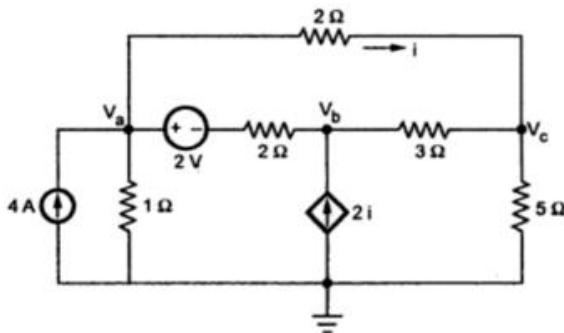


Fig.2 (a)

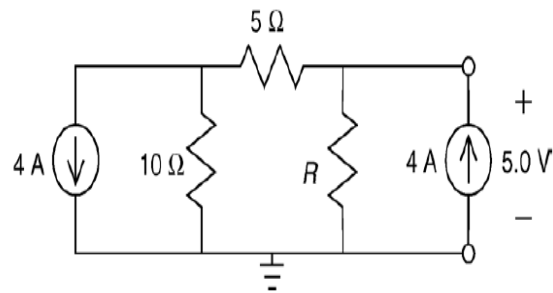


Fig.2 (b)

- b. Consider the circuit shown in Fig.2 (b). Find the value of the resistance, R using source transformation technique. (6)

- Q.3** a. Find the current $i(t)$ for the network in Fig.3. When the voltage source is $e(t)=2e^{-0.5t}u(t)$ and $v_C(0^-) = 0$ (9)

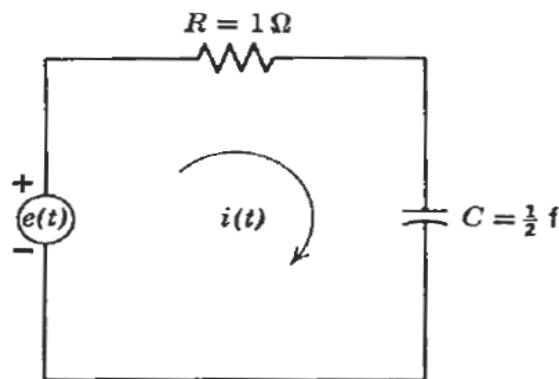


Fig.3

- b. Find particular solutions for the differential equation $\frac{d^2 i}{dt^2} + 3\frac{di}{dt} + 2i = 0$ subject to the initial conditions: $i(0^+) = 1, \frac{di(0^+)}{dt} = 0$ (7)

- Q.4** a. State and prove the following properties of Laplace Transform (2+3+3)
 i) Modulation, ii) Multiplication by t^n , iii) Derivative

- b. Given that $F(s) = \frac{12(s+1)(s+3)}{s(s+2)(s+4)(s+5)}$, find the inverse Laplace transform using partial fraction expansion method (8)

- Q.5a. In the circuit shown in the figure Fig.5 (a), find the value V_{TH} and R_{TH} , (3+3)

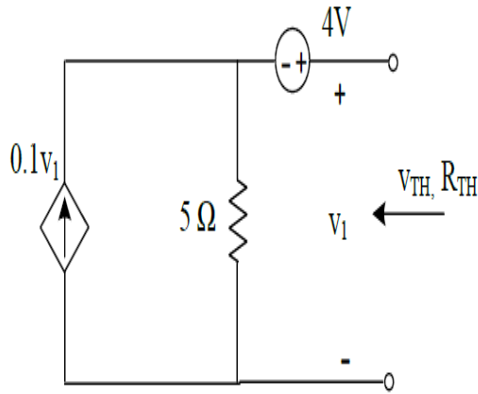


Fig.5 (a)

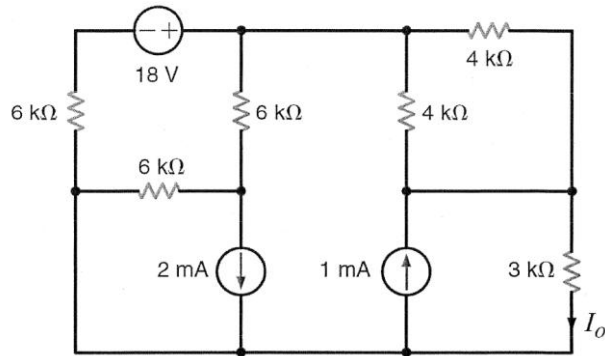


Fig.5(b)

- b. State the superposition theorem and find I_0 in the network shown in Fig.5 (b). (10)

- Q.6 a. Determine the ABCD parameters of the network shown in Fig.6 (a). (6)

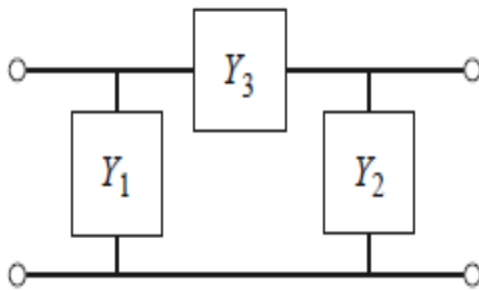


Fig.6 (a)

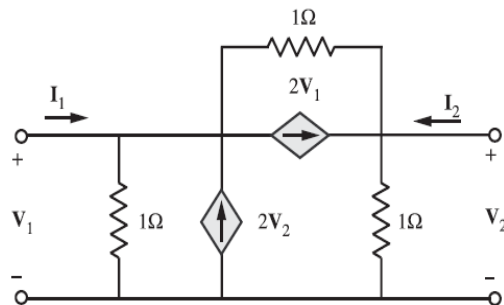


Fig.6 (b)

- b. Determine y and z parameters of the network of Fig.6 (b) (10)

- Q.7 a. Test whether the polynomial $P(s)$ is Hurwitz polynomial or not. (7)
 $P(s) = s^4 + 3s^3 + 5s^2 + 5s + 2$

- b. Find the transform impedance $Z(s)$ of the given one port network shown in Fig.7 (4)

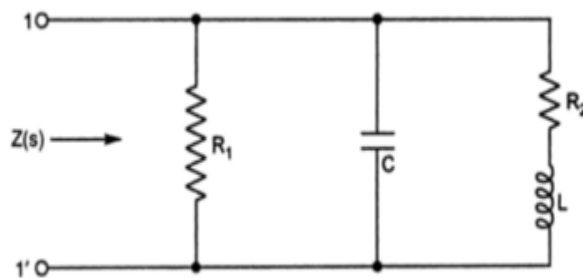


Fig.7

- c. The transfer function of a system is given $G(s) = \frac{s+3}{s(s^2+2)}$, determine its response for unit step input. (5)

- Q.8 a. Write the properties of LC-impedance functions and find whether $Z(s)$ is LC function or not? $Z(s) = \frac{s^5+4s^2+5s}{3s^4+6s^2}$ (8)

- b. Synthesize the following impedance function using II form of Cauer network. (8)

$$Z(s) = s \frac{(s^2+3)(s^2+5)}{(s^2+2)(s^2+4)}$$

- Q.9 a. Synthesize the following function $Z_{21}(s)$ into the form shown in Fig.9 (a) (9)

$$Z_{21}(s) = \frac{2}{s^3 + 3s^2 + 4s + 2}$$

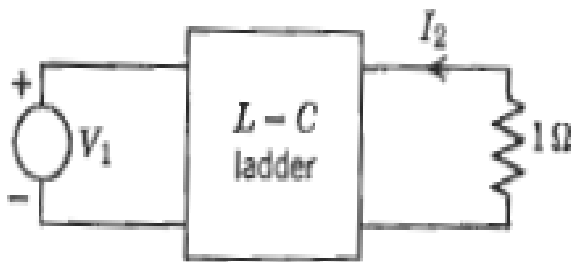


Fig.9 (a)

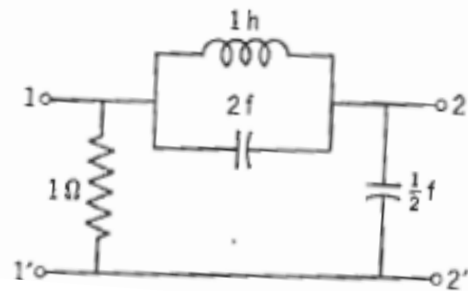


Fig. 9(b)

- b. Show that the residue condition holds for the network shown in Fig.9 (b) (7)