

DiplETE – ET (New Scheme)

Time: 3 Hours

JUNE 2017

Max. Marks: 100

PLEASE WRITE YOUR ROLL NO. AT THE SPACE PROVIDED ON EACH PAGE IMMEDIATELY AFTER RECEIVING THE QUESTION PAPER.

NOTE: There are 9 Questions in all.

- Question 1 is compulsory and carries 20 marks. Answer to Q.1 must be written in the space provided for it in the answer book supplied and nowhere else.
- The answer sheet for the Q.1 will be collected by the invigilator after 45 minutes of the commencement of the examination.
- Out of the remaining EIGHT Questions answer any FIVE Questions. Each question carries 16 marks.
- Any required data not explicitly given, may be suitably assumed and stated.

Q.1 Choose the correct answer or best alternative in the following (2×10)

- a. Where is the ROC defined or specified for the signals containing causal as well as anti-causal terms?

(A) Greater than the largest pole	(B) Less than the smallest pole
(C) Between two poles	(D) Cannot be defined

- b. Which result is generated/ obtained by the addition of a step to a ramp function?

(A) Step Function shifted by an amount equal to ramp
(B) Step function of zero slope
(C) Ramp function of zero slope
(D) Ramp Function shifted by an amount equal to step

- c. $L[f''(t)]$ is:

(A) $SL[f''(t) - f(0)]$	(B) $F(s)$
(C) $SL[f(t)]$	(D) $F(s+a)$

- d. What should be the value of Laplace transform for the time-domain signal equation $e^{-at} \cos \omega t \cdot u(t)$?

(A) $a / (s + a)$ with ROC $\sigma > -a$
(B) $\omega / \{(s + a)^2 + \omega^2\}$ with ROC $\sigma > -a$
(C) $A\omega / (s^2 + \omega^2)$ with ROC $\sigma > 0$
(D) $s + a / \{(s + a)^2 + \omega^2\}$ with ROC $\sigma > -a$

- e. For high efficiency of transfer of power, internal resistance of the source should be

(A) Inversely proportional	(B) less than the load resistance
(C) more than the load resistance	(D) equal to the load resistance

- f. Which operation is likely to get executed or performed by Millman's theorem in terms of converting the voltage or current sources into a single equivalent voltage or current source?

(A) Subtraction	(B) Differentiation
(C) Combination	(D) Integration

- g. In a series RLC circuit that is operating above the resonant frequency, the current
 (A) is zero (B) is in phase with the applied voltage
 (C) lags the applied voltage (D) leads the applied voltage
- h. A certain series resonant circuit has a bandwidth of 2 kHz. If the existing coil is replaced with one having a higher value of Q, the bandwidth will
 (A) increase (B) be less selective
 (C) decrease (D) remain the same
- i. What is the meaning of the term velocity factor of a transmission line?
 (A) The velocity of the wave on the transmission line multiplied by the velocity of the wave of light in vacuum.
 (B) The ratio of the characteristic impedance of the line to the terminating impedance
 (C) The index of shielding for coaxial cable
 (D) The velocity of the waves on the transmission line divided by the velocity of light in a vacuum
- j. What is the input impedance of a shorted lossless line of length wavelength/4?
 (A) Z_0 (B) infinity
 (C) 0 (D) complex


**Answer any FIVE Questions out of EIGHT Questions.
 Each question carries 16 marks.**

- Q.2** a. Find the Laplace transform of (8)

$$f(t) = \begin{cases} t^2, & 0 \leq t \leq 1 \\ \sin 2t, & 1 < t < \pi, \\ \cos t, & t > \pi \end{cases}$$


- b. Find the Laplace transform of $t \cdot \cos(\omega t)$ (8)

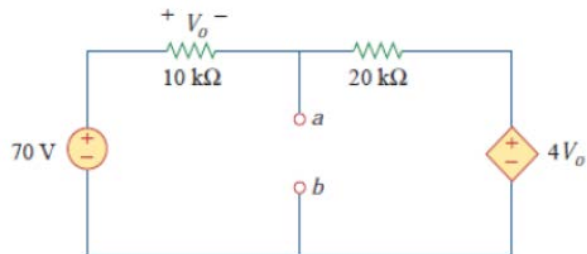- Q.3** a. Find the Thevenin Equivalent Voltage at terminals a-b of the circuit



(8)

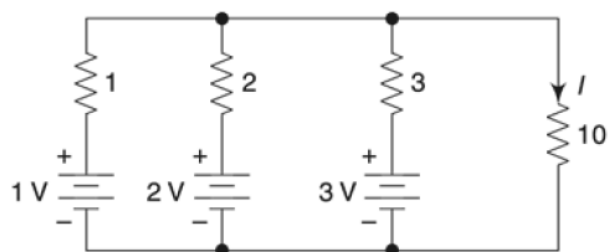
- b. Find the Load current using Millman's theorem. All resistance values are in ohms



(8)

- Q.4** a. The bandwidth of a series resonant circuit is 400 Hz.
 (i) If the resonant frequency is 4000 Hz, what is the value of Q?
 (ii) If R is 10 ohm then, what is the value of X at resonance?
 (iii) Find the inductance L and capacitance C of the circuit. (8)

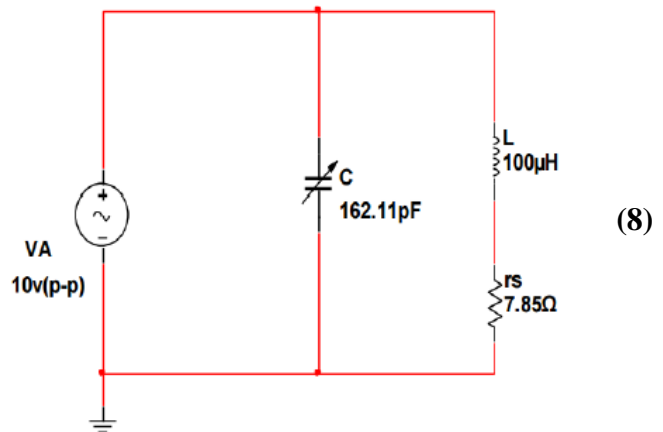- b. Find the value of Resonance frequency, Inductive reactance, Capacitive reactance, Total impedance of the circuit, Total current supplied by voltage source, Q factor, and band width of the given circuit.



- Q.5** a. A transmission line operating at 300 MHz has $Z_0 = 60 \text{ ohm}$, $\alpha = 0.02 \text{ Np/m}$, $\beta = 0.6 \text{ rad/m}$ Find the line parameters R, L, G, and C (8)

- b. How does frequency distortion occur in a line? (4)

- c. Define the following
 (i) Reflection Loss (ii) Reflection Coefficient (4)

- Q.6** a. A certain transmission line operating at $\omega = 10^6 \text{ rad/s}$ has $\alpha = 8\text{dB/m}$, $\beta = 1\text{rad/m}$ and $Z_0 = 60 + j40 \text{ ohm}$ and is 2 m long. If the line is connected to a source of $10 \angle 0^\circ \text{ V}$, $Z_g = 40 \text{ ohm}$ and terminated by a load of $20 + j50 \text{ ohm}$. Determine
 (i) The input impedance
 (ii) The sending end current
 (iii) The current at the middle of the line (10)

- b. A single phase transmission line has two parallel conductors 3m apart, the radius of each conductor being 1 cm. Calculate the loop inductance per km length of the line if the material of the conductor is (i) copper (ii) steel with relative permeability of 100. ($\mu_r = 1$) (6)


- Q.7** a. Describe various characteristics of filters. (8)

- b. What are balanced and unbalanced attenuators? (8)


- Q.8** a. An antenna with impedance $40 + j30 \text{ ohm}$ is to be matched to a 100 ohms lossless line with a Shorted stub. Determine
 (i) The required stub admittance
 (ii) The distance between the stub and the antenna
 (iii) The stub length (10)

- b. For the given transmission line calculate and sketch the voltage at the load and generator ends for $0 < t < 6 \mu s$

(6)

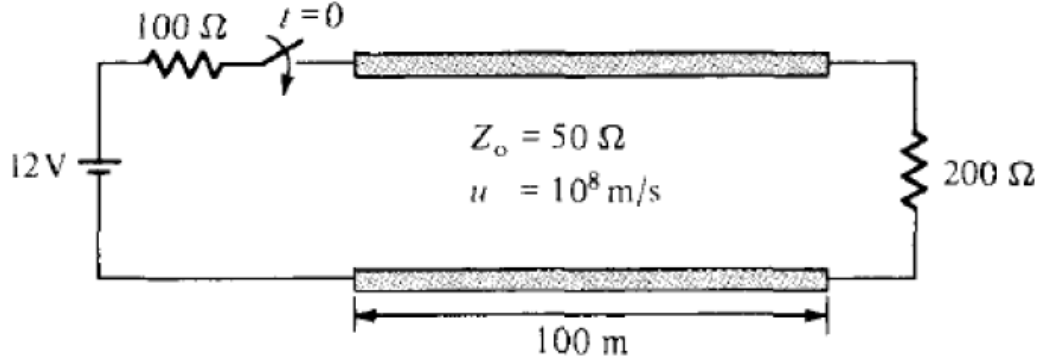

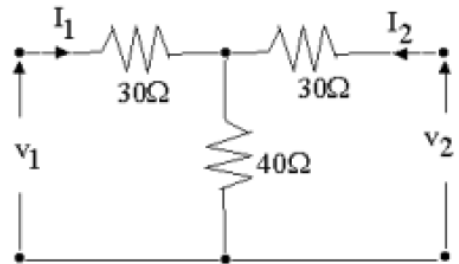- Q.9 a. Find the z-and ABCD-parameters of given network and also prove the property of symmetry of the network



(8)

- b. Find the Y parameter of the given network

(8)

